

HAROLD E. EDGERTON

PAPERS

MC 25

SERIES 3. LABORATORY NOTEBOOKS

NUMBER: T-1

DATED: 26 September 1927 TO 16 July 1931

Sept. 26, 1927
July 16, 1931

NOTEBOOK T 1

THYRATRON'S. I.
Massachusetts Institute of Technology

COMPUTATION BOOK

NAME

H. E. EDGERTON

Course

Used from SEPT 26 1929, to JULY 16 1931

RECEIVED
MAR 22 1937
U.S. PATENT OFFICE

Sept. 26, 1929
July 16, 1931

United States Patent Office
Before the Examiner of Interferences


Truckees:
vs. : Interference 73,473

Edgerton Exhibit 23
Notebook T 1

Mar. 1, 1937

Clara Schlosky
Notary Public

BLAKE
NOTARY PUBLIC
NEW YORK

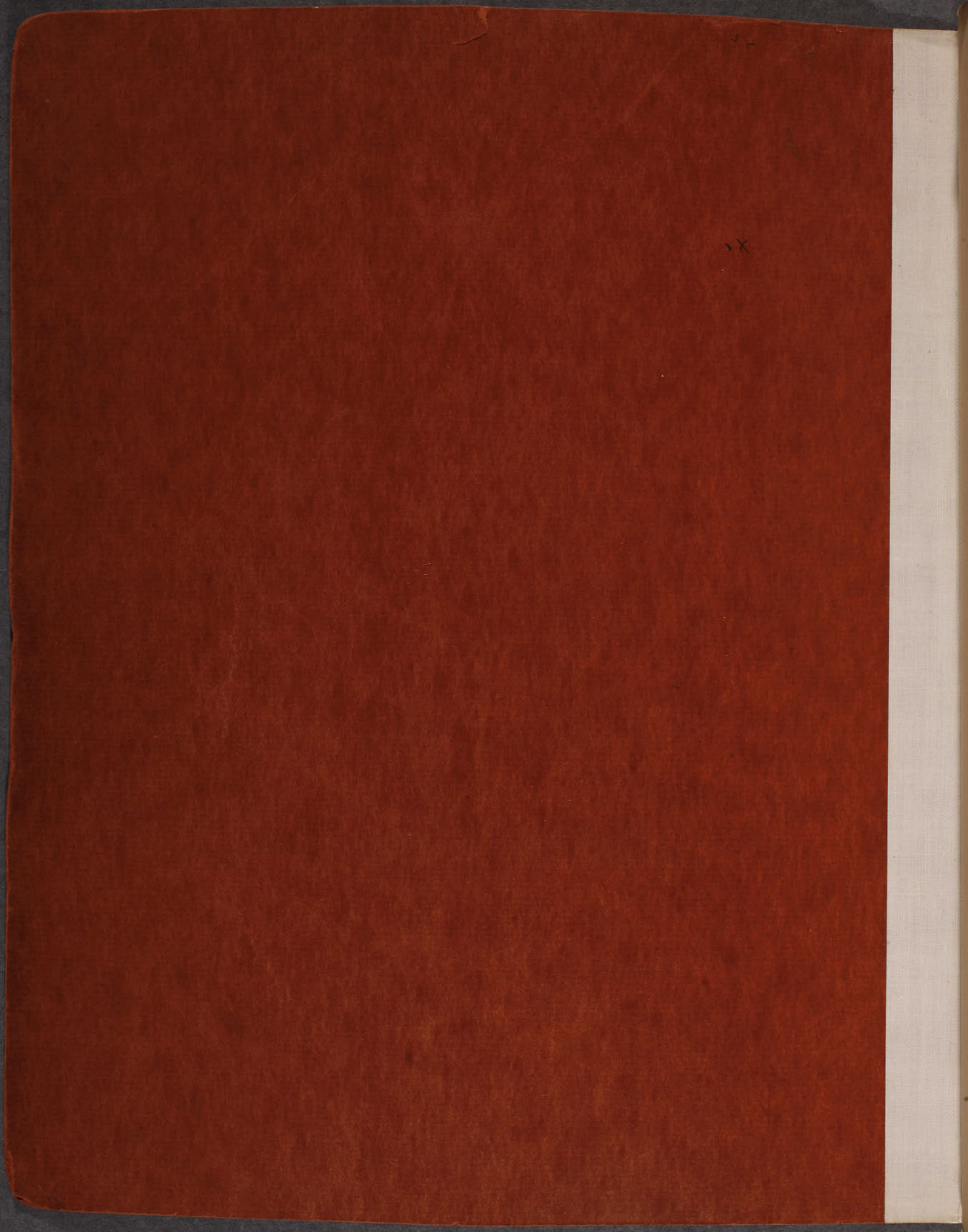

10-13-1927.
Edgerton


Speed Control.

For various purposes in the laboratory it is desirable to have a source of constant frequency alternating current. This frequency must be exactly 60 cycles.

There is a motor generator set in the laboratory rated 5 kW on the a. c. generator. The motor is run from the 250 volt d. c. mains. This is the set we wish to have run at a constant speed.


Speed Control by the Thyatron Tube.

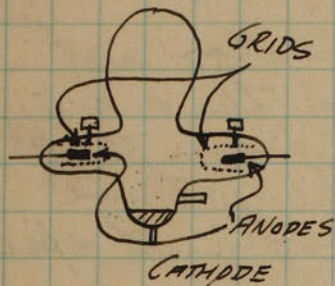A mercury arc rectifier is made by the General Electric Co which has grids around the anodes. This rectifier is called the thyatron. The sketch shows the general layout of the tube.



field current.

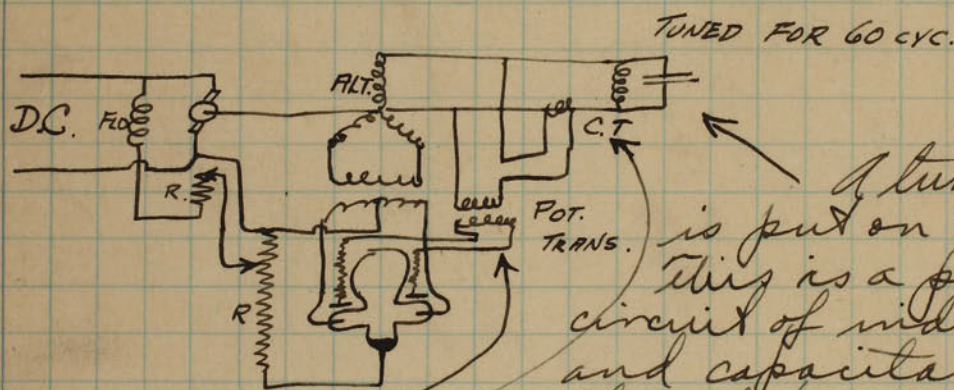
The circuit shown below was devised to control speed of the D.C. motor by varying its



A tuned circuit is put on the alternator. This is a parallel circuit of inductance and capacitance and is tuned for 60 cycles.

A current transformer is put in the line going to the tuned circuit. Its secondary is connected in series with the primary of the grid potential transformer.

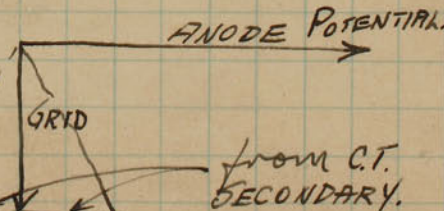The whole scheme of control is to shift the phase relation between the grid potential and the anode potential. These ^{are} shown on a vector diagram ~~are shown~~. To the grid potential is added a potential which depends upon the frequency. This comes from the C.T. in the tuned circuit



Notebook Number: T-1

Scanning and Separation Record


___ unmounted photograph(s)

___ negative strip(s)

3 unmounted page(s)
(notes, drawings, letters ...)

was/were scanned where originally located between page
4 and 5.

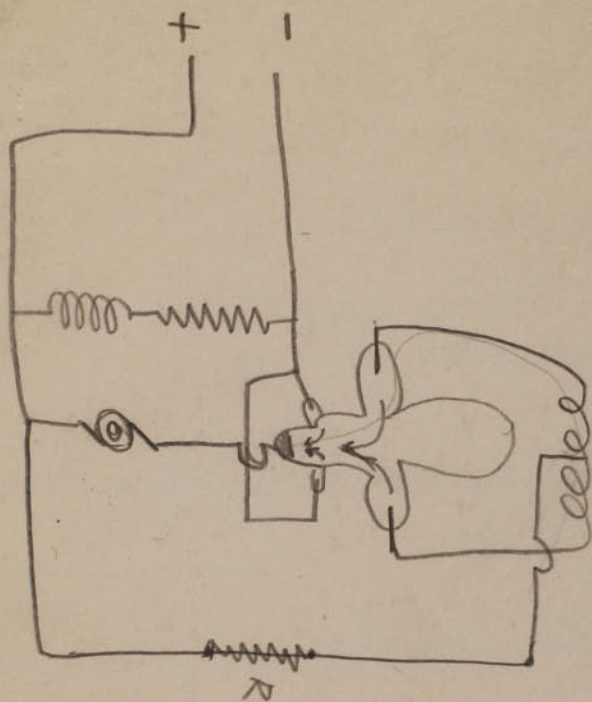Item now housed in accompanying folder in MC 25, box 166





12:20


12-130

mass




"

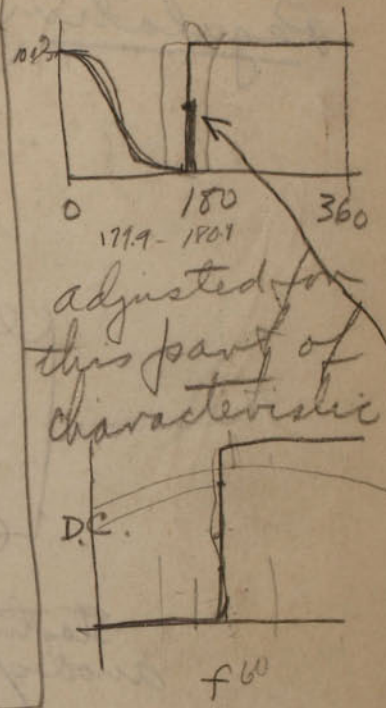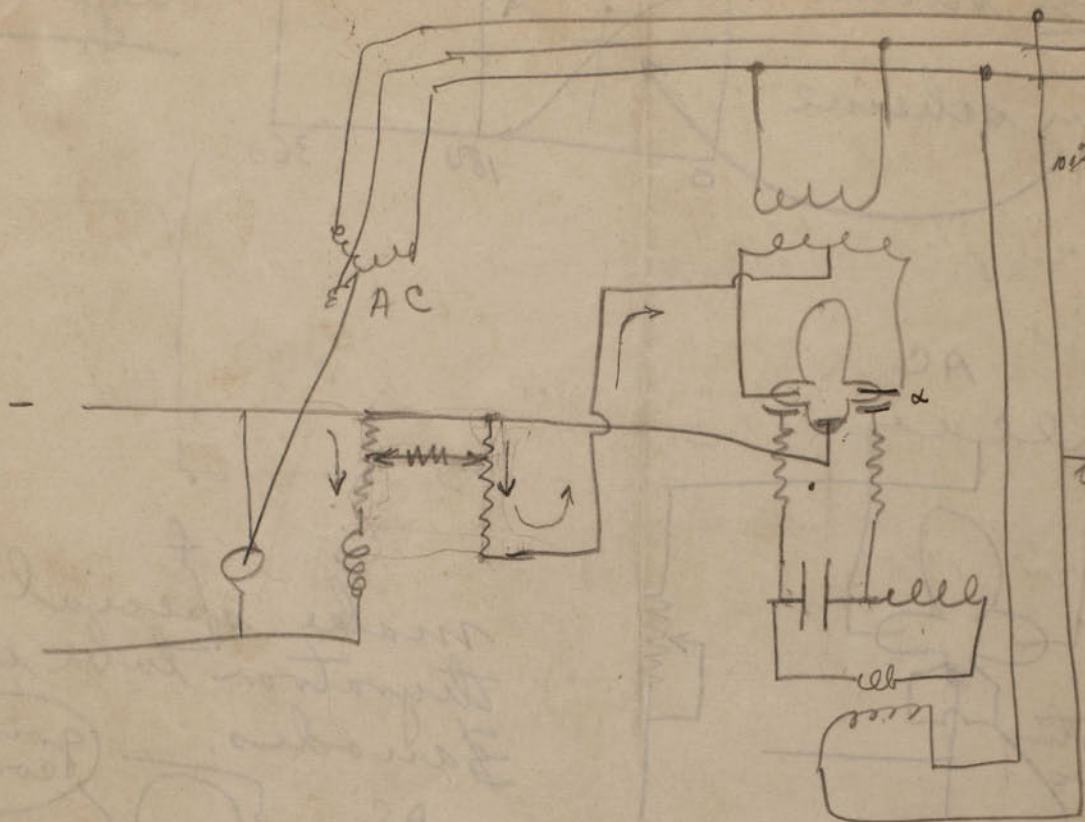

adjusted for
this part of
characteristic


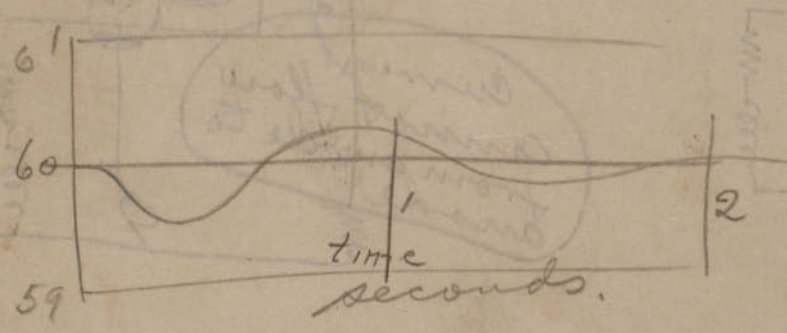


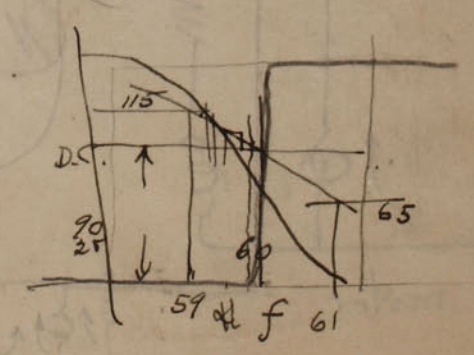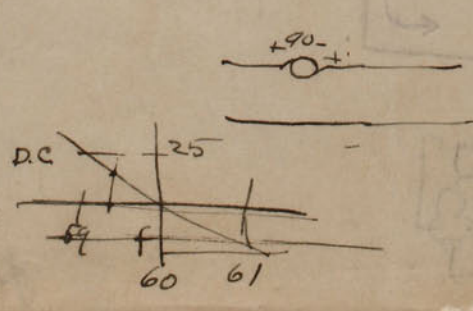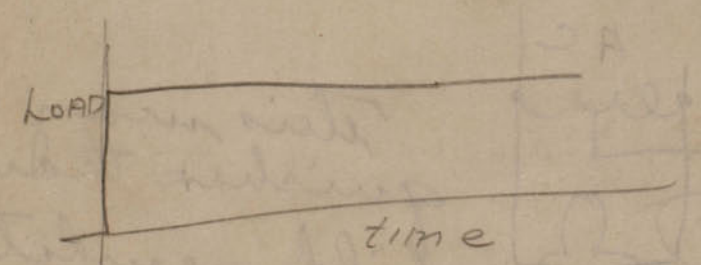Holds
 $60.00 \pm .05$
for all
loads from
0 to 150%





10-20-1927
Edgerton,

Off and on scheme
or
Regulation scheme


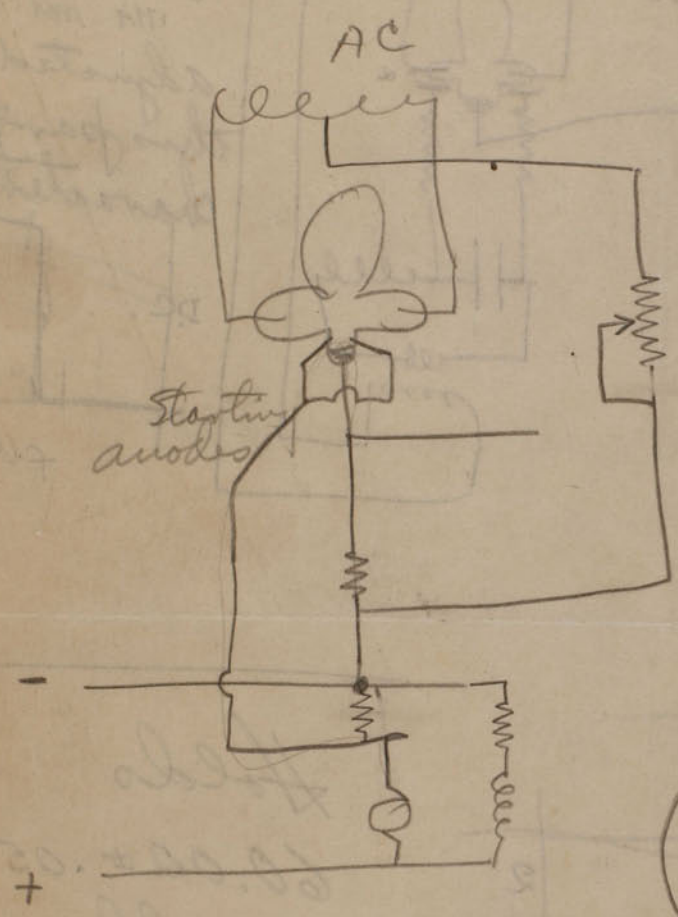
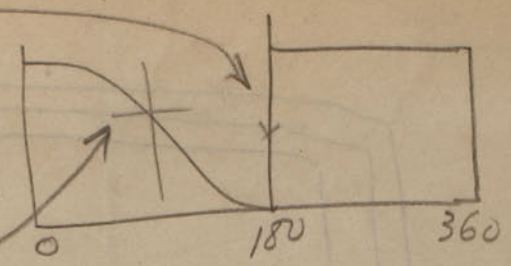


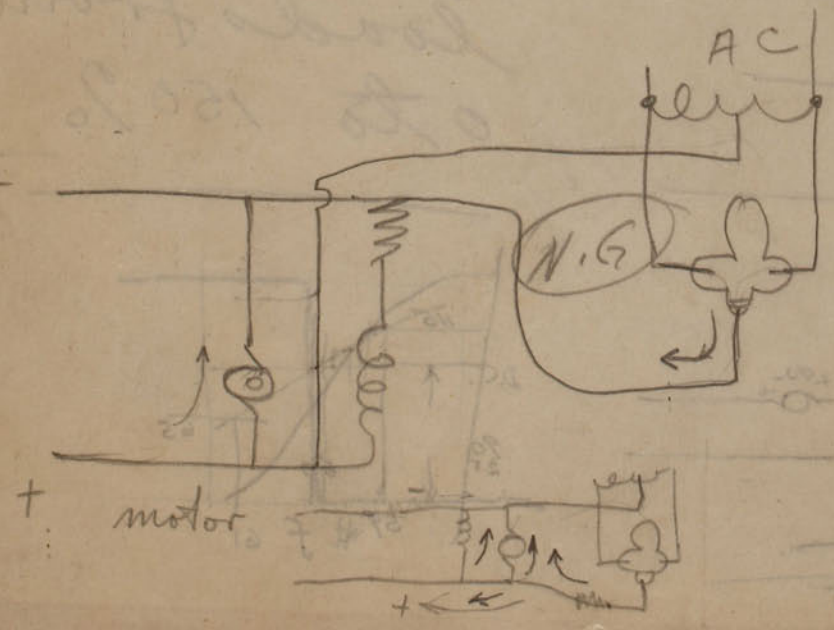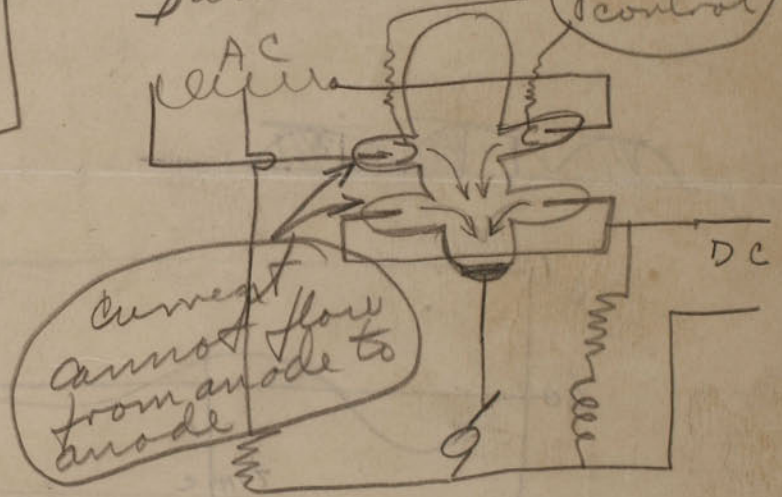make special
thyatron tube with
3 anodes. grid control



This may be
quicker than the
field regulation.

over for
present hookup

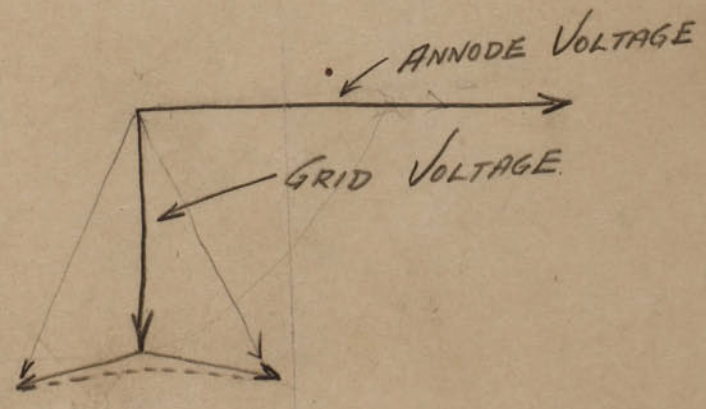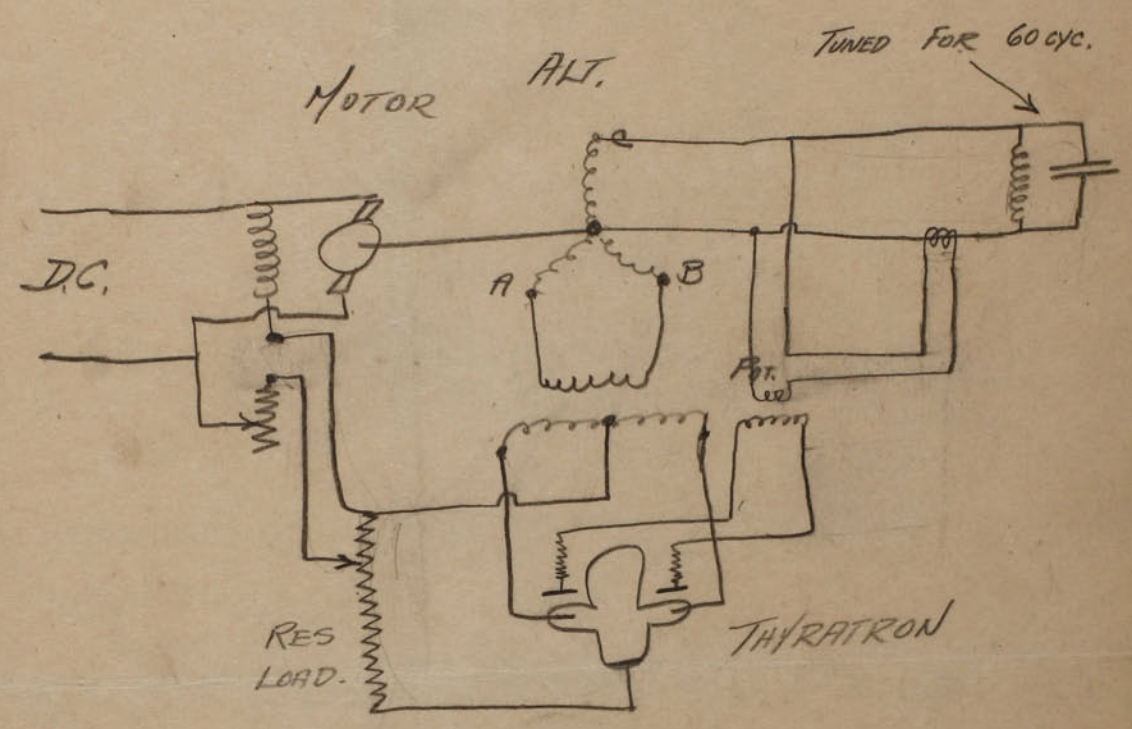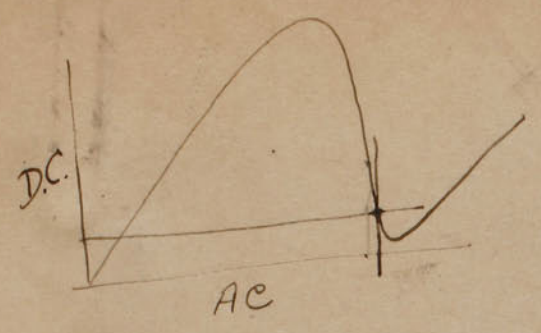

VARIATION CAUSED
BY FREQ. CHANGE.


METHOD OF SPEED CONTROL

H. E. EDGERTON
SEPT. 15, 1927.

10-13-27
Edgerton

The rectifier supplies current to a ~~rectifier~~ resistance load. From this any percentage may be tapped off to control the D.C. motor field as shown in the wiring diagram.

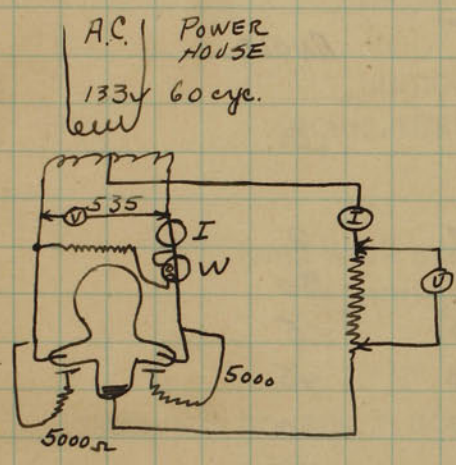A 20 ampere thyatron tube has been purchased and will now be tested.




Load curve.

This was not carried farther due to the rating of the transformer supplying the anode voltage.

← A.C. →				← D.C. →	
V	I	W	f.	E	I
K	D	x20	D	D	D
528	1.23	22.	60	217	1.62
527	1.65	30	60	216	2.20
527	1.86	34	60	216.5	2.44
524	2.31	43	60	215.0	3.05
520	2.78	51	60	214.0	3.65
518	3.17	58.5	60	213.0	4.17
520	3.52	66.0	60	215.0	4.67
522	3.79	69.8	60	215.0	5.02
538	-	-	60	220	-


10-13-27
Edgerton

PENCIL CONNECTIONS USED FOR PAGE 7.

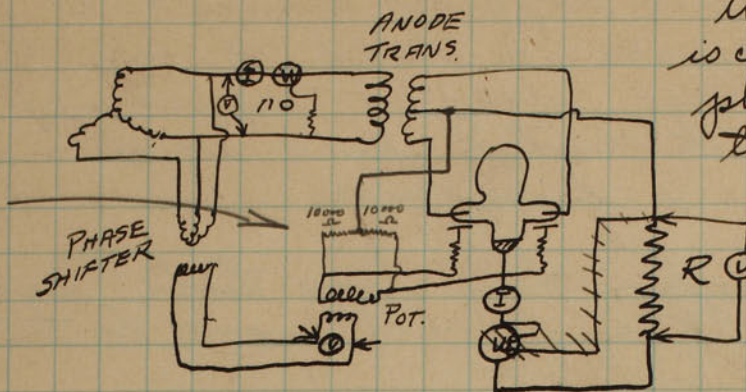

The grid circuit is connected to a phase shifter to investigate the effect of phase shift between the two.

← A.C. →					← D.C. →		ANGLE.
V	I	W	f	V _G	V	I	
K D	D	20	D	DX10?	D	D	D.
420	3.34	49.4	60	110	169	4.39	0
420	3.07	42.5	60	113	136	3.57	30
420	3.26	47.5	60	112	160	4.15	15
422	2.72	33.5	60	115	108	2.83	45
424	2.22	22.0	60	113	74	1.90	60
430	1.72	12.0	60	117	41	1.06	75
433	1.38	8.5	60	118	29	.73	90
438	1.05	5.5	60	118	17.0	.48	105
442	-	2.5	60	117	10.0	.26	120
444	-	-	60	118	3.0±	.10	135
443	-	-	60	118	-	-	150
							180
							210
							240
418	3.32	49.5	60	115	169	4.38	248
				116			300
				115			330
				112			360

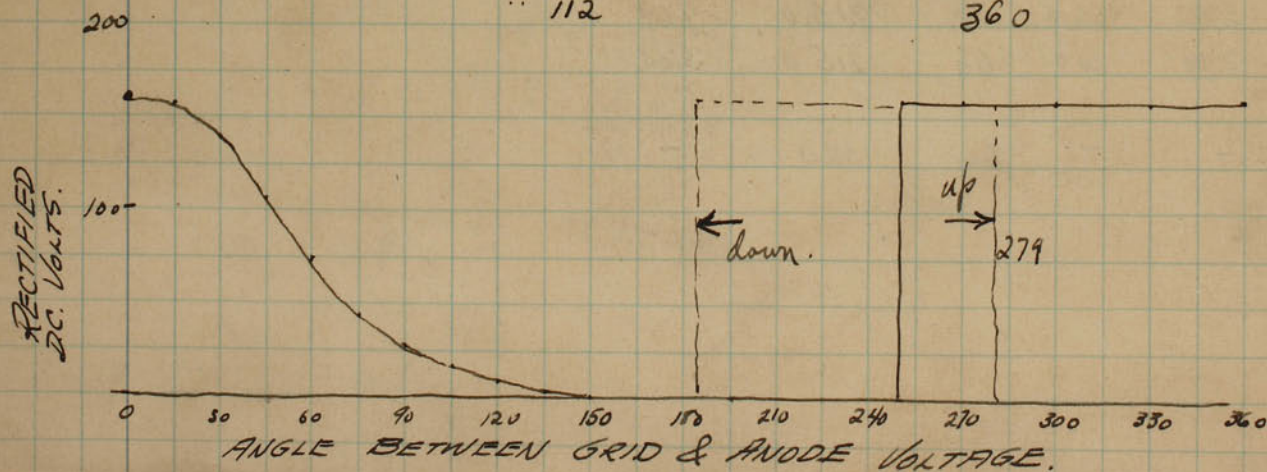

Notebook Number: T-1

Scanning and Separation Record


___ unmounted photograph(s)

___ negative strip(s)

1 unmounted page(s)
(notes, drawings, letters ...)

was/were scanned where originally located between page
6 and 7.

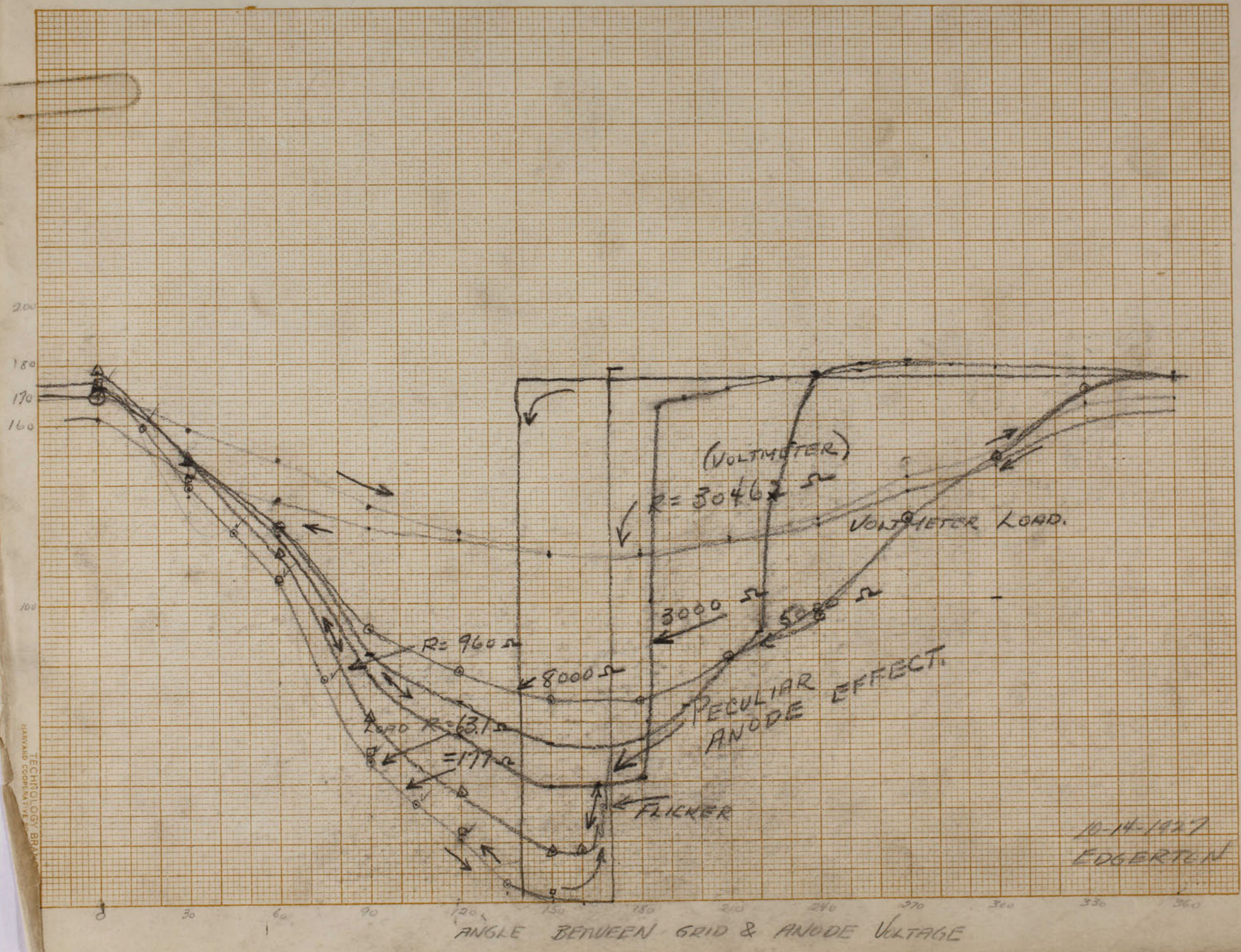Item now housed in accompanying folder in MC 25, box 166




10-14-1927
 EDGERTON

HARVARD UNIVERSITY
 TECHNOLOGY DEPARTMENT

A 60 cycle tuned circuit. (parallel)


Three condensers 8.8 mf 9.78 mf. 8.49 mf.
and an air core reactance with a variable
reactance (mutual) i.e. variable coupling,
connected in parallel.

Test of circuit containing condensers

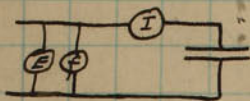

E	f	I
111	60	1.13

Inductive circuit

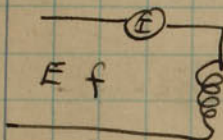


E	f	I
111	60	1.33

$1.33 - 1.13 = .20$ amperes of leading current
needed. This requires a condenser of a capacity.

$$C = \frac{I}{2\pi f E} = \frac{.20}{111 \cdot 377} = 4.78 \text{ m.f.}$$


A total of 31.75 mf is needed for resonance
to occur at 60 cycles. Three condensers were
obtained (1.95 + 2.28 + .50) mf. bringing the total
to 31.8 mf. The .5 mf condenser burnt out so
only 31.3 mf remains.

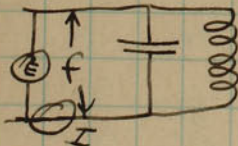The parallel circuit was now
connected up and found to be O.K.



E	f	I
110	55.7	.235
110	57.25	.190
110	56.1	.198 MA143
110	57.35	.158
110	59.3	.128
110	61.3	.136
110	62.2	.154
110	60.4	.127
110	59.8	.126


10-14-27
Edgerton

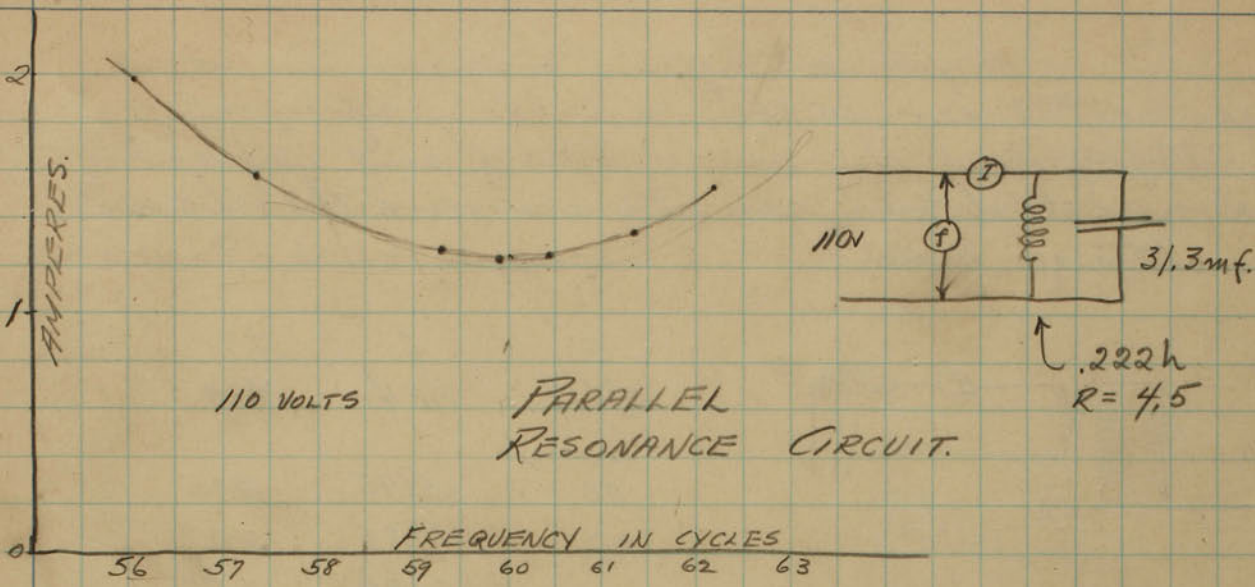

This curve shows that the parallel resonance circuit will not give critical enough control to hold the frequency within limits desired.

By using a great deal more condensers in parallel and a smaller reactance with a smaller resistance this curve could be made much sharper in the V portion. This was not considered feasible because of the bulk needed by the condensers.

SERIES RESONANCE

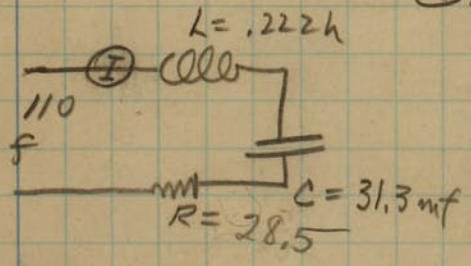


E	f	I
MV14	Mf4	MA9
110	61.1	3.42
110	59.3	3.48
110	57.5	3.47
110	56.3	3.42

Worse than the Parallel!


This can be made sharper by reducing the resistance but doing this allows the current to become excessive. A Potential transformer will cut this down by reducing the voltage impressed.

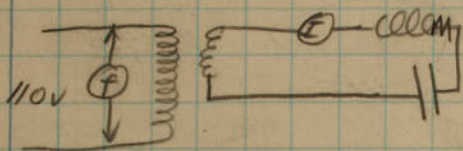A filament lighting transformer was connected across the variable frequency supply and the inductance and capacity connected in series across the low voltage side.




E MV14
f MF4
I MA9.

110	58.45	2.15
110	59.85	2.21 ?
	61.60	1.77
	62.1	1.60
	58.1	1.95
	57.1	1.64
	58.8	2.1
	59.1	2.17
	60.65	2.0
	58.6	2.15

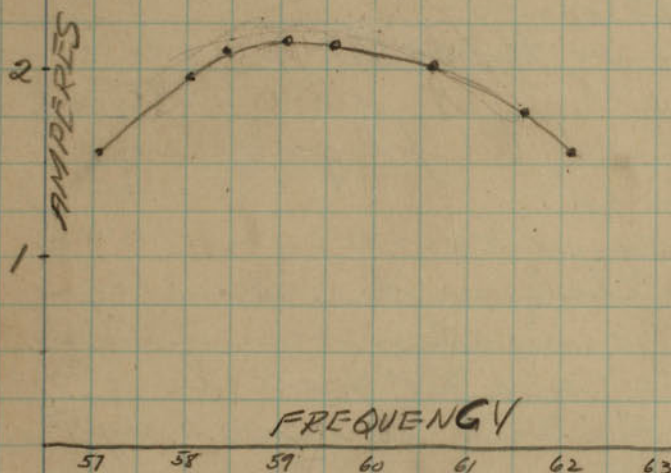

E	f	X5 W	I'	MV12 E'	cos θ	θ
110	62.8	29	1.63	126	.809	36
110	60.8	47.3	2.12	148	1.00	0
110	59.05	38.5	1.90	132	.921	23
110	57.5	23.8	1.47	103	.737	43

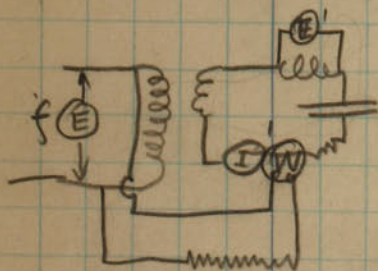


57	94	0
57.7	104	
59.3	135	
60.8	148	
63	125	

This looks better!! The magnitude swings some but the important thing is that the angle varies over a wide range, and it is the determining factor.


10-14-27

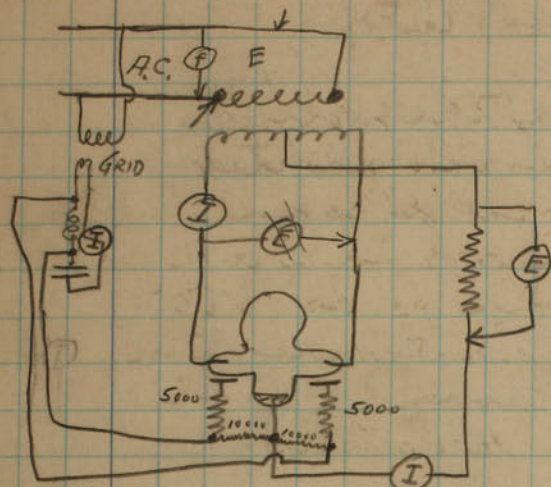The idea now is to take the drop off the inductance, put it through the grid transformer. This drop gives a voltage which swings with frequency.



The drop across the inductance was found to be large enough to control the tube.

		A.C.		D.C.	
E	I	f	I_T	E	I
106	.5±	58	1.41	127	.72
149		58.8 (60)	1.82	115	
		59.7 (59.2)	1.67	100	
		60.45 (58.7)	1.62	78	
		60.9 (60.5)	1.91	66	
114±		62.0 (61)	1.89	40	

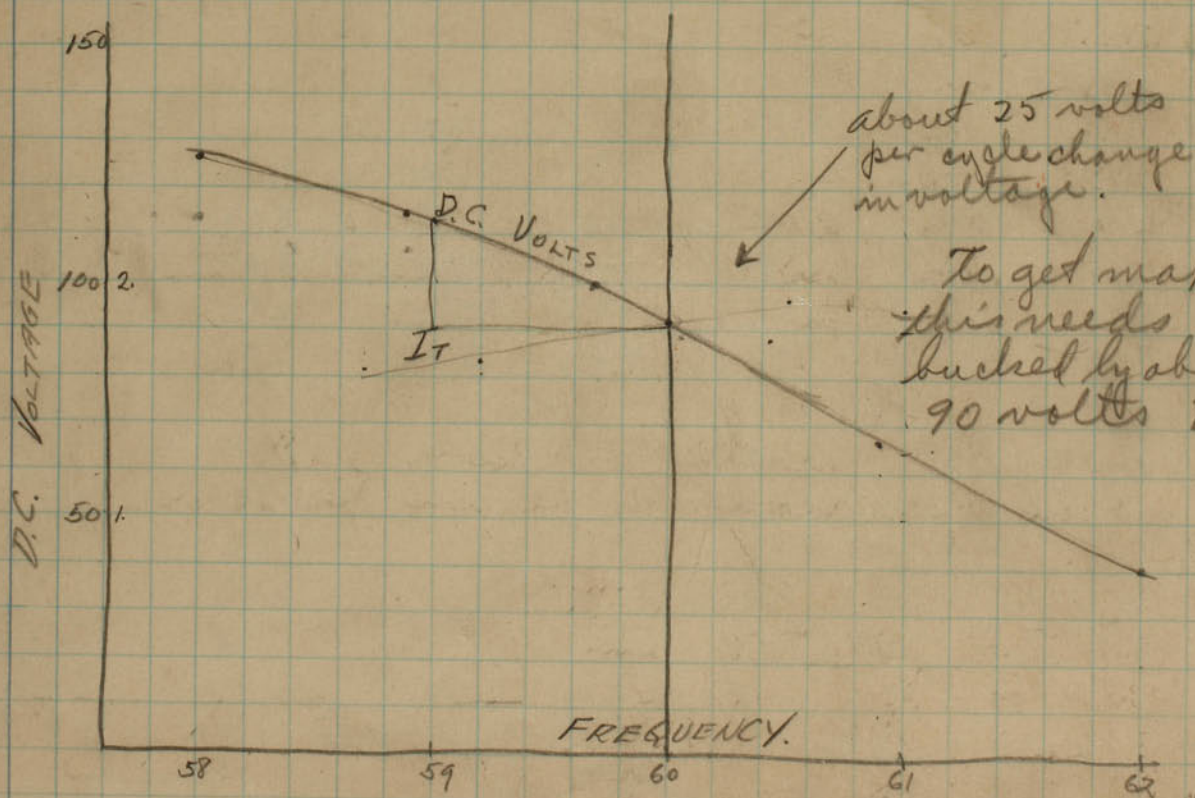



Camb. Mass.
May 29 1929

-18-27
Lester


When using the vertical cutoff point of a thyatron tube by having the grid ^{voltage} about $180 \pm$ degrees from the anode, trouble is experienced due to inductance in the circuit.

The angle which allows the anode to conduct is ~~less~~ different than the angle which stops the conduction.

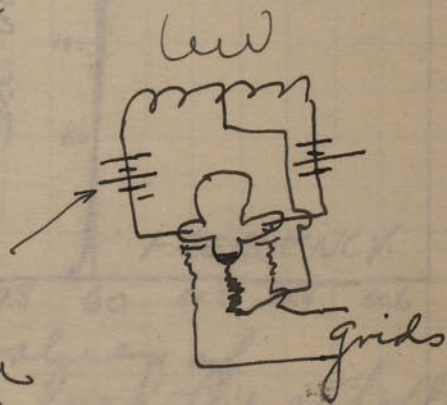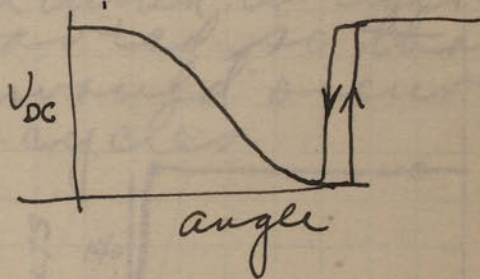
This may be remedied by putting in a biasing battery in the anode circuit as shown in the figure.



The object of these batteries is to have the instantaneous anode voltage negative until the other anode is through with its conduction. The size of the batteries will be determined by the ac. anode voltage and the inductance.

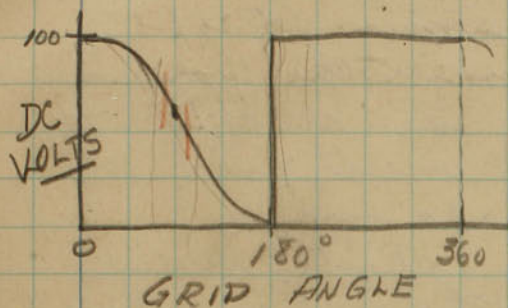
10-18-27
EdgertonScheme using Vertical Cutoff.

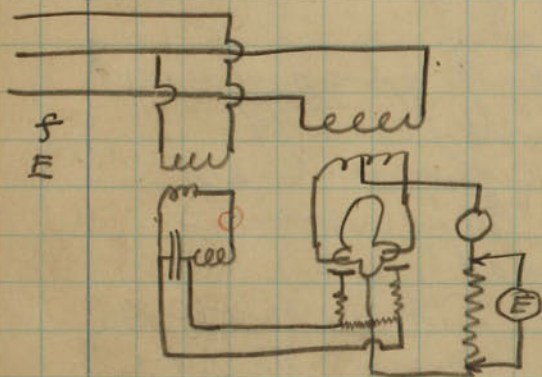Observing the voltage rectified curves plotted against grid phase angle, we notice an abrupt cutoff at 180° when the load resistance has an ohmic value less than 100 ohms.




Connecting the apparatus up as indicated in the following wiring diagram gives us the below readings. L in the tuned circuit was varied so that cutoff would occur at 60 cycles.

F	f.	E_{DC}	I_{DC}
443	59.0	0	0
451	59.95	0	0
	59.99	20 ± 10	
	60.0+	$90 \pm$	
	60.02	$120 \pm$	
438	60.10	176	2.86
440	60.6	177	2.88

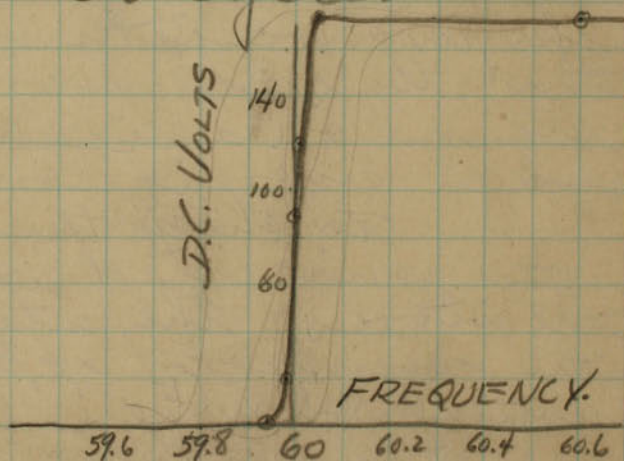

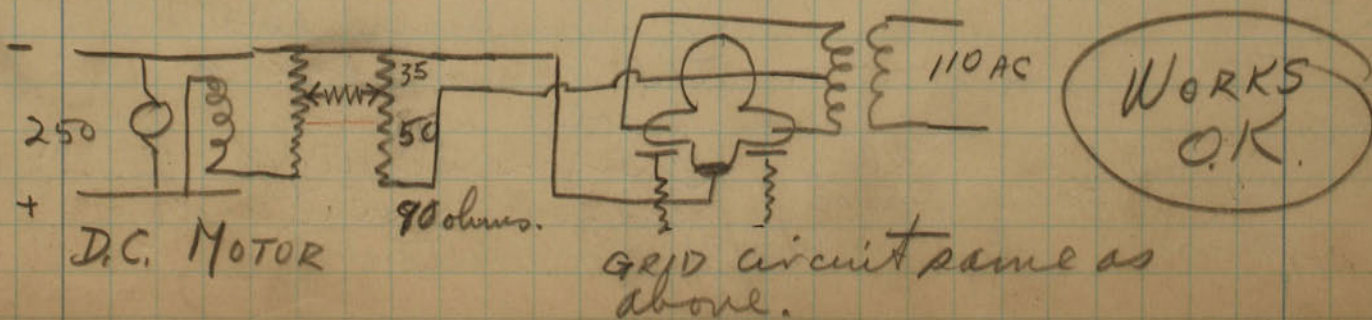It checks also on decreasing values of frequency. With $176/12$ ohms load the cutoff and cutoff voltage differ by .4 cycles and the slope appears to be vertical on both.



GRID circuit same as above.

10-19-1929
Edgerton

I connected up the outfit the same as yesterday except I used a lower tap on the anode transformer (3850). This was done in order to cut down the power required from the a.c. supply since apparently the cutoff occurred at 1 amp. rectified D.C. Also slide wire resistances were substituted for the heavy stove resistances used yesterday. The values of current and the % voltages were about the same as before.


When I tried to regulate frequency I found that the cuton and cutoff occurred about at a difference in frequency of .5 cycle. This made speed regulation terrible!!

Connecting in the stoves which were used in the previous test the regulation was again o.k.

Looking for differences between the two resistances it is observed that the slide wire resistance is wound on a iron tube (enameled), which gives it considerable inductance.

To check this guess, inductance was connected in series with the stoves. The cutoff varied with the manner of approaching as was noticed ~~was~~ when the slide wire resistances were used.

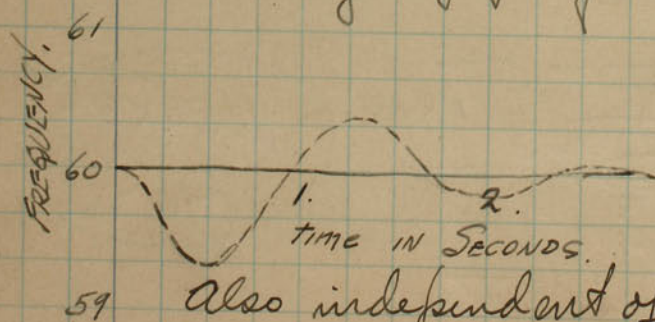With load on the A.C. generator no change of frequency was evident.



also independent of dc or a.c. voltages.

Sudden switching of $1\frac{1}{2}$ times full load on the A.C. Generator gives a frequency curve similar to the one sketched.

field not enough of the
can be used.


Ratio of L and C for a resonant circuit

$$f = \frac{1}{2\pi\sqrt{LC}} \quad f=60$$

$$\sqrt{LC} = \frac{1}{377} = .00265$$


$$LC = .00000702 = 7.02 \times 10^{-6}$$

	50	60	70
$2\pi f$	314	377	440
$\frac{1}{2\pi f}$.00318	.00265	.00227
$()^2$	10.1	7.02	5.16
			$\times 10^{-6}$

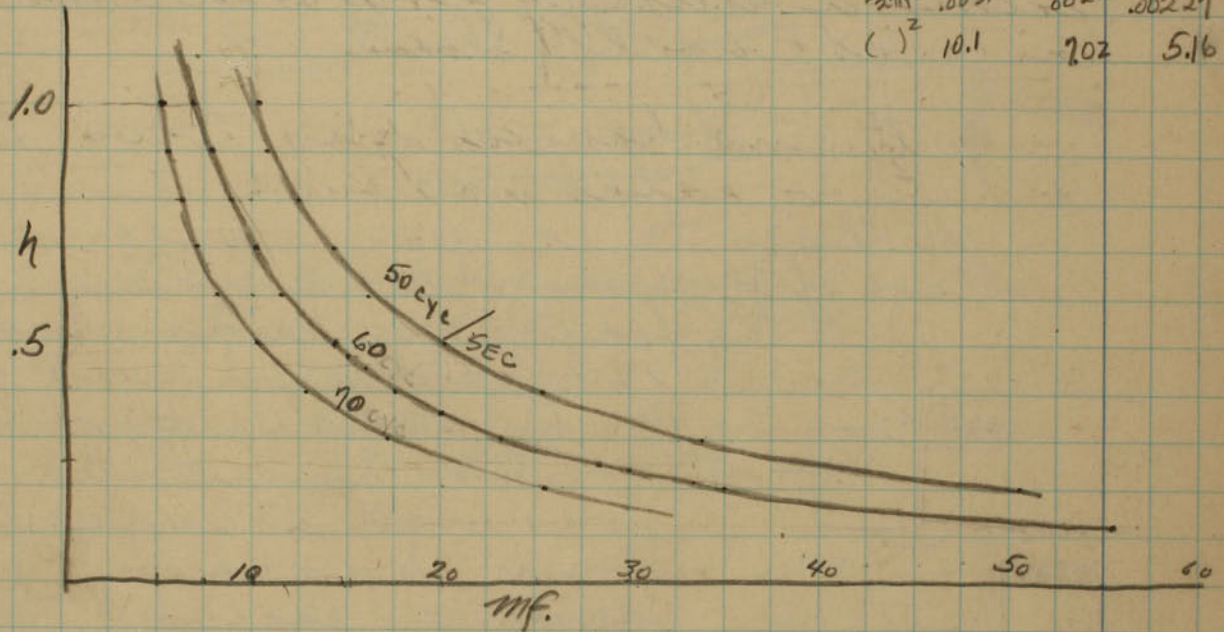


Edgerton
11-15-27

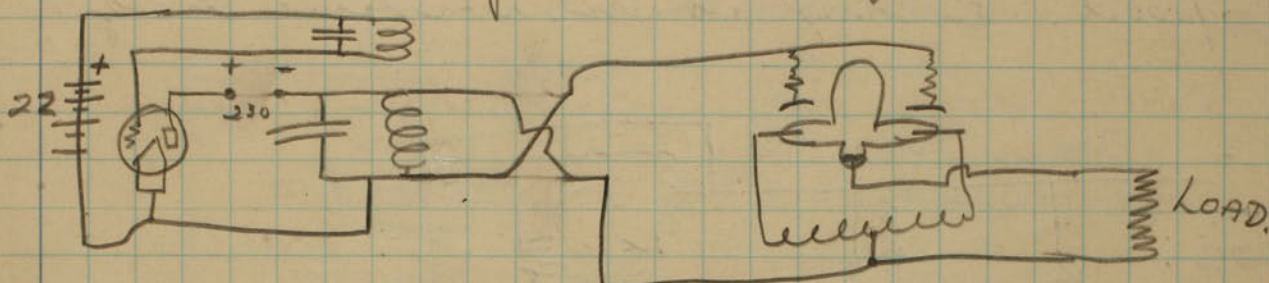A vacuum tube oscillator was connected up to oscillate at 120 cycles. Its output was connected across the grids in parallel.



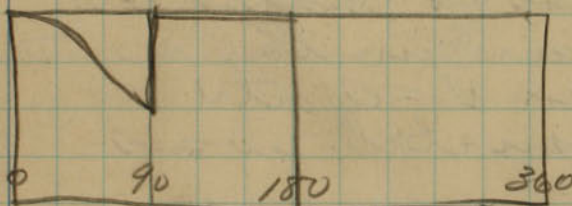This arrangement gave a variation of thyatron output with phase angle between the independently oscillating tube circuit and the alternator.




The variation is as sketched in the curve.

Notice that at 90° the full on occurs. This is because the 120° grid potential is positive because of the second wave coming in.

In order to connect back into the field circuit it was necessary to change the d-c lighting system to ac. in order to avoid a short circuit.

11-16-27
Edgerton

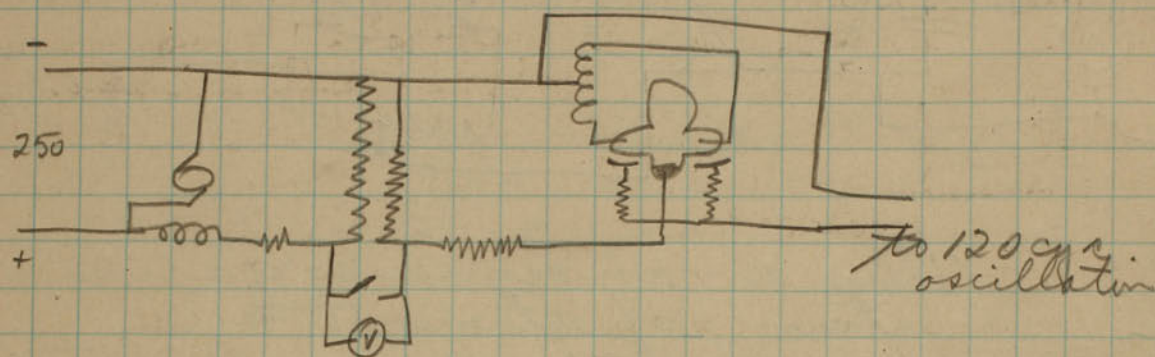The rectifier was connected so that it would feed back into the field circuit a correct amount of current to maintain constant speed. Below is the wiring diagram



The frequency of the m-g set was made to be 60 cycles. Then the tuned circuit was adjusted until the variations in the voltages were small. When $V=0$ the synchronising switch was closed.


If the m-g set speeds up the anode voltage leads (more) the grid voltage. The current from the thyatron decreases and the current in the field increases. This tends to reduce the speed.

The opposite effects are evident when the speed of the m-g set is reduced.

The outfit worked O.K. but came out of step too easily. The field must increase faster!

11-23-1927
Edgerton

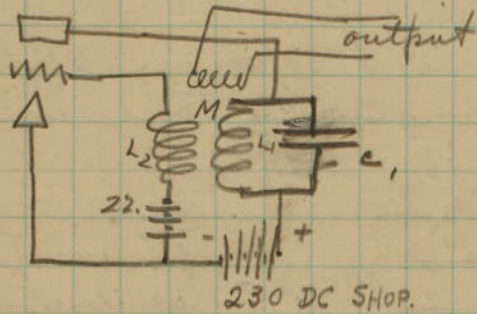Some difficulty was encountered in getting a 60 cycle tuned circuit to oscillate with a vacuum tube. The below gives the present hookup which works satisfactory at 60 cycles.




$$\frac{N_2}{N_1} = \frac{3}{1}$$

$C_1 =$ about mf.

$L_2 = ?$ $L_1 = ?$ Iron core trans.

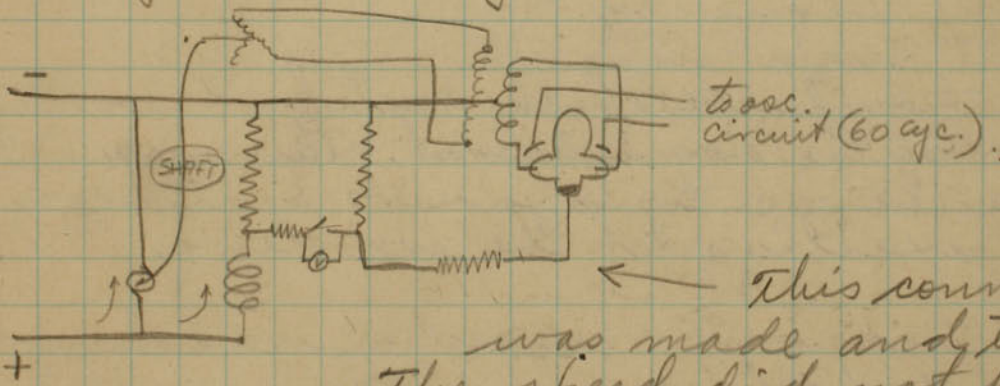The output was put on the grids of the thyatron tube. Then the m-g set was run so that the frequency was 60 cycles. Beats in the rectified dc voltage gave an indication of the exact frequency of the tuned circuit. By adjusting the inductance and capacity of the osc. circuit it was possible to bring the two systems into phase.



to osc. circuit (60 cyc.).

This connection was made and tried.

The speed did not hold constant but fluctuated a great deal, even when under no load conditions. Evidently the field current does not change fast enough.


Looking from the thyatron ^{side}, the circuit is a parallel one consisting of resistance and inductance. We wish the current to go through the inductance v.e. field circuit. To accomplish this an inductance will be put in the resistance circuit.

11-25-1927
Edgerton

Loads of different power factors (lagging) were tried on the thyatron circuit to determine the proper amount of inductance to use to smooth out the current wave.

12-9-1927

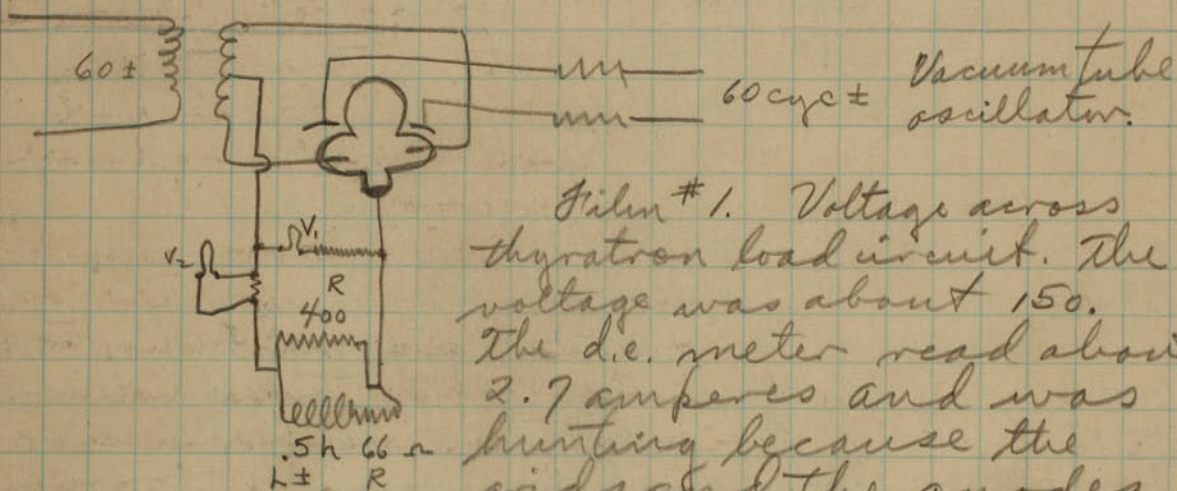A single element oscillograph was connected up to study the circuits




Film #1. Voltage across thyatron load circuit. The voltage was about 150. The d.c. meter read about 2.7 amperes and was hunting because the grids and the anodes were not at the same frequency.

The two halves of the rectified voltage were not of the same height. This was because the a.c. transformer's neutral did not exactly split the winding.

The transformer connection was changed so that each half wave would be similar.

Edgerton
12-13-1927.

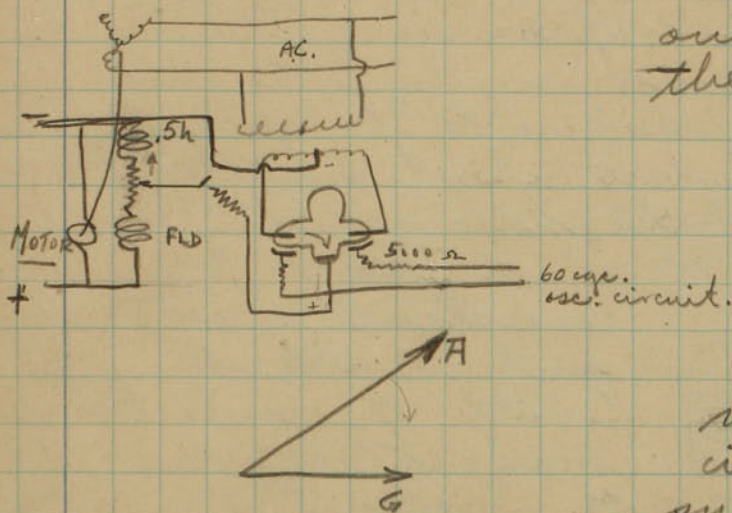The vacuum tube oscillating circuit was connected up and its output connected across the grids of the thyatron.



Many attempts were made to synchronize and hold the d-c. motor in step with the vacuum tube tuned circuit but none were successful.


The speed would hover around synchronous for a few seconds and then would start accumulative hunting and fall out of step, i.e. the rectifier would give full rectification and the motor would speed up.

Either the effect upon the field circuit is not fast enough or the tuned circuit is disturbed by the conduction from the grid.

Edgerton
Dec 17.

Today I returned to the scheme using the vertical cutoff portion of the characteristic as described on page 13.

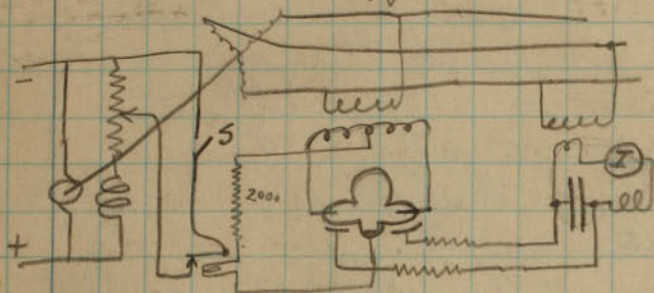Instead of coupling the rectified current directly to the field circuit, it was made to operate a relay which short circuited a portion of the field resistor.



A large resistance was put in series with the contactor magnet in order to make the circuit time constant as small as possible.

When this system was tried out it was noticed that the frequency had a variation of about .5 of a cycle. I opened the switch S and regulated the frequency by hand. When increasing the frequency the contactor did not close until the frequency was about .5 of a cycle above that, when it opened! I also noticed that the ammeter (A) changed its reading considerably when the main anodes of the thyatron were conducting. This shows that current flows in the grid circuit when current is flowing in the anode.

A 15 ma. d-c. ammeter was put in one of the grid leads. Its reading was erratic, sometimes one way and sometimes another.


The next step was to put more resistance in the grid leads. The resistance was increased from 5000 ohms to 65,000. This caused less interference with the tuned circuit but control was not positive at all times.

DEC 27-1927
EDGERTON

CHARACTERISTIC CURVES

OF VT-42.

ARC DROP.

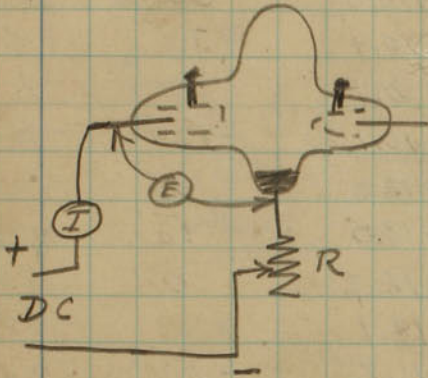


I
MA 128

E
MV 73


GRID OPEN
AFTER START.

6.0	21.	
8.3	20.5	
9.4	20.0	
11.6	19.8	(anode red hot).
4.0	21.4	
2.9	22.2	


goes out about 2.5 amps.

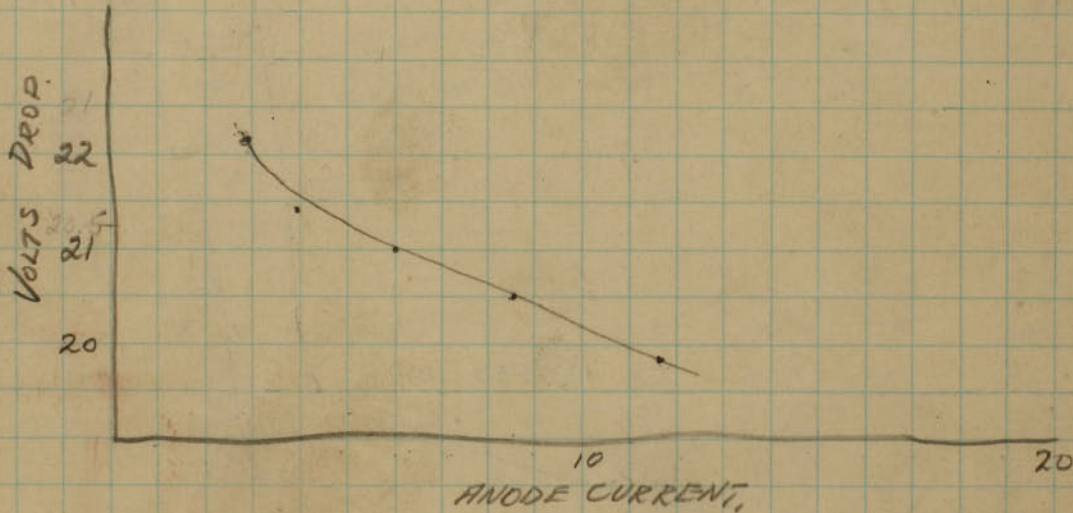


GRID-ANODE VOLT-AMPERE

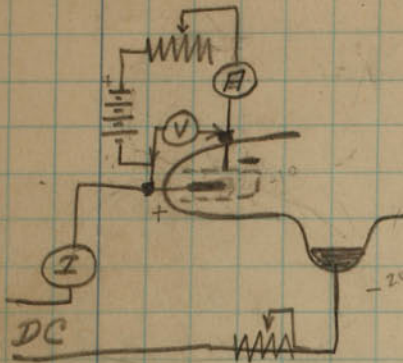

I_{ANODE} MA 128	I_{GRID} MA 137	V MV 73	8 AMP ANODE	
			I_G	V
5	0	-10.7		
"	+ 75 MA	-10.5	-330 MA.	-18.9
"	+ 180	-10.4	-318	-15.8
"	+ 355	-10.1	-250	-11.9
"	+ 480	-10.1	-124	-10.3
↓	- 50	-12.0	- 65	-10.0
	-100	-13.5	- 30	-10.0
	-168	-16.2	0	- 9.8
	-182	-19.1	+ 68	- 9.8
	- 30	11.8	+150	- 9.6
			+250	- 9.2
			+355	- 8.9
			+495	- 8.7

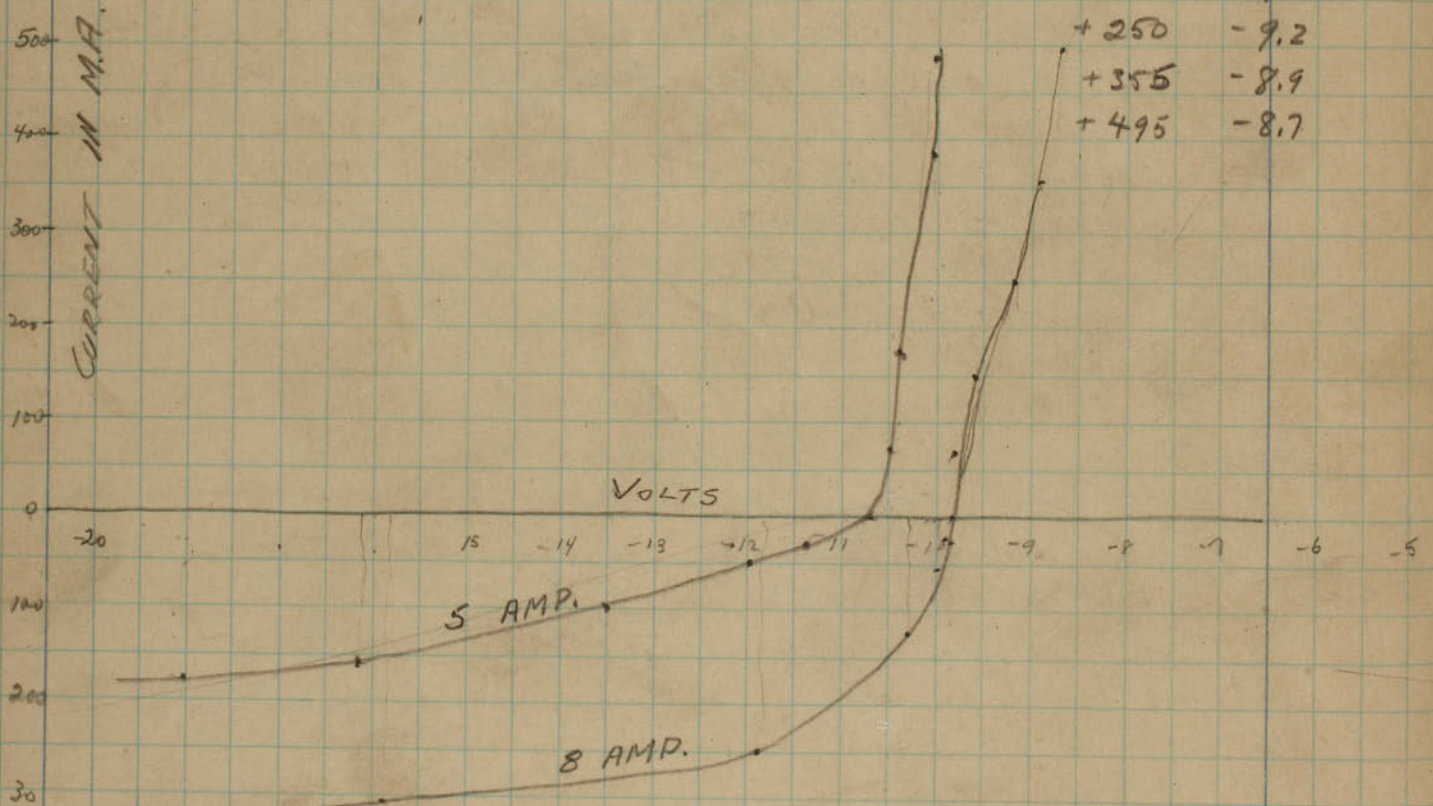

Dec 31, 1927
Edgerton & Church

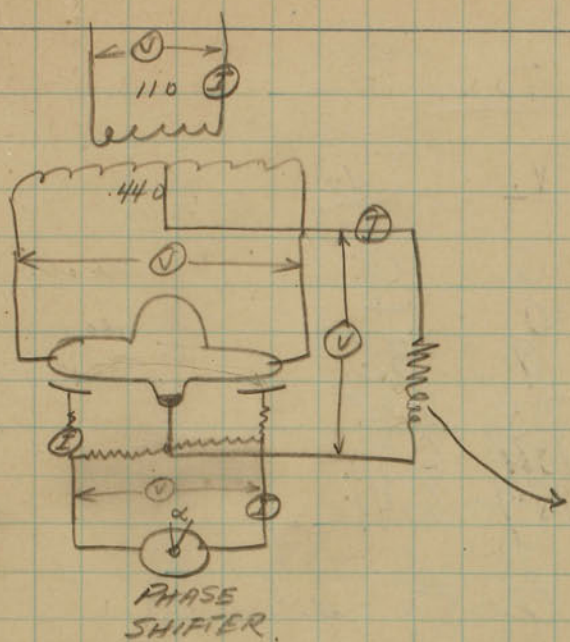

Keep alive excited
with dc. from
power supply.
110v 60 cycle obtained
from sine wave
m-g set.

E f I
116.5 60.9 .477


A.C.			GRID			D.C.			Notes
V_p	V_s	I_s	V	I_g	DEG	V	I_{ac}	I_{dc}	
446	446	0	220	0	51°	0	0	0	Grid tied with Resistances Inductive Load.
446	-?	-?	220	-	105°	4	-	- 2	
443	-?	-?	220	-	150°	33	.35	- ?	
438	-?	-?	220	-	195°	97	1.10	- ?	
436	1.22	-	220	-	240°	171	1.72	1.73	
436	1.25	-	220	-	270°	172	1.88	1.75	
446	0	0	220	0	48°	0	0	0	Grid Tied with Inductive Load.
447	-	-	220	-	105°	1	-	-	
443	-	-	220	-	150°	12	.49	-	
419	2.54	-	220	-	195°	92	3.75	-	
412	4.20	-	220	-	240°	155	6.30	-	
412	4.24	-	220	-	270°	157	6.40	-	
448	0	0	220	0	51°	0	-	-	Grid tied with Autotransformer Open Circuit Resistances
448	-	-	220	-	105°	16	-	-	
448	-	-	220	-	150°	78	-	-	
448	-	-	220	-	195°	148	-	-	
448	-	-	220	-	240°	178	-	-	
448	-	-	220	-	270°	175	-	-	
448	-	-	220	-	300°	160	-	-	
448	-	-	220	-	330°	135	-	-	

<u>A.C.</u>		<u>Grid</u>		<u>D.C.</u>	
<u>V_s</u>	<u>I_s</u>	<u>V</u>	<u>Deg</u>	<u>V</u>	<u>I_{dc}</u>
44.8	0	660?	85°	0	0
44.8	—	660	105°	0	—
44.8	—	660	150°	9	.35
42.7	2.0	660	195°	73	2.95
41.4	4.18	660	240°	154	6.30
41.4	4.27	660	270°	157	6.41


Inductive Load
Increased Grid
Voltage!

Oscillographic tests show that
angle reading on phase shifter
is not correct.

Feb 17 1930
S. E. Edgerly

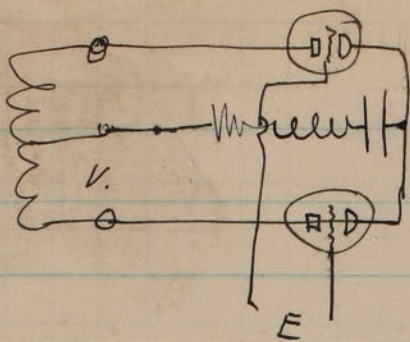

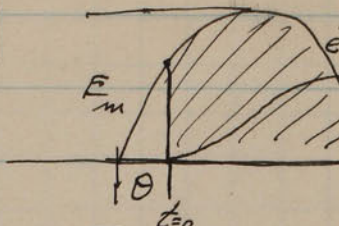Assume no voltage drop in rectifier for first approx. that is the voltage across the load is large with respect to that across the rectifier.



$$L \frac{di'}{dt} + Ri' + \frac{1}{C} \int i' dt = E_m \sin(\omega t - \theta) \quad 1$$

$$CL \frac{di'}{dt} + CRi' + \int i' dt = CE_m \sin(\omega t - \theta) \quad 1$$

This voltage continues to act until the current becomes zero or the other anode takes the current.

Let $t = a\lambda$ $dt = a d\lambda$

$$\frac{CL}{a} \frac{di'}{d\lambda} + RCi' + \int i' d\lambda = CE_m \sin(\omega a\lambda - \theta) \quad 1$$

multiply by $\frac{1}{a}$

$$\frac{CL}{a^2} \frac{di'}{d\lambda} + \frac{RC}{a} i' + \int i' d\lambda = \frac{C}{a} E_m \sin(\omega a\lambda - \theta) \quad 1$$

Let $\frac{LC}{a^2} = 1$ or $a = \sqrt{LC}$

then $\frac{di'}{d\lambda} + R\sqrt{\frac{C}{L}} i' + \int i' d\lambda = E_m \sqrt{\frac{C}{L}} \sin(\sqrt{LC}\omega\lambda - \theta) \quad 1$

let $R\sqrt{\frac{C}{L}} = k$

$$\frac{di'}{d\lambda} + k i' + \int i' d\lambda = E_m \sqrt{\frac{C}{L}} \sin(\sqrt{LC}\omega\lambda - \theta) \quad 1$$

$p = \frac{d}{d\lambda}$

$$p i' + k i' + \frac{i'}{p} = A \sin(\omega_0 \lambda - \theta) \quad 1$$

$$A = E_m \sqrt{\frac{C}{L}}$$

$$\omega_0 = \sqrt{LC} \omega$$

$$\frac{i'}{p} (p^2 + kp + 1) = A \sin(\omega_0 \lambda - \theta) \quad 1$$

or in the charge form since $i = \frac{dq}{dt} = \frac{1}{a} \frac{dq}{d\lambda} = p q$

$$\frac{p^2 q}{a^2} + \frac{kpq}{a} + \frac{q}{a} = A \sin(\omega_0 \lambda - \theta) \quad 1$$

$$p^2 q + kpq + q = \sqrt{LC} A \sin(\omega_0 \lambda - \theta) \quad 1$$

Regulation - Angle Characteristics of a Thyatron with Inductive load

April 5/1930

J. E. Edgerton


A thyatron which is grid controlled (angle) and feeds into a pure resistance circuit always has its load current and load voltage in exact proportion. This problem is treated in a research report that Mr. E. A. Church and the writer prepared in Dec. and Jan. 1928.

Inductance in the load circuit of a grid controlled thyatron gives a different curve of regulation voltage against angle (between the anode voltage and that of the grid). When the grid goes positive the current in the anode circuit starts. The inductance allows a certain rate of increase and the transient gives the same current as a sine wave of impressed e.m.f. impressed on a RL circuit (neglecting the non-linear rectifier circuit).


With a pure resistance load the current stops at the same time that the anode voltage does. However with inductance the current continues to flow and maintains the arc. Across the load, during the time the arc is maintained, the impressed e.m.f. from the circuit is negative. This cancels out ~~the~~ some of the positive voltage. Thus the regulated voltage - angle voltage curve will be steeper than with the resistance case. This can be seen on the preceding page on the diagram of instantaneous current and voltages.

L-R Circuits
V-Angle Curves.

Apr 5 1930
A. E. Edgerton

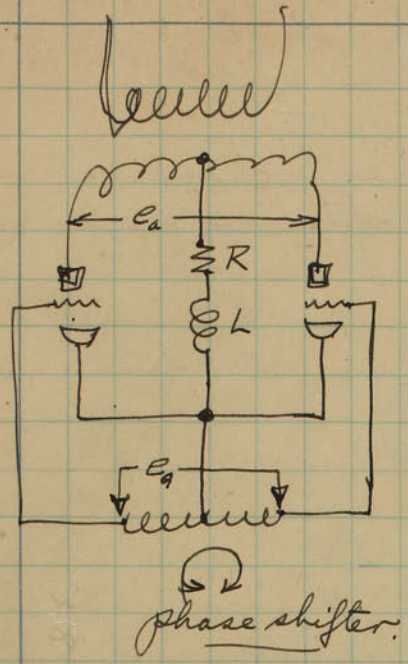


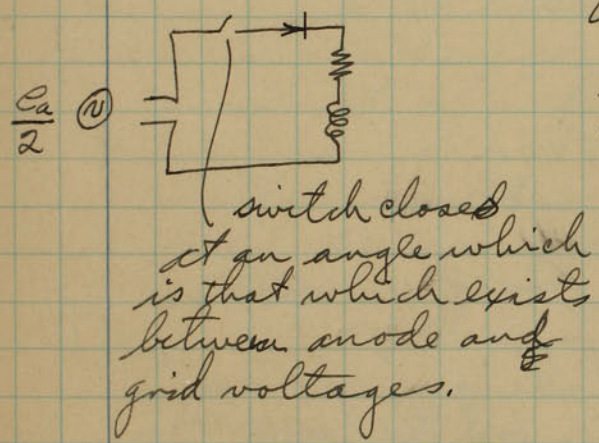We will consider first the case where the inductance is small enough to not maintain the current ~~at~~ continuously. That is, the current in the load circuit will be of pulses. This case is somewhat simpler since the initial boundary conditions are known when an anode starts to conduct.



The electrical circuit to be considered is then as shown in the sketch to the left. The switch closes when the grid voltage becomes zero (or slightly positive). The rectifier characteristic limits the current flow to one direction as shown by the arrow. The switch opens at the instant that

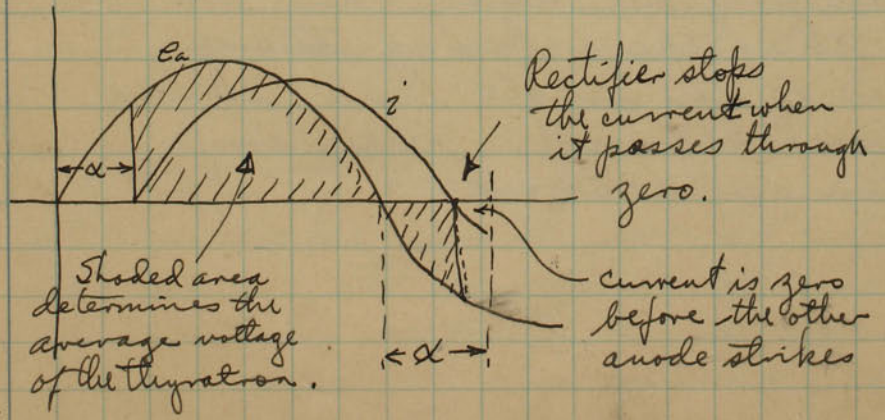
the current is zero and this represents the regain of control by the grid in the thyatron. A d.c. voltmeter across the L-R circuit will read the average voltage across these circuit elements.



Stroboscope.

Apr 5 1930
A. E. Edgerton

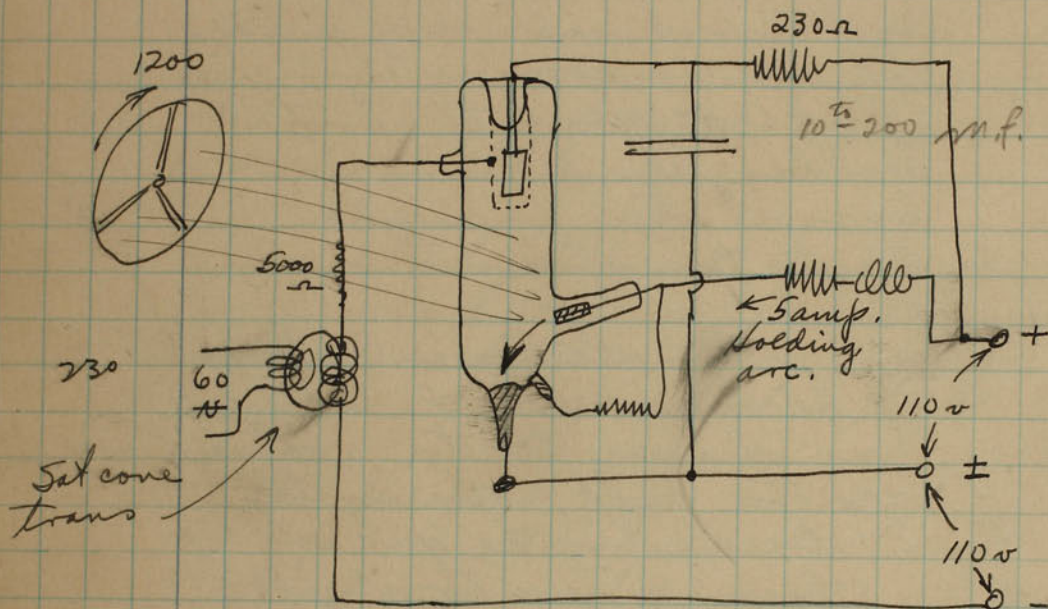A thyratron tube of special design given me by Dr. Elder of the Research Lab of the G. E. Co. The following circuit was used to get stroboscopic light from the tube.



The grid is normally biased 110 volts by minus shop. The transformer which is shown on the left is of special design. The magnetic path for the secondary is highly saturated so that the induced e.m.f. is very peaked.

This stroboscope was used to observe a thin white line on a black disc. The distinction was very good. The machine driving the disc ran at 1200 r.p.m. thus there being ~~three~~ three images of the single line, spaced 120 mechanical degrees. The lamp flashes 60 times a second.

Frequency Limitation of the Mercury Stroboscope

Apr 11 1930
H. E. Edgerton
Hall.

A General Radio oscillator was used to regulate the freq. Mr. Hall fixed up this circuit. It fed into the grid circuit same as the experiments of Apr 5, except the neg. bias of the grid was varied to fit the needs of the oscillator. With 110 volts on the condenser freq. up to 1200 were reached with fair definition of the line. This line was a radial white strip (about 1/8") on a 12" black disc. The disc rotated at 1200 r.p.m.

In the afternoon we put 220 volts on the condenser and varied the amount of capacity. For the high frequencies the constants of the condenser circuit were not fast enough for stroboscopic action.

With a high voltage on the condenser more energy can be stored in the condenser and discharged more quickly (due to ~~low~~ small capacity for equal light). However the resistance that blocks the circuit must be larger and thus the time constant of the circuit that charges the condenser is slower.

We showed I believe that this tube would give satisfactory stroboscopic action from 20 cyc/sec. to 700 ± cyc/sec.

A large Western Electric cone was excited with 150 volts 60 cyc ac. and the stroboscope was run at about 59 or 61 cycles. The surface of the cone could be seen to warp and oscillate at a slow speed. We could see the vibration patterns of the surface. Prof Boules saw this and was interested.

For some tests 300 m.f. were used.

55 M.f. = $\sqrt{55} \times 10 \text{ farads}$

$\frac{1000}{220 \times 2\pi \times 60}$

$C =$

$\frac{1}{2\pi \times 60 \times C}$

$\frac{1}{2\pi \times 60 \times C}$

$\frac{1}{2\pi \times 60 \times C}$

$\frac{1}{2\pi \times 60 \times C}$

$\frac{1}{2\pi \times 60 \times C}$

$\frac{1}{2\pi \times 60 \times C}$

1 KVA at 300 m.f. 60 Hz

Stroboscope -

April 21 1930
J. E. Elgerton

Previous works to date (Apr. 21, 1930) which I have on loose sheets were today glued into this book on the following pages 33 to 38.


The circuit on page 35 was used successfully as an open-house display in the spring of 1929. Mr. Robert V. Kleinschmidt and Mr. Ben B. Folger of Arthur D. Little, Inc. came over and demonstrated the setup to them the week after open-house. They were interested in a slow speed stroboscope. I gave them a price which was high because of the difficulties I expected in the construction and test of the device.

The main disadvantage of the circuits on pages 34, 35, 37 is the fact that a contact on a rotating device must carry the entire current which gives the light. The first contact that touches gets a heavy surge of current which causes arcing with the metal by burning. Part of this trouble can be eliminated by inserting a small amount of inductance which cuts off the rapid rise of current. It also tends to make the current oscillatory.

The circuits of pages 33 and 36 are better since the transient is tripped by the switching circuit. Page 33 circuit does not have a holding arc. The high potential from the spark coil magnet is transferred by being connected to a tin foil around the cathode outside the glass. A surge of current discharges the condenser and the resistance to the line keeps it from building up, maintaining the spark.

Cambridge Mass.
May 28, 1929.

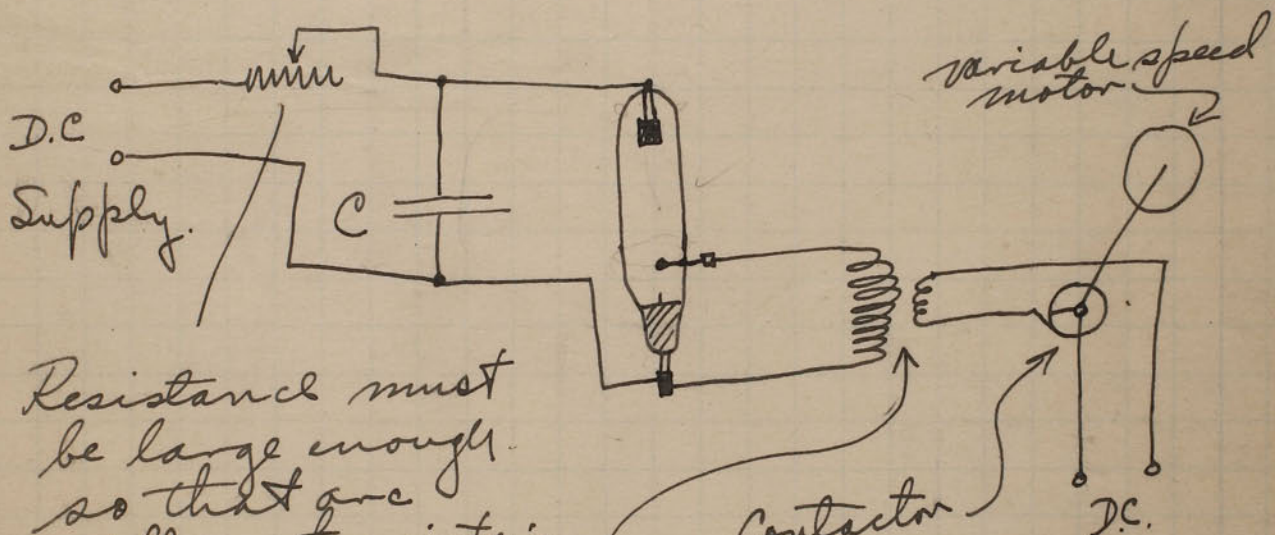Method of operating a
mercury arc tube as a
Red Stroboscope.



Resistance must
be large enough
so that arc
will not maintain
itself.

Spark coil giving high
voltage to break down
tube and start arc.


This circuit was shown to me by
H. E. Edgerton on May 28, 1929.

Charles Kingsley Jr.
Cambridge, Mass.

STROBOSCOPE

This describes an idea for the utilizing of an ionized mercury vapor tube as a means of obtaining stroboscope action.

A current of sufficient magnitude to give enough light is sent through the mercury tube at definite periods of time. This is accomplished by having a variable speed motor drive a metallic disc. This disc has a small insulating segment on its rim. A narrow brush ~~also~~ makes contact with the rim of the disc. When the insulated sector and the brush are together the current that normally passes from brush to disc is shunted into the mercury tube.

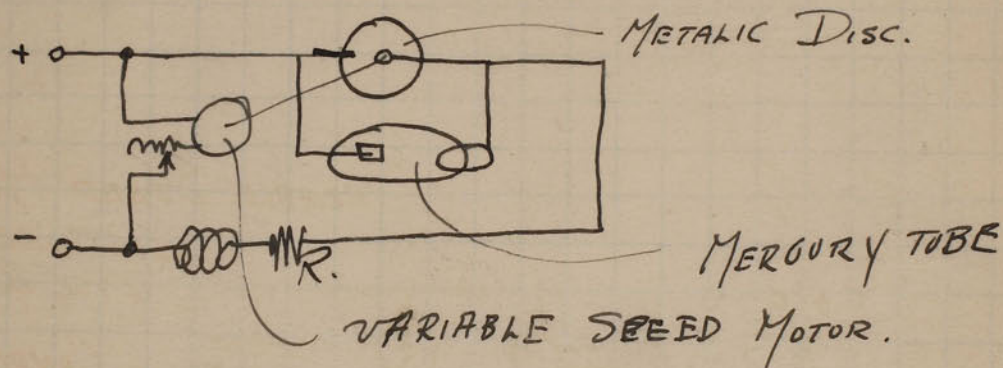


Witnessed in operation, May 16, 1929

Thomas S. Gray
Cambridge, Mass

MERCURY STROBOSCOPE.

A stroboscope using a mercury vapor tube is described herein. The light from such a device is much more susceptible to photography than other types of stroboscopes using neon lamps.

The method of obtaining stroboscopic action is to discharge a condenser through the ionized mercury vapor at periodic times. A small variable speed motor driving an insulated disc with one small contact and brush furnish the interrupting of the circuit at definite intervals of time. A resistance is put between the condenser and the source of constant potential that is used for a supply. This limits the current taken by the condenser during the time that it is being charged.

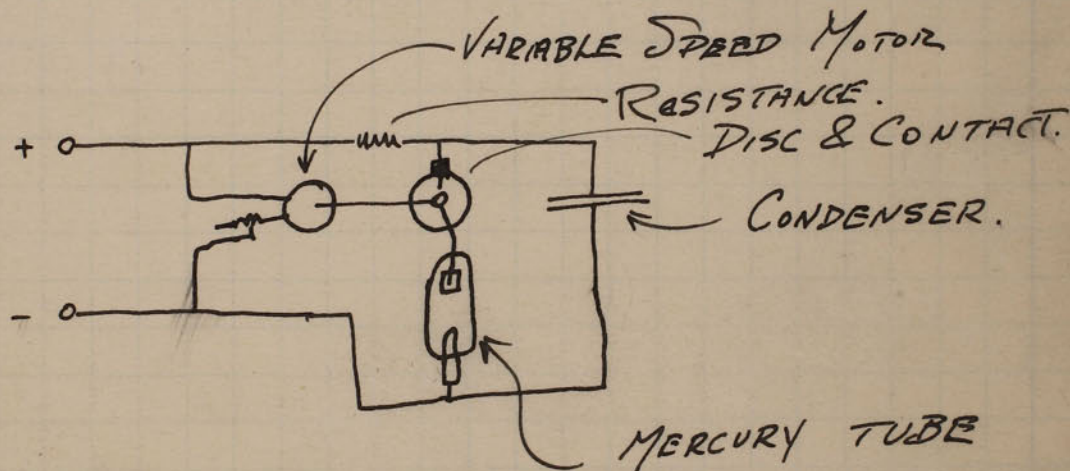

The source of d-c. voltage must be 220 volts or more in order to have the discharge fast and strong enough.

Witnessed in operation, May 16, 1929



*Thomas S. Gray
Cambridge, Mass.*

United States Patent Office
 Before the Examiner of Interferences
 Trucksess v. Edgerton - Int. 73,473

Edgerton Exhibit 8
 Page 36 of notebook TI.

Feb. 27, 1937



Clara Schlosky
 Notary Public

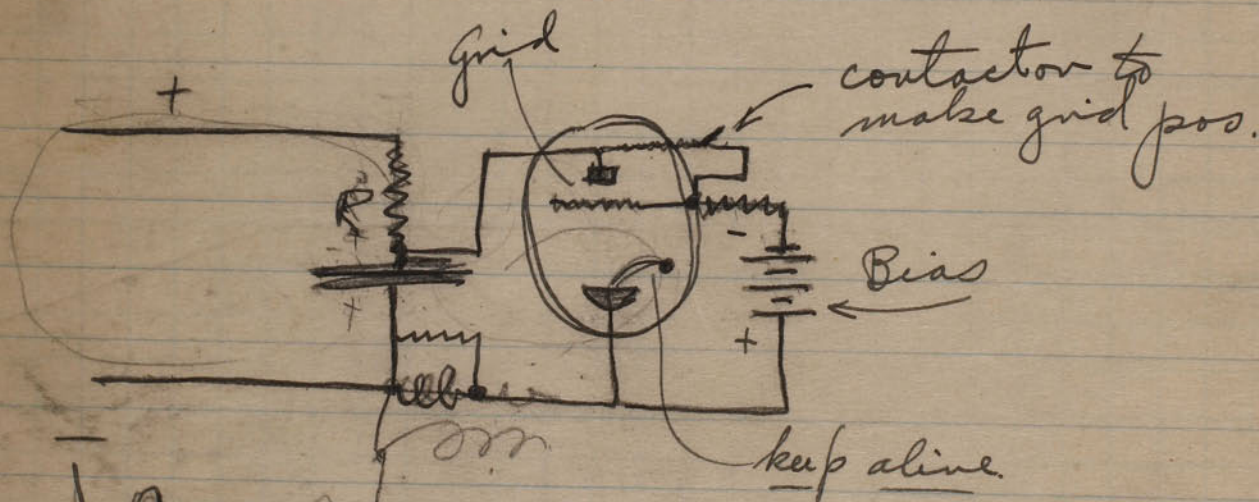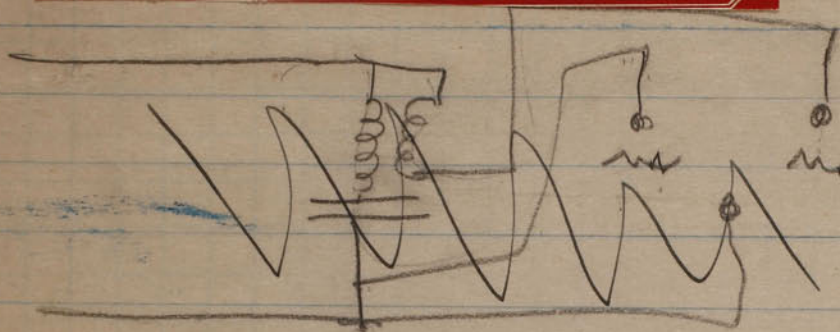


This circuit was shown
 to me by H. E. Edgerton
 on May 28, 1929

Charles Kingsley Jr.
 Cambridge, Mass.

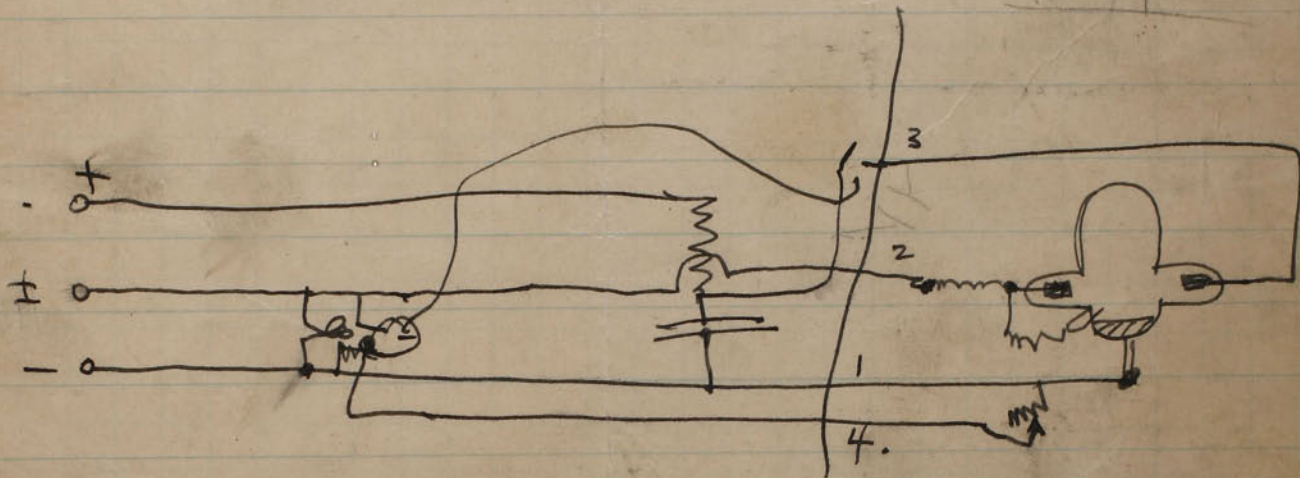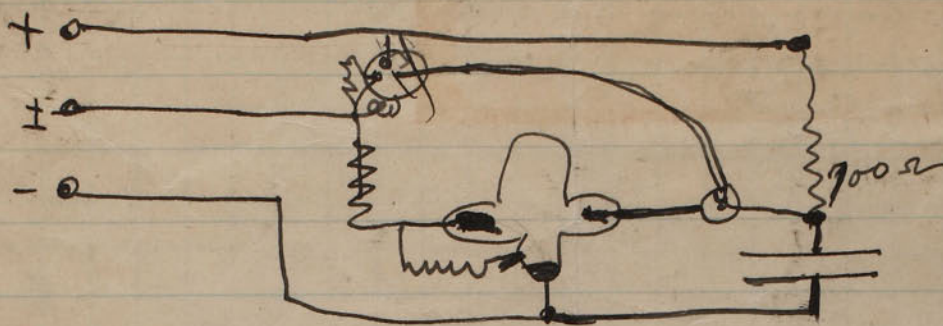This circuit was used for an open-house demonstration in 1929.





Current

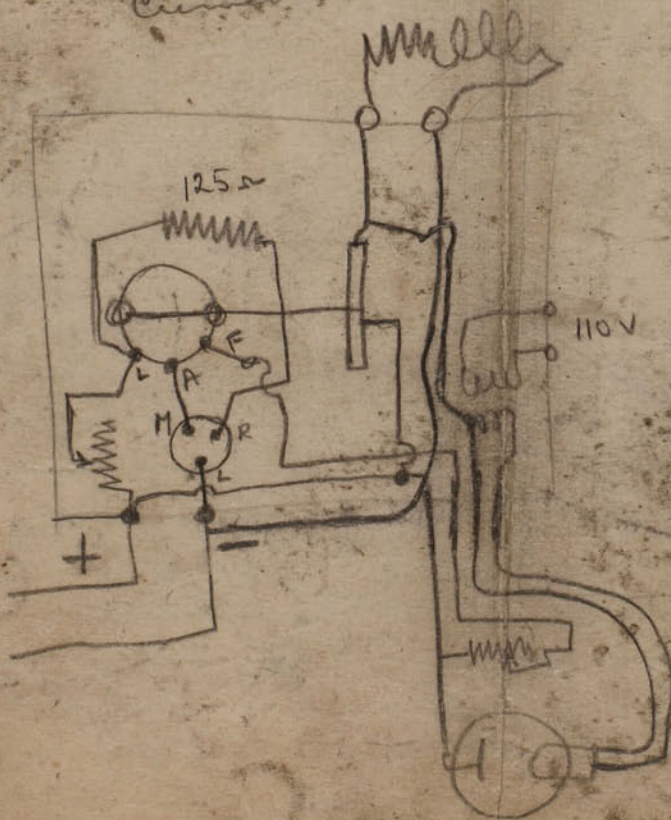


Condenser



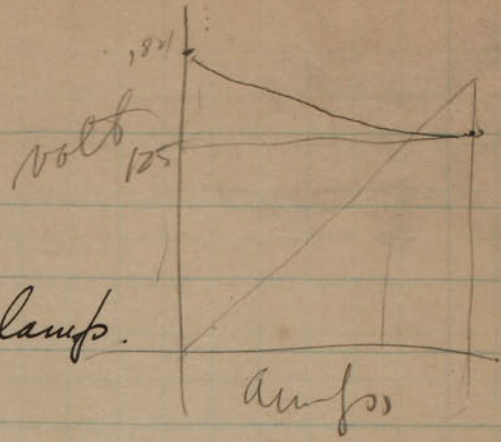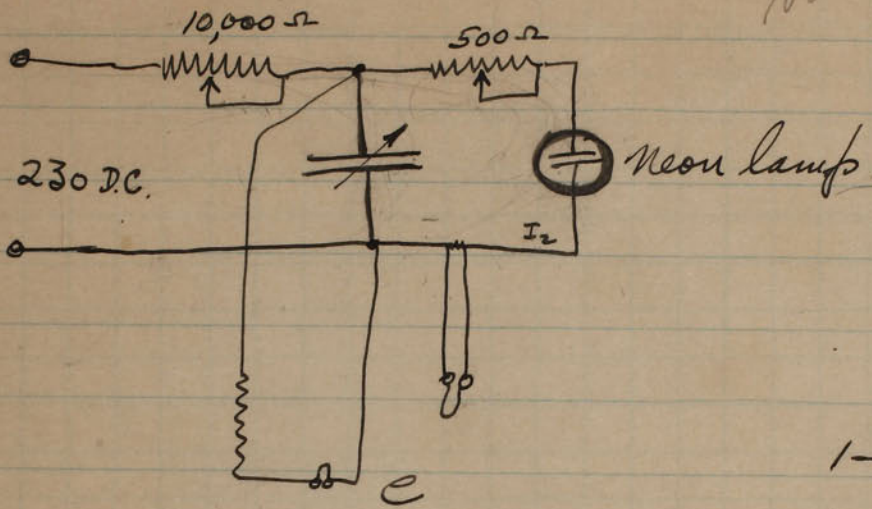Thirring diagram for an experimental hot cathode ~~ball~~ stroboscope for an open-house display. This was not used due to the darkening of the bulb.




1-10,000 ohm.
 1-500 ohm.
 condenser.

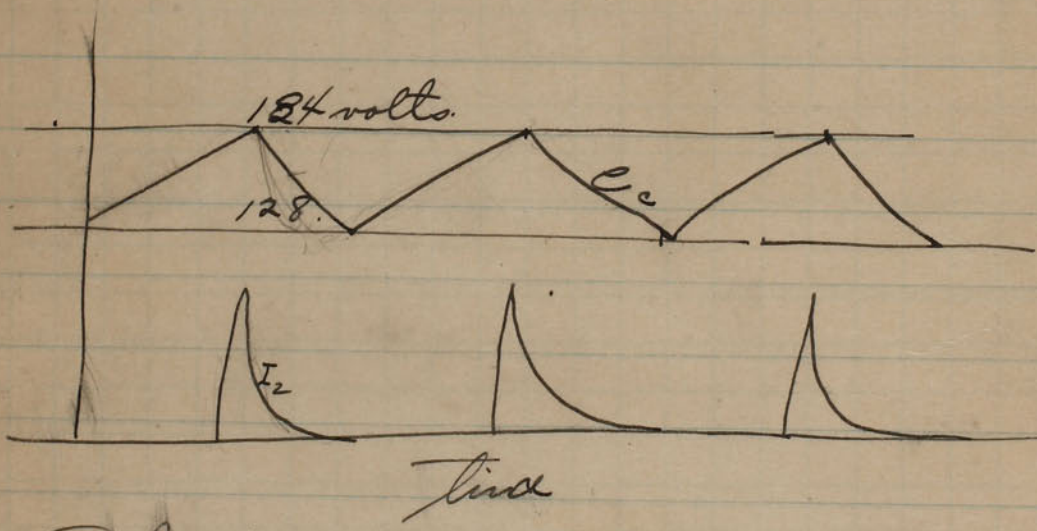


10 watts.
 $\frac{10^0}{150} = .066 \text{ mils}$
66 mils

Reducing R_2
 184


60 cycle.

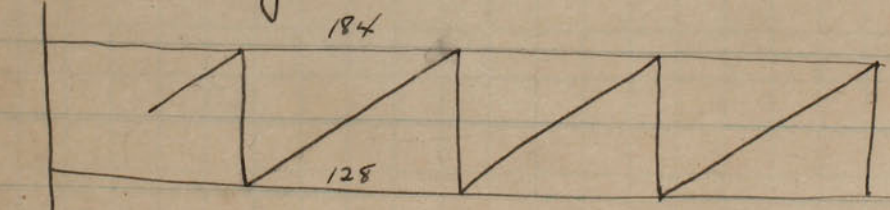
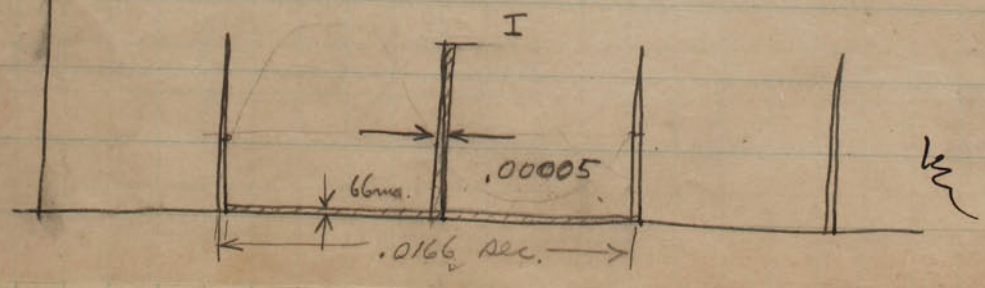
$$I = \frac{.066 \times .0166}{.0005000} = 21.8 \text{ amps.}$$



A-C operated Stroboscope

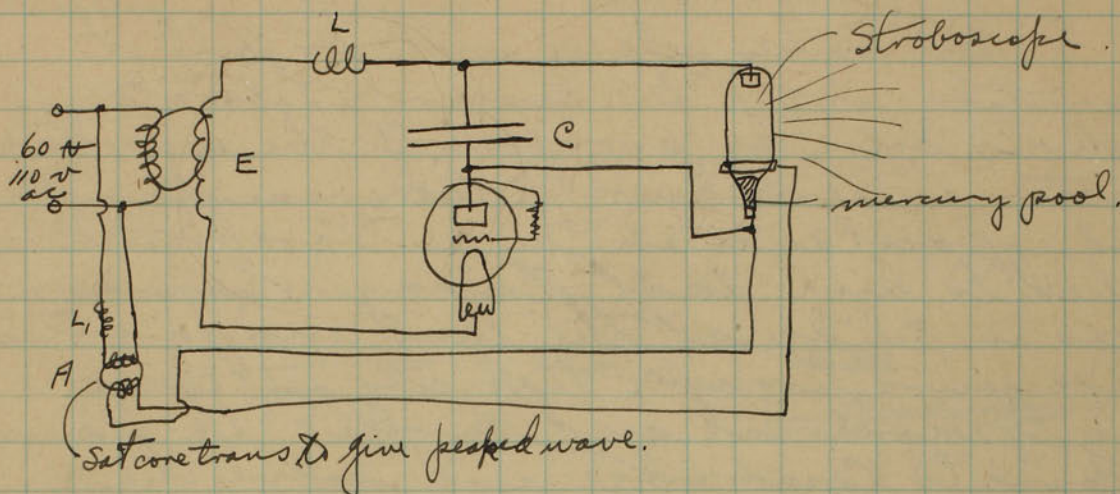April 21 1930
A. E. Edgerton


The transient through L C and the rectifier should last about $1/8$ or $1/4$ of a cycle. It should not overload the hot cathode of the rectifier and should allow the stroboscope to go out after the surge.

The transformer A should give high enough voltage to break down the ~~st~~ stroboscope and start the cathode spot.

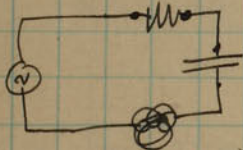H. E. Edgerton
May 26/1930

A-C on circuit of RC and iron-core reactor

Dr. Suikes who is with Dr. Hull at Schenectady in the E. E. Research Laboratory wished to solve the problem of the iron-core reactor in series with the resistance and capacitance on the integrator. I talked to him last Friday when I was in Schenectady at the time my parents were going through that city on their way to Montreal and Europe. He plans to come to Cambridge and solve the problem if it is possible. I sent him the pamphlets which describe the machine and the type of problems that it handles, today.



Steady state.


$$E \sin \omega t = Ri + \frac{1}{C} \int i' dt + N \frac{d\phi}{dt}$$

Between ϕ and i there is a single valued functional relation given by the magnetization curve of the material composing the core of the coil.

$$\frac{d\phi}{dt} = \frac{d\phi}{di} \cdot \frac{di}{dt}$$

which gives
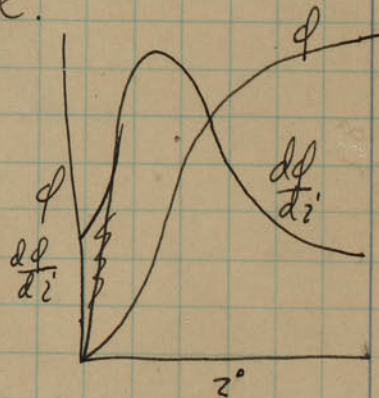
$$E \sin \omega t = Ri + \frac{1}{C} \int i' dt + \left[N \frac{d\phi}{di} \right] \frac{di}{dt}$$




note that $\frac{d\phi}{di}$ is a variable with i . It has a numerical value for each value of current and changes as the current changes. It is a variable coefficient.

Rewriting
$$\left[N \frac{d\phi}{di} \right] \frac{di}{dt} = E \sin \omega t - Ri - \frac{1}{C} \int_0^t i dt$$

Integrating both sides with time after separating.
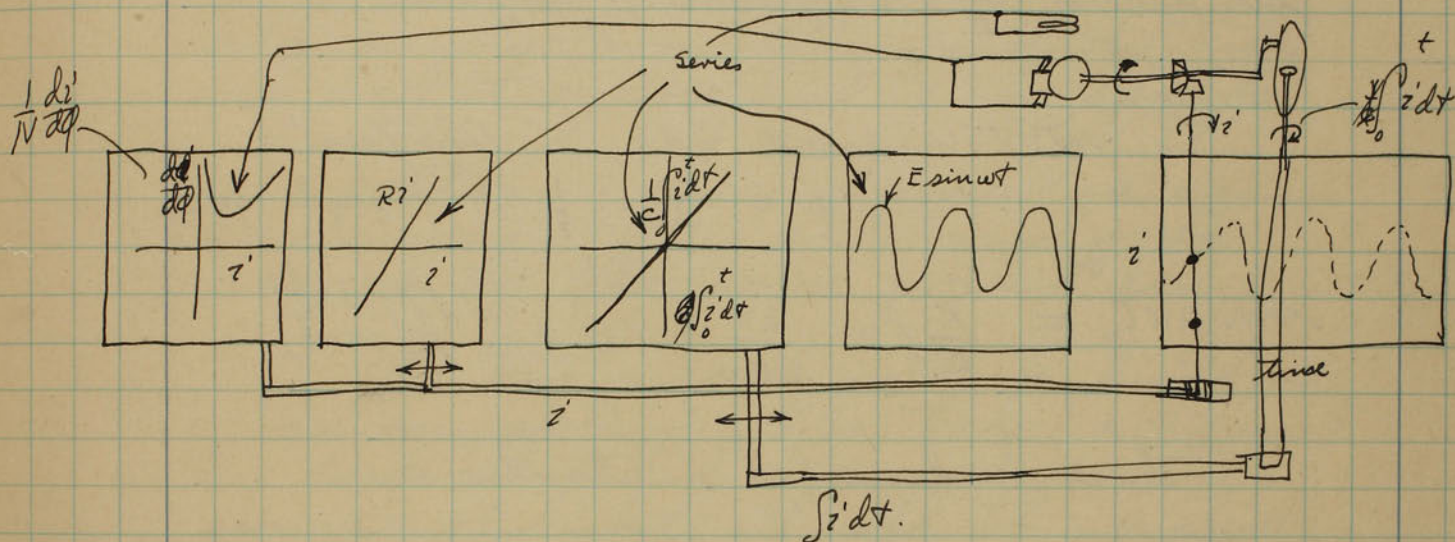
$$\int_0^t \frac{di}{dt} = i = \int_0^t \frac{1}{N \frac{d\phi}{di}} \left[E \sin \omega t - Ri - \frac{1}{C} \int_0^t i dt \right] dt.$$



Since $\frac{1}{N \frac{d\phi}{di}}$ is not a function of time it may be either in or out of the integral sign. no!

If a standard magnetization curve may be used it is possible to reduce the number of constants and so make the solutions apply to any problem. List of constants:

R	C	N	E	ω	$\phi-i$ function
1	2	3	4	5	6

Six ~~are~~ constants which take different values with different problems.

Let τ = a new variable which will be equal to time ^{divided} multiplied by some unknown constant "a".

$$\tau = a t$$

$$t = a \tau$$

$$\sin \omega t = \frac{R}{E} i' + \frac{1}{CE} \int_0^t i' dt + \left[\frac{N}{E} \frac{d\phi}{di'} \right] \frac{di'}{dt}$$

changing variables $t = az$
 $dt = a dz$

$$\frac{d}{dt} = \frac{1}{a} \frac{d}{dz}$$

$$\int_0^t dt = \int_0^{az} a dz =$$

$$\sin a\omega t = \frac{R}{E} i' + \frac{a}{CE} \int_0^{az} i' dz + \left[\frac{N}{E} \frac{d\phi}{di'} \right] a \frac{di'}{dz}$$

Let $a\omega = 2\pi$ 1 cyc./sec.
 $a = \frac{2\pi}{\omega} = \frac{1}{f}$ $f = \text{freq in cyc./sec.}$

$$\sin 2\pi t = \frac{R}{E} i' + \frac{2\pi}{CE\omega} \int_0^{\frac{2\pi}{\omega} z} i' dz + \left[\frac{N}{E} \frac{d\phi}{di'} \right] \frac{\omega}{2\pi} \frac{di'}{dz}$$

three fundamental constants,

Let $\underline{\underline{A}} = \frac{R}{E}$

$\underline{\underline{B}} = \frac{2\pi}{CE\omega} = \frac{1}{CEf}$ since $\rightarrow \omega = 2\pi f$

$\underline{\underline{C}} = \frac{Nf}{E} \frac{d\phi}{di'} = \text{a function of } i'$


Stroboscope for Dyn. Lab.

May 27 1930
H. S. Edgerton

Mr. L. D. Bardsley who has been developing a mercury arc stroboscope for use in the dynamo laboratory found trouble with flickering.

We tried to eliminate this with a wire wound around the tube and had it connected to the spark coil. Later it was connected to +250 volts and also connected again to the anode. This external grid reduced the flicker a great deal.

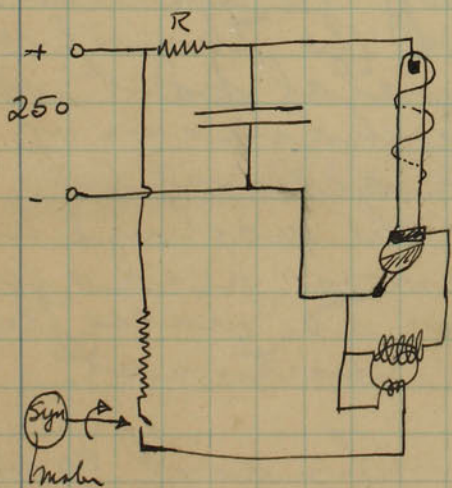The stroboscope is to be built in a box on casters. The tube, a 22 inch ac Cooper Hewitt lamp will be the source of light. It will be ignited or started with a spark coil which is interrupted with a spark coil an automobile distributor driven by a synchronous motor.



Cooper Hewitt tube.

A two way switch is to be on the unit. One way gives the tube the regular ac connection in order to warm it up. The other switches on the synchronous motor contact maker and gives 60 cycles stroboscopic action.

Sept 16 1930

Stroboscope.


H. E. Edgerton.

I constructed a strobe
 be used for observation
 electrical angle of disc
 of the generators of the 15th
 development of the New England
 Company, located near
 and East ~~Ham~~ Barnet Vt.
 Previously I had got
 a 3.5. single phase tube
 and measured the angle of a
 5 kw induction machine Mr.
 Spencer brought Mr. L. Thurston
 (movie camera man) over and he
 took some shots with a 1.9 lens
 and 12 frames a second. He said that
 the light was sufficient for photographic
 purposes. (Panchromatic
 used.)



1 SEC. F. 4.5.

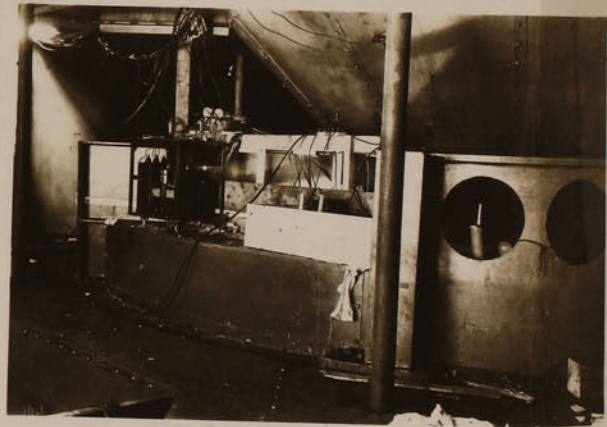On Thursday the 4th
 went to the 15 mile falls
 was constructed so that
 rotor of #2 generator
 Upon this was mounted
 Below it was a sheet
 was part of the fan in
 the rotor. Upon this were accurately
 located 52 white lines
 52 poles) adhesive tape
 stuck to the lines in order
 photographs have more



The windage was too
 with a cold spell and
 conditions for the thyro
 circuit that I was
 transformer could not
 voltage to trip the circuit. After
 some I got a 110-440 volt transformer and
 put



Sept 16 1930

Stroboscope.

H. E. Elynton.

I constructed a stroboscope to be used for observation of the electrical angle of displacement of the generators of the 15 mile falls development of the New England Power Company, located near St Johnsbury and East ~~Werra~~ Barnet Vermont.

Previously I had connected up a 3.5. single phase tube in the lab and measured the angle of a 5 kw induction machine Mr. Spencer brought Mr. L. Thurston (movie camera man) over and he took some shots with a 1.9 lens and 12 frames a second. He said that the light was sufficient for photographic purposes. (Panchromatic film was used.)

On Thursday the 4th of Sept I went to the 15 mile falls plant. A platform was constructed so that it cleared the rotor of #2 generator by $\frac{1}{2}$ an inch. Upon this was mounted the thyatron. Below it was a sheet metal part which was part of the fan mechanism of the rotor. Upon this were accurately located 52 white lines (the machine has 52 poles) adhesive tape arrows heads were stuck to the lines in order to make the photographs have more contrast.

The windage was terrific and combined with a cold spell made adverse operating conditions for the thyatron with the circuit that I was using. The grid transformer could not supply enough voltage to trip the circuit. After experimenting some I got a 110-440 volt transformer and


found that it gave much better operation.
I returned to Boston on the 8th of sept.

On the 12 Spencer again called and wished me to bring up the oscillograph and an assistant to watch the stroboscope. Mr. Sullivan went with me.

I took a 1000 volt plate ~~by~~ transformer which had a mid tap. Thus I could use both tubes in opposition. 15000 ohms was put in the grid circuits where I used 5000 before. This was increased because the 5000 ohm resistors could not stand the current.

Circuit for

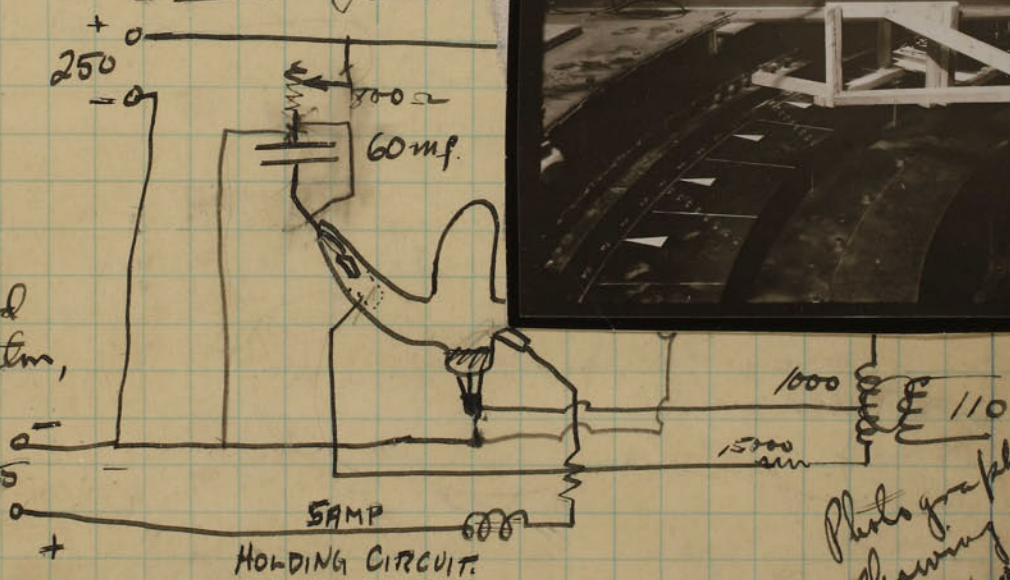This circuit worked very satisfactorily. Was seen by Oliver, Dillard, Spencer, Thurston, Fisk Sullivan, Patterson, Coe, Bancroft, Treat, Lee and others.



Photograph showing arrows on the poles and frame work supporting thyatron.

If the grid impedance is put in the neutral leg the operation of the grid transformer will be somewhat different. It might be some advantage to use two grid transformers and a neutral resistance to get favorable action.

Moving picture of system disturbances were taken. I returned to Boston with Sullivan on Sept 16, 1930. today had a great time.




found that it gave much better operation.
I returned to Boston on the 8th of sept.

On the 12 Spencer again called and
wished me to bring up the oscillograph
and an assistant to watch the stroboscope.
Mr. Sullivan went with me.

I took a 1000 volt plate ~~by~~ transformer
which had a mid tap. Thus I could use
both tubes in opposition. 15000 ohms was
put in the grid circuits where I used
5000 before. This was increased because
the 5000 ohm resistors could not
stand the current.

Circuit for stroboscope

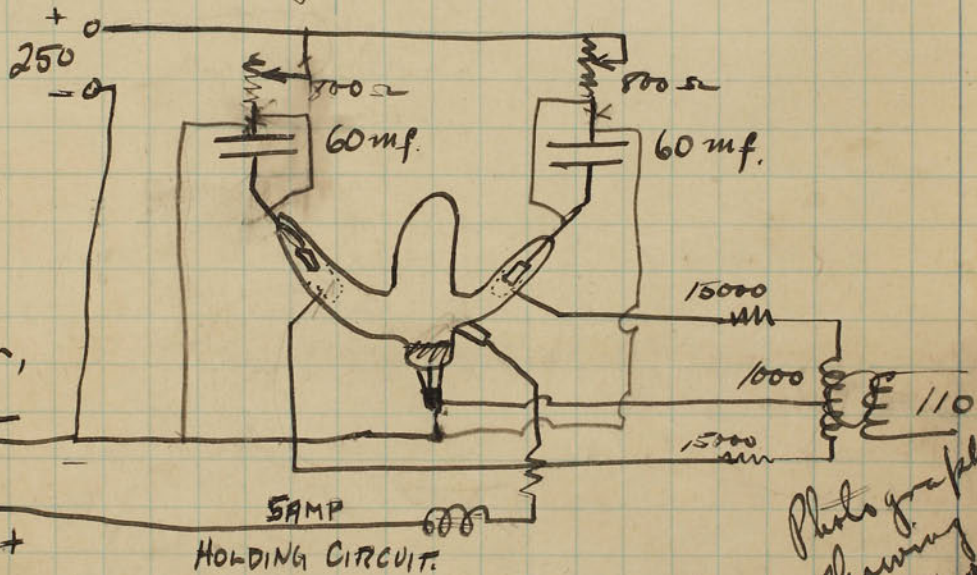This circuit
worked very
satisfactorily.
Was seen by
Oliver, Dillard
Spencer, Thurston,
Fisk Sullivan
Patterson, Coe,
Banckler, Treat,
Lee and others.



Photographed
showing amount on
the poles and
framework supporting
thyatron

If the grid impedance is put in
the neutral leg the operation of the
grid transformer will be somewhat
different. It might be some advantage
to use two grid transformers
and a neutral resistance to get
favorable action.


Moving picture of system disturbances
were taken. I returned to Boston
with Sullivan on Sept 16, 1930. today had a great time.

No 2.
Mile Fall
Sept 1930
scope test




Plued in
Sept 29 1930.

H. Edgerton,
Nov. 14. 1929

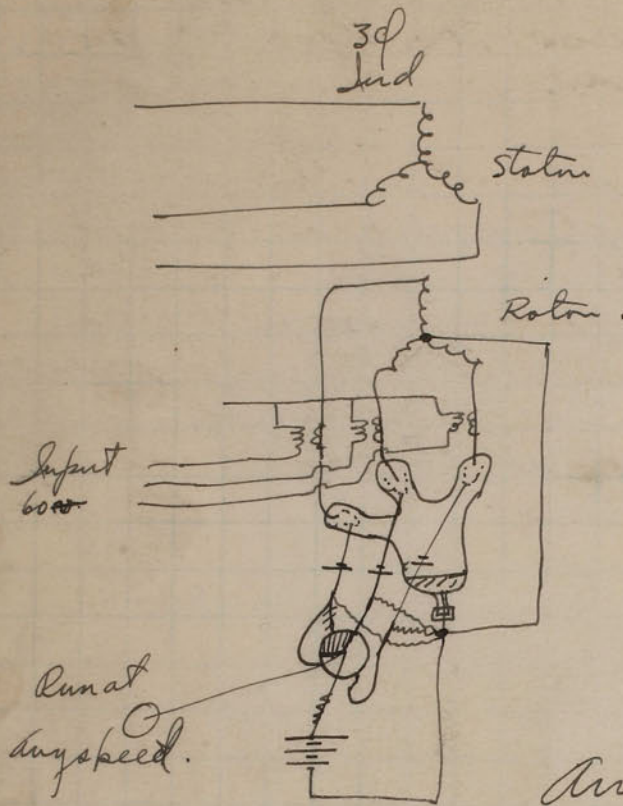

The disadvantage here is that the rectifier works single phase on a heavy inductive load.

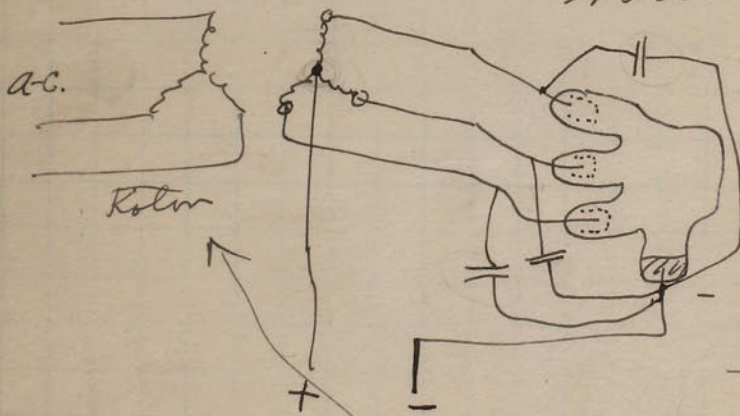Another scheme would be to shift d-c from one arm to another in rotor circuit. The condensers will help the arc to transfer from one phase to the next. The more rotor phases the better such a motor will operate.






It would be best to let the ~~stator~~ ~~armature~~ currents be commutated and put the 3φ into the rotor. Then an anode arm could be connected to each coil.

Sept 29 1930
H. S. Edgerton

Inverter

Inverters that give single phase power will always need to have energy storage properties such as condensers and inductances or the flow of d-c will be objectional.

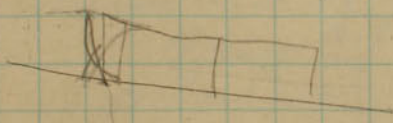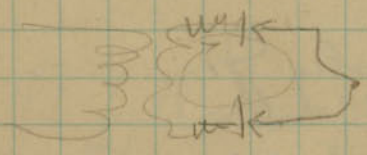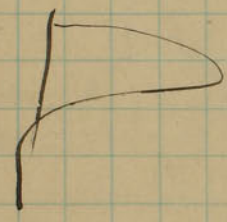
Polyphase inverters however should have particular advantages for the reason that power can be transferred gradually from one phase to the next and thus draw only a continuous flow of energy, no storage device being needed.



Sept 30, 1930
H. L. Hayden

Trooboscope Circuit for ac. operation 120 flashes/sec.

1 Kva 220v = 55 m

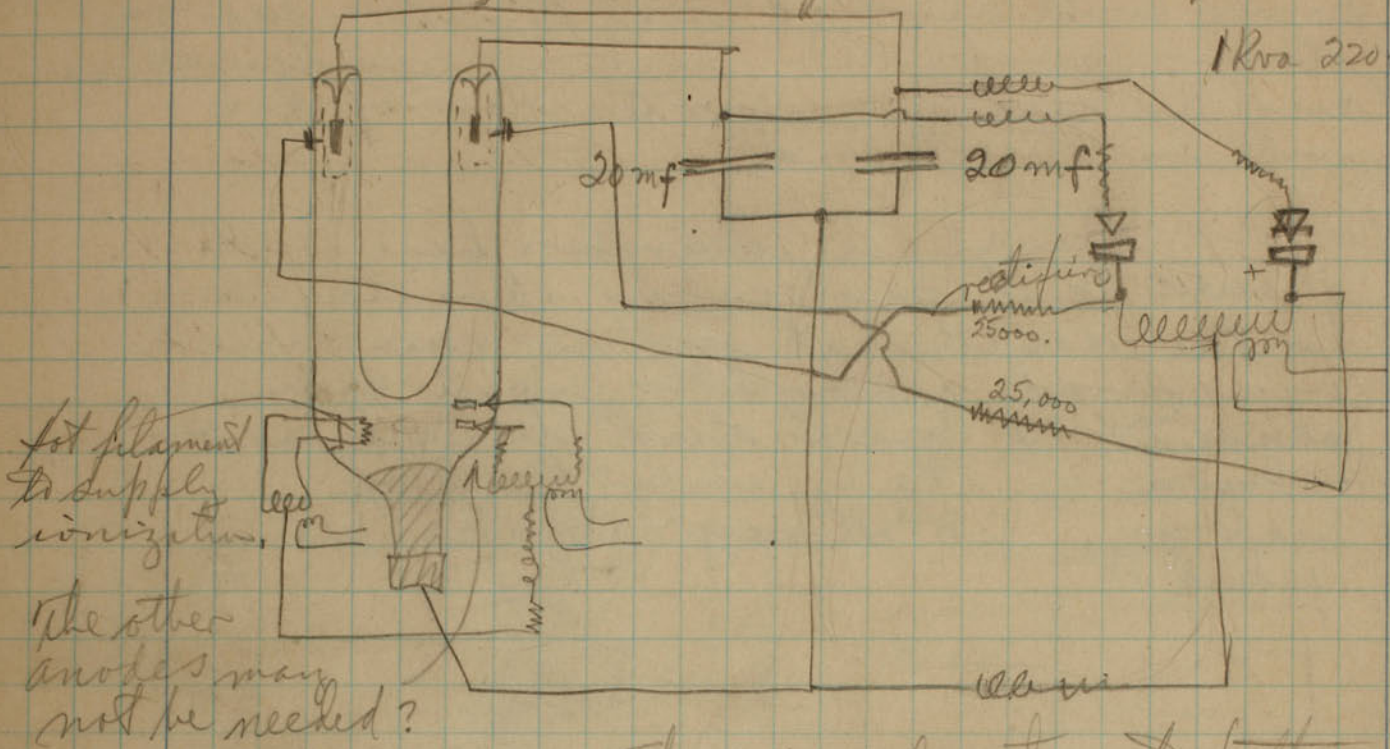

hot filament
to supply
ionization.


The other
anodes may
not be needed?



there is an advantage to putting
resistance in the neutral circuit.

Charles Kingsley Jr.
Oct 2, 1930.


H. L. Hayden
10-2-30

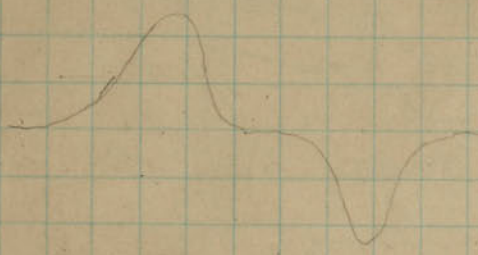

Oct. 2, 1930.
H. E. Edgerton

Speed Regulation of A-C Motors by means of Controlled Rectifiers.

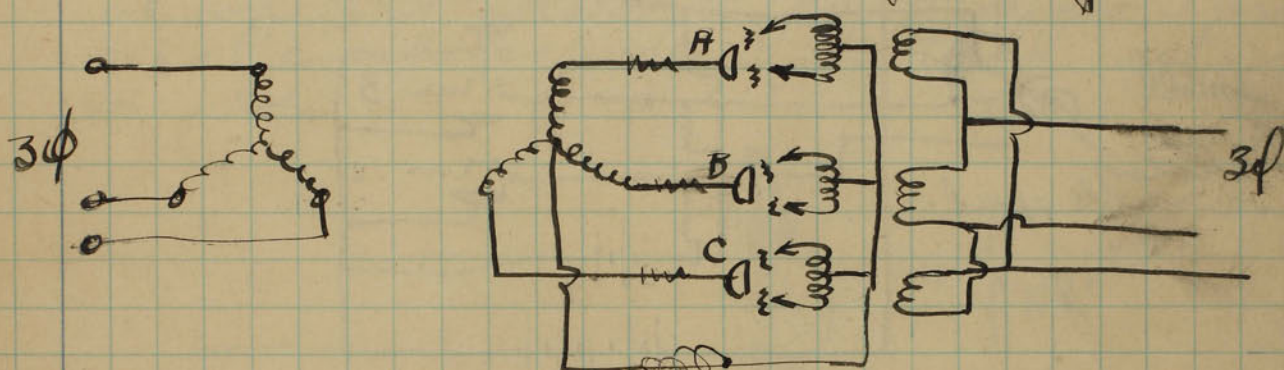The motor used is a wound rotor induction motor. The windings on both sides of the gap are to be polyphase. One winding will be fed by alternating current (polyphase) and thus set up a rotating field. The other winding if fed with d-c will cause the motor to run synchronously. The d-c is in one winding only.




The full wave rectifiers as shown in the sketch (A, B, C) are able to supply d-c to each of the ~~rotor~~ phases. There is no limit to the number of phases.

Now if the phases are fed in rotation at a certain frequency the magnetic field that they produce rotates at a corresponding speed with respect to the rotor. This field will tend to stay in step with the rotating field due to the winding on the other side of the gap. The rotor will run at a speed which corresponds to the sum of the frequency of the supply and the frequency of field transfer or it will run at a frequency which corresponds to the difference of these frequencies.

By this means the rotor can be made to operate at speeds both above and below the synchronous.

cont

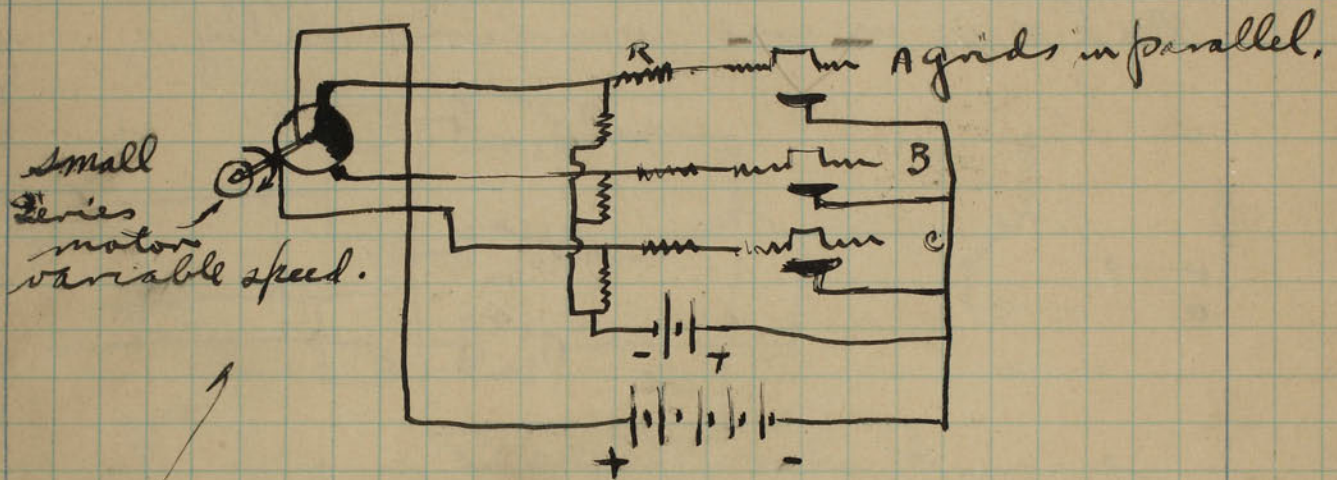The function of the grids in the thyatron rectifier is to control their operation. The grids may be made positive in rotation by means of a ~~small~~ small switch. A more satisfactory scheme would be to change the phase of a-c on the grids such that the change of field from one phase to the other would be gradual.



The contactor switches the field from one phase to the next by making the grids + in rotation.

Charles Kingsley Jr.


Oct 2, 1930

H. R. Hazen




10-2-30

October 11, 1930
S. E. Edgerton

Stroboscope

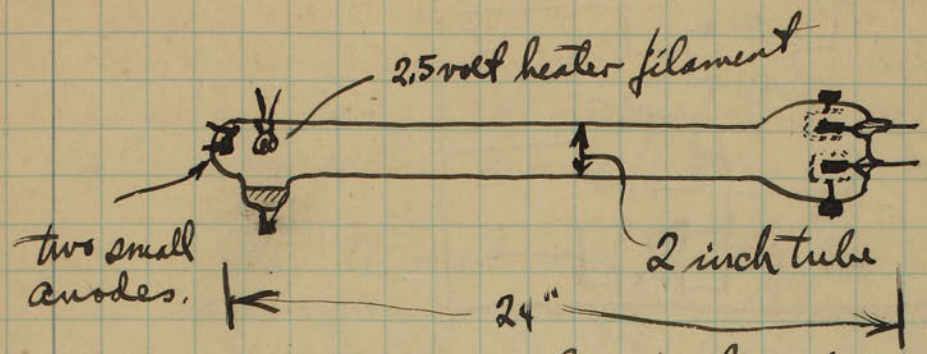

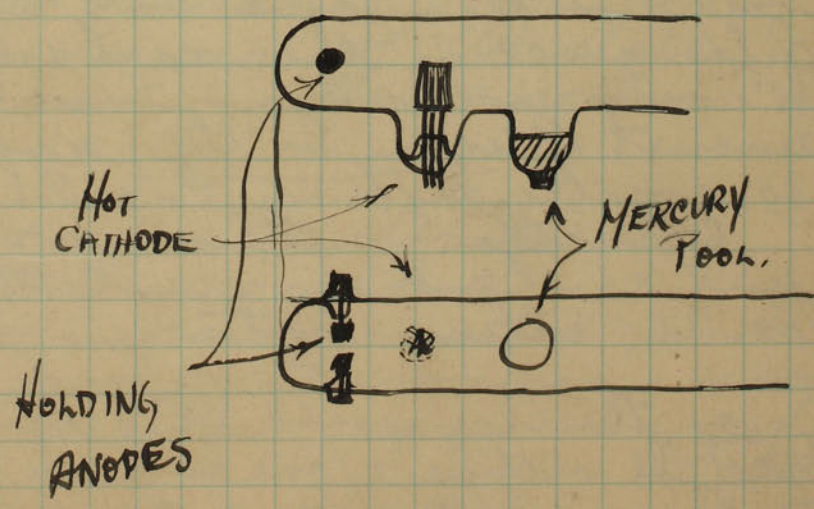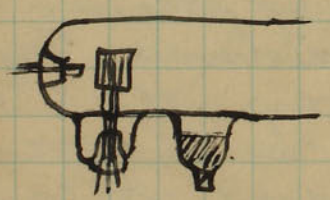
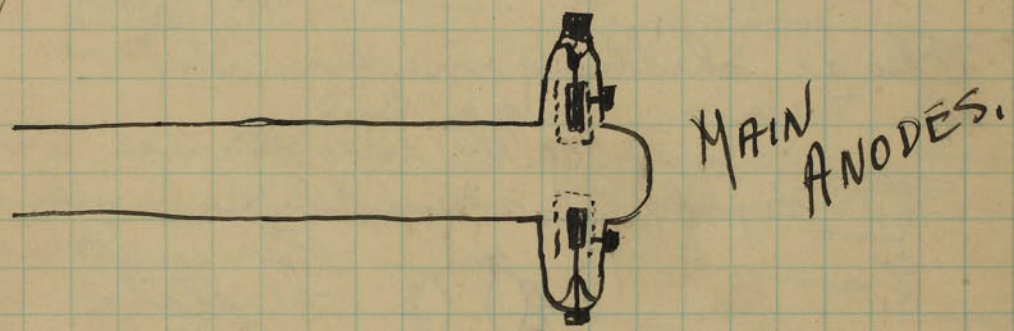
This will be used with the same circuit as shown on page 48. A high resistance connection will probably be put between the mercury pool and the heater filament in order to establish proper potential relationships when the tube gets ready to fire.



12" Disc rotating $\frac{3600}{60}$ r.p.s.
 $60 \times \pi/2 = 2260$ inch sec.
 $\frac{1}{2}$ inch = 222×10^{-6} sec.
 $\frac{1}{4}$ inch = 55.5×10^{-6}
 $\frac{1}{32}$ inch = $14. \times 10^{-6}$


Oct. 16, 1930
A. E. Edgerton,

Speed Control.

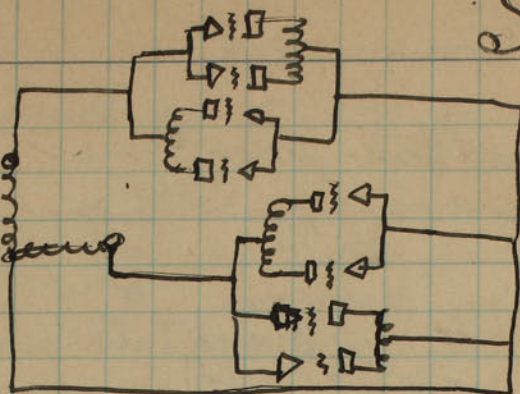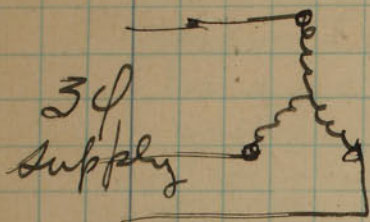

A rotating field will be set up by the 8 thyristors feeding into the two phase rotor circuit. A mechanism will shift the rectification from phase to phase so that the resultant speed is constant in magnitude and rotates at a constant speed.

Phase shifting mechanism

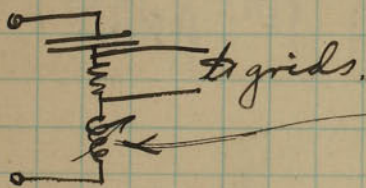


The inductance will be varied periodically. For instance take the stator winding of a small machine. Make the rotor of laminated iron. As the rotor rotates there will be a great difference in the reactance because the rotor is unsymmetrical and the amount of iron in the magnetic path is greatly different in the two cases. Another method would be to put a short circuited ^{90 degree phase} winding on the other rotor circuit.

The idea would be to block completely ^{out} two of the rectifiers (one on each phase). Then the phase shifters (90 electrical degrees in time) would transfer the rectified current from one phase to the next at slip frequency. At that time the transfer was complete, then another would be immediately started, etc.

Cont.

Using two full wave rectifiers on each phase makes it possible to allow current to flow in either direction.

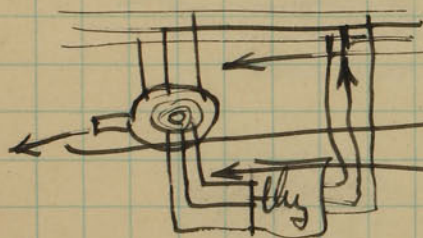The thyristors may be thought of as a frequency converter. They take power from the rotor at slip frequency and pump it back into the lines at standard frequency (when the machine operates as a motor).




Power to motor = 1.0

Shaft power $\approx 1 \times (1-s)$

Power from rotor $\approx 1 \times s$

This power is sent back into the lines by means of the thyristors which act as a frequency converter.

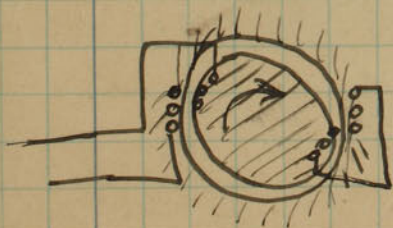If the machine is to be run above speed then power must be put in the rotor circuit. The power that comes out of the shaft is the sum of the stator and rotor power - the I^2R and core losses.



Variometer for ~~shifting~~ changing inductance. A capacitor in series and enough to give near resonance will give large phase shifts for small changes of angle of position of the rotor.

Oct 24, 1930
 N.S. S. S. S. S.


Stroboscope tests.

Spencer of the U.S. Power Co came over with Fish and Thurston, the last two who are photographers for the U.S. P. Co.

The stroboscope was set up to approximate as closely as possible the 15 mile falls job.

A f 3.5. movie camera (35 mm) that belongs to the institute was set up above the disc about 3 or 4 feet.

The ~~best~~ best circuit used was

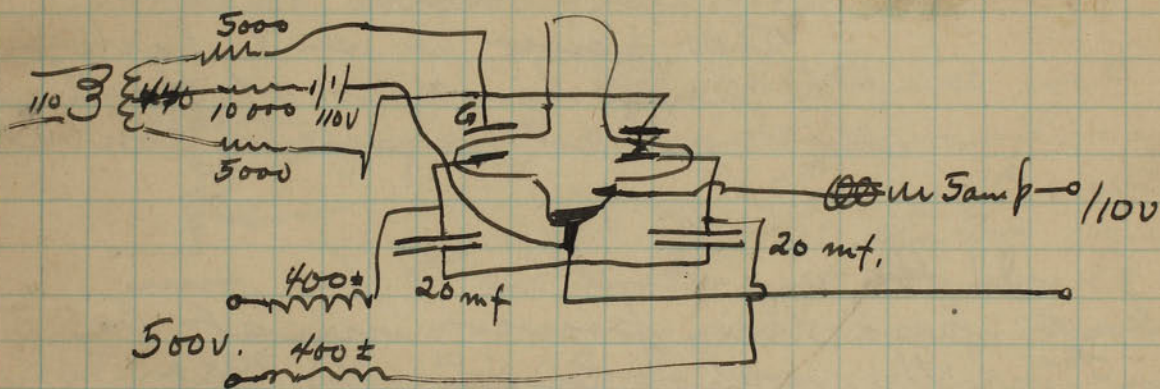

5 frames per second
 f. 3.5 lens.

Oct 30 1970

Notebook Number: T-1

Scanning and Separation Record

 unmounted photograph(s)

 1 negative strip(s)

 unmounted page(s)
(notes, drawings, letters ...)

was/were scanned where originally located between page
54 and 55.

Item now housed in accompanying folder in MC 25, box 166





Notebook Number _____
 Scanning and Separation Record
 (Laminated photographs)
 (negative strips)
 (unmounted page(s))
 (notes, drawings, letters)
 were scanned when on
 and _____
 item now listed in accompanying list


Oct 30, 1930

D.C. Stroboscope

Oct. 25, 1929.
H. E. Edgerton

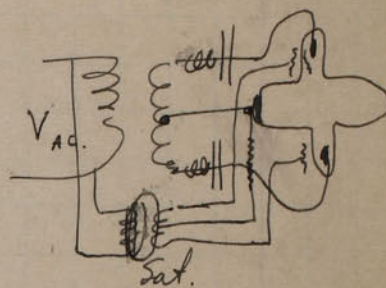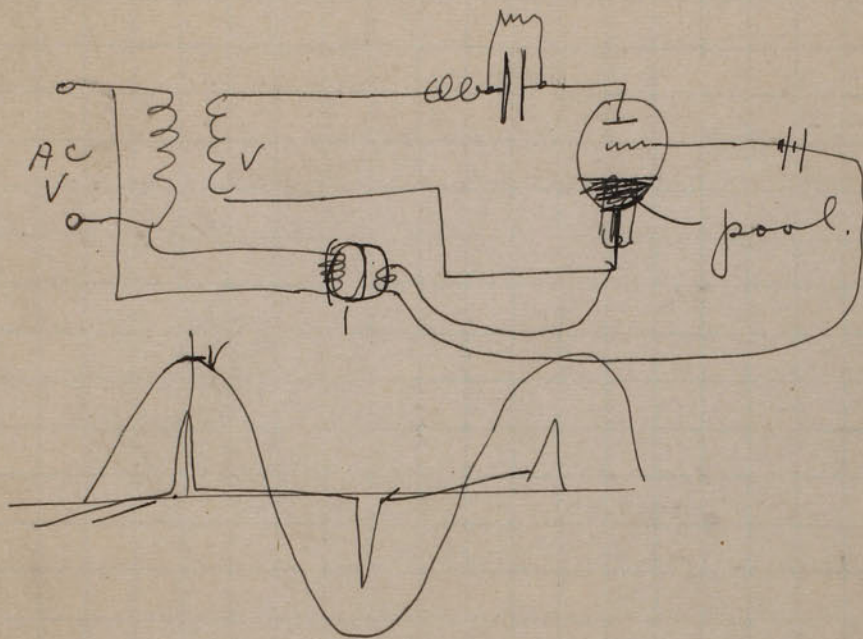


Oct. 25 1929
H. Edgerton.

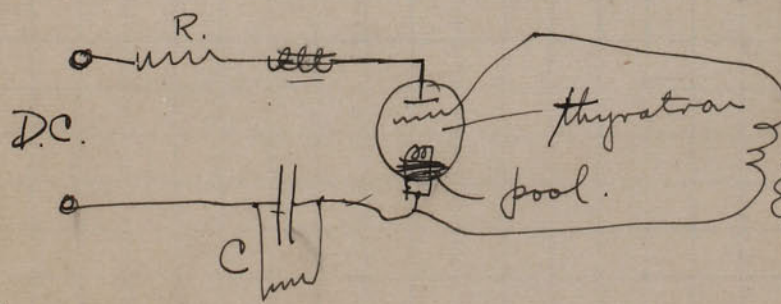

Stroboscope

trip voltage.

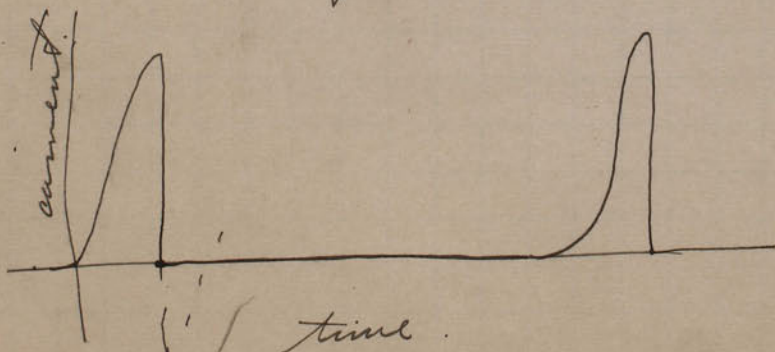

Oct 30 1929

Name H. F. EDGERTON Dept. RESEARCH
(Type write Name and Dept.)

Agreement

Place Schenectady N. Y. Date June 3 1929

In consideration of my employment with the General Electric Company from June 3 1929 to Aug 20 1929, I agree:

I will communicate to the Company's Patent Department all inventions made or conceived by me during my employment by the Company or within a period of one (1) year from the end of such employment which are along electrical lines or along lines of the Company's work and investigations, or of those of companies in which it may have a substantial interest, or resulting from or suggested by any work which I may do for the Company, or at its request, and will assist the Company and its nominees in every proper way (entirely at its or their expense) to obtain for its or their own benefit patents for these inventions in any and all countries, the inventions to be and remain the property of the Company or its nominees whether patented or not.

As a matter of record I have given below a complete list of all inventions, patented or unpatented, including a brief description thereof, which I made or conceived prior to my employment, and I desire that these inventions shall be excluded from this agreement.

WITNESS:

(Signed) Harold E. Edgerton
(Sign first name in full)

State of New York
County of Schene ctady } ss.

On this 3rd day of June 1929 before me personally came Harold E. Edgerton to me personally known, and known to me to be the same individual described in, and who executed the foregoing agreement, who acknowledged to me that he executed the same, and for the purpose therein set forth.

Agnes J. Hardway
Notary Public

RESERVED INVENTIONS AND BRIEF DESCRIPTIONS THEREOF

Stroboscope - a device, using an electrical circuit including an mercury arc lamp, for observing moving objects.

Speed-Control an electrical network for controlling the speed of a d.c. motor.

(Continue list on back of form)

Original to be signed by employee, acknowledged before a Notary Public, and forwarded to the Patent Department at Schenectady. Copy to be given employee.




[SEE OVER]

Oct 30 1890

RESERVED INVENTIONS AND BRIEF DESCRIPTIONS THEREOF (Continued)


A series of horizontal dashed lines for writing, with a vertical line down the center. The page contains very faint, illegible ghosting of text from the reverse side.

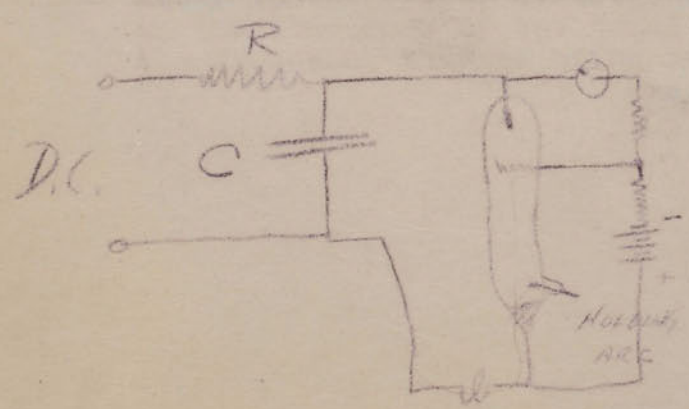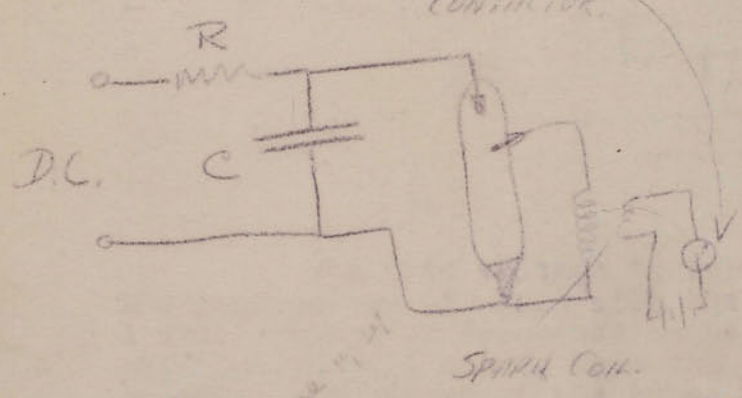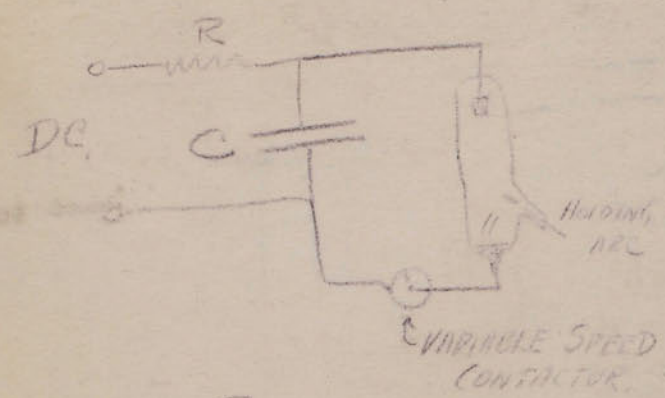STROBOSCOPE CIRCUITS, USING IONIZED MERCURY VAPOR TUBES,



H. F. EDGERTON
JUNE 6 1929.

CIRCUIT TO HOLD CONSTANT FREQUENCY.

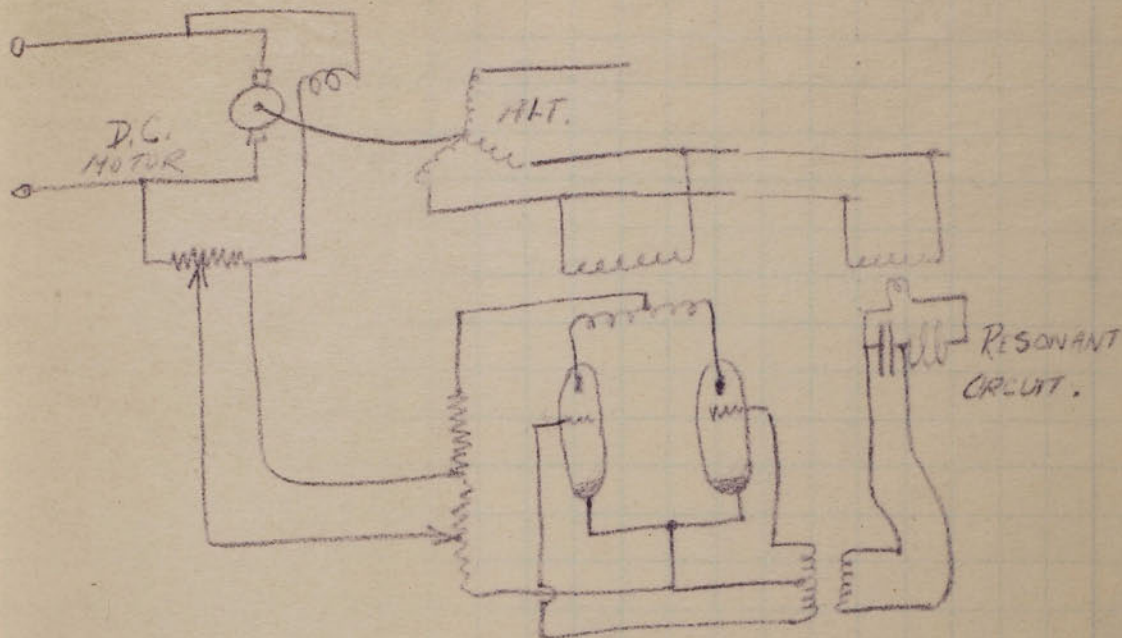


The grid voltage is approximately 180 degrees out of phase with the anode voltage. A small change of frequency means a large phase shift which will either turn the thyratrons on or off. The output of the tubes is connected so that it influences the field of the d.c. motor in the proper direction. A small change in the constants of the tuned circuit will move the frequency that is being regulated.

H. E. Edgerton
June 6, 1929.

Spectrum Analysis
of Troboscope Output,
Stockberger's Radiation Laboratory.


Nov. 22, 1930
A. S. Edgerton

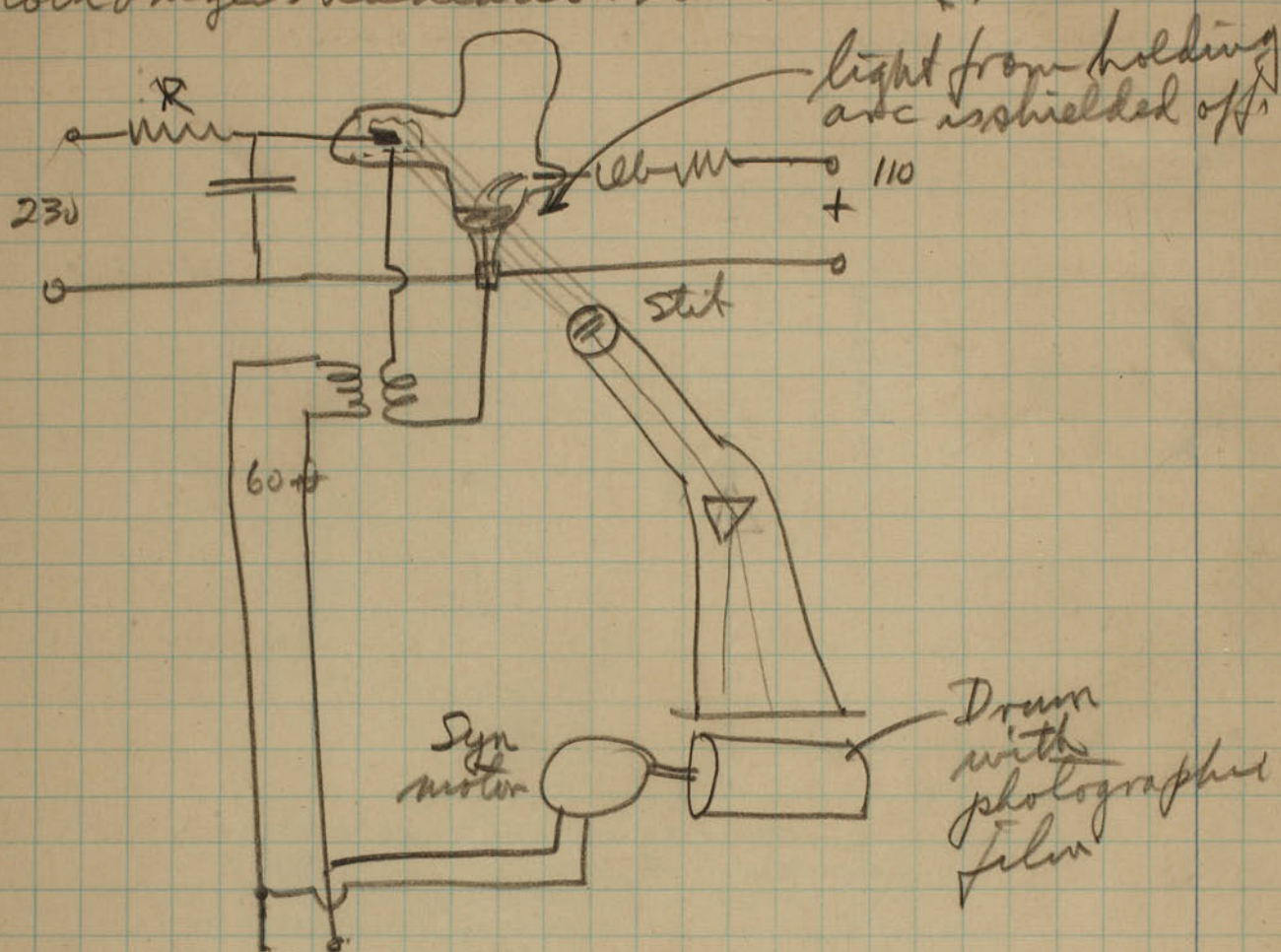


This picture looks interesting. Apparently there is a shift of wavelength which is about 6 angstroms for one wave length according to Stockberger. MacCubbin said it might be due to Doppler effect. The persistence of some of the lines give a clue to the deionization time.

Mon Nov 24 1930
D. E. Day

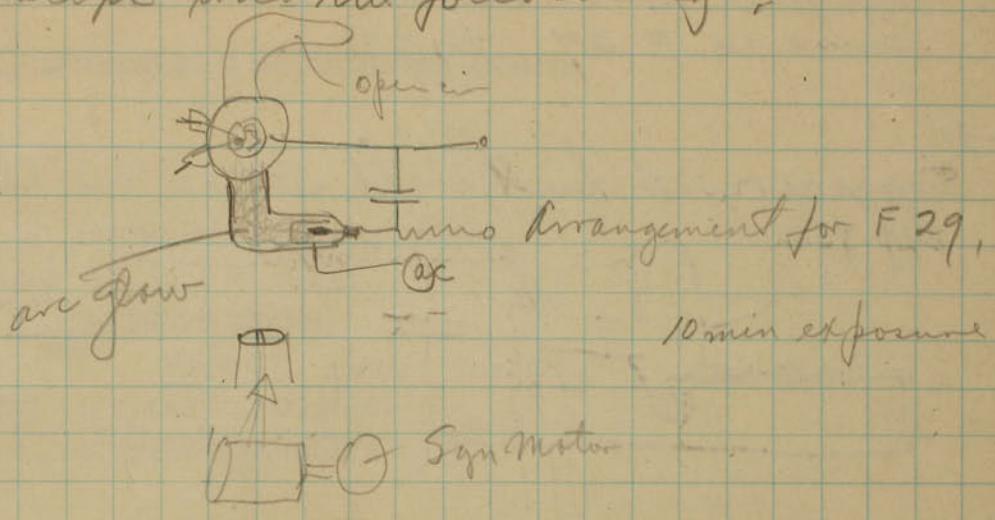For the picture taken Saturday the arrangement of the thyatron and the spectroscope was the following.



Tests today.

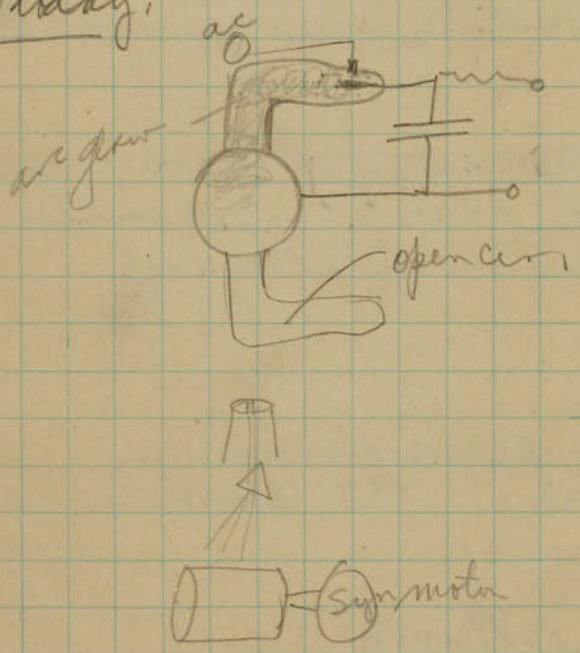


Arrangement for F30.

30 min exposure.

Arrangement for F31.
10 min exposure.

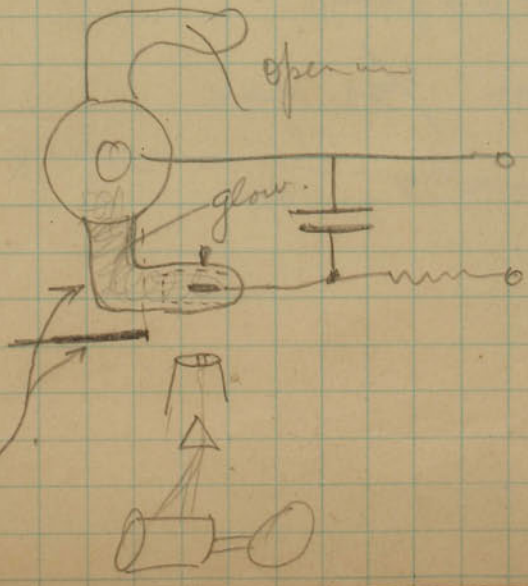Cardboard screen to shield light from part of arm



November 28, 1930


J.H. Edgerton, D.C.S. & L.B.

Radiation Laboratory ⁴⁻¹¹⁵ see B-32 notebook.

F32. The slit was reduced from 3mm to $\frac{1}{2}$ mm.
Same as F29, Exp 30m.

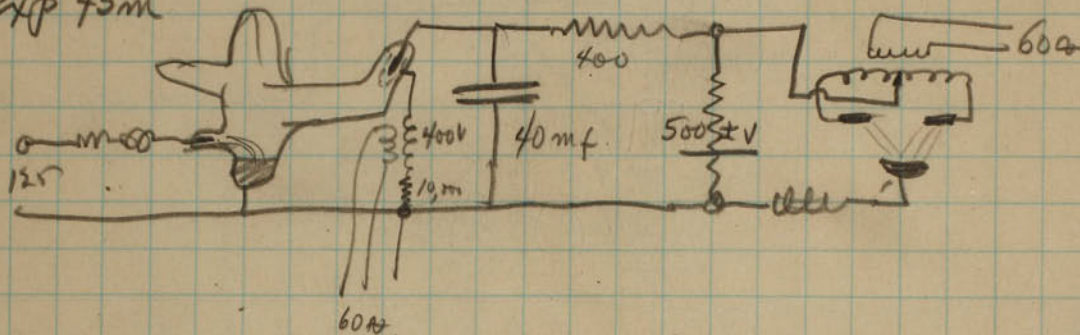11-29-30.

F33. Same circuit but with 500v± on the condenser
Exp 45m



Full wave 500 volt rectifier used for cond. supply - rect.

F34 Same circuit as for 33 except for
220v on grid and a bias of -110 volts.
4 feet of lamp cord put in discharge
circuit.
Exp 1 hr 19 min.

F35. Same as 34. Two exposures
90° apart #1 1 min #2. 5 min.

Circum of drum $10\frac{1}{8}$ inch
Speed = 1800 rpm.

$10\frac{1}{8}$ inch for $\frac{1}{30}$ sec

$$1 \text{ inch equals } \frac{1}{30 \cdot 10\frac{1}{8}} = 3290 \times 10^{-6} \text{ sec.}$$

Notebook Number: T-1

Scanning and Separation Record

1 unmounted photograph(s)

 negative strip(s)

 unmounted page(s)
(notes, drawings, letters ...)

was/were scanned ^{in place on page} where originally located between page 61 and .

Item now housed in accompanying folder in MC 25, box 166

↓ F29

10 MIN

↓ F30

30 MIN

F 31





10 MIN



F 32



30 MIN

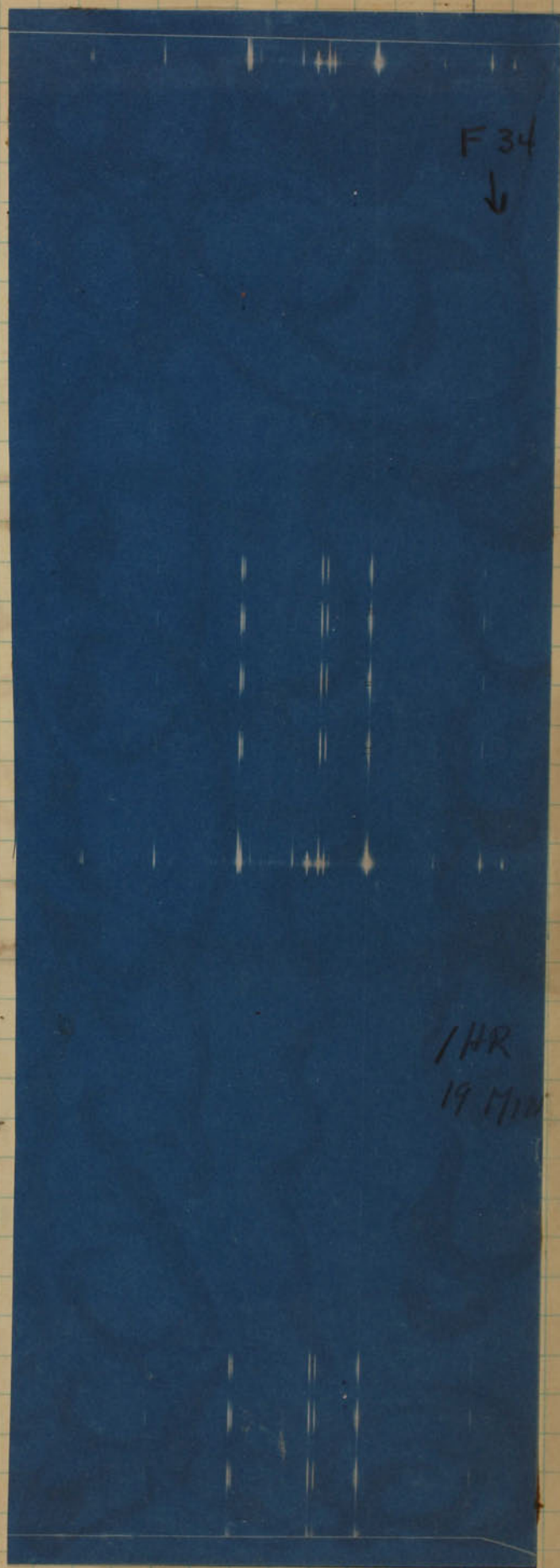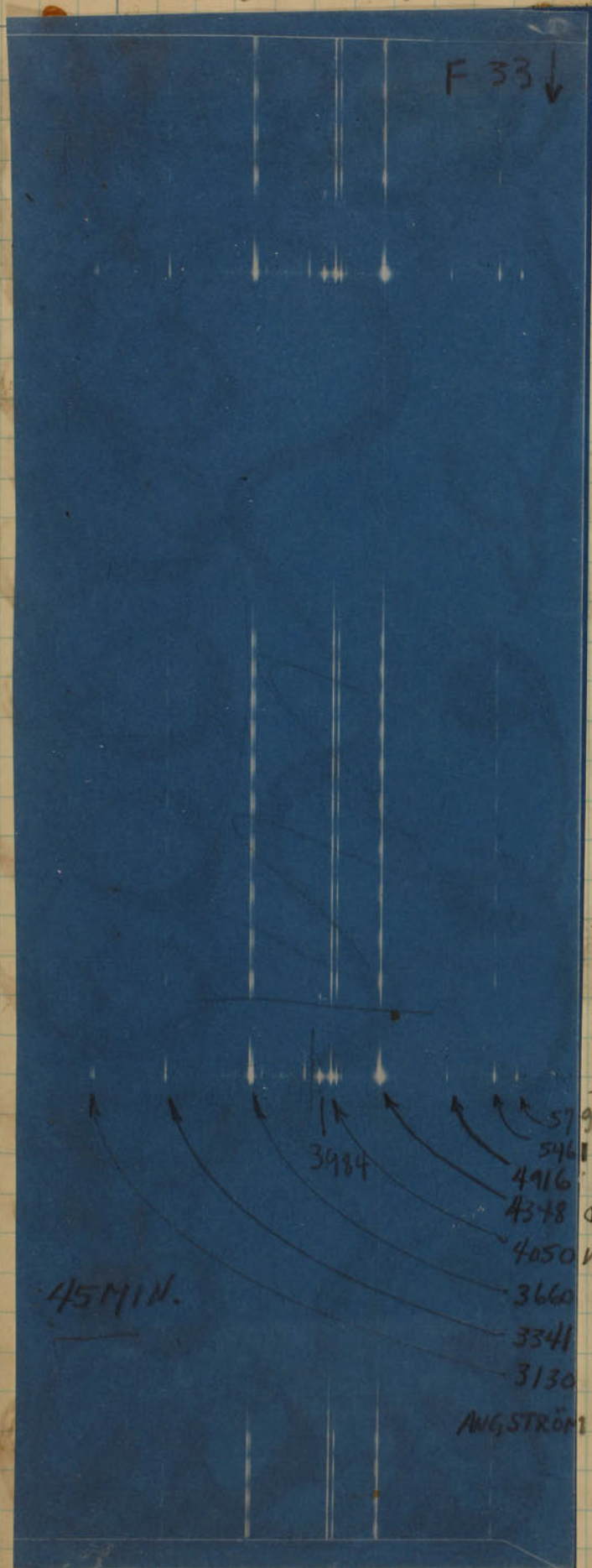

1 ANGSTRÖM = 10^{-8} CM.

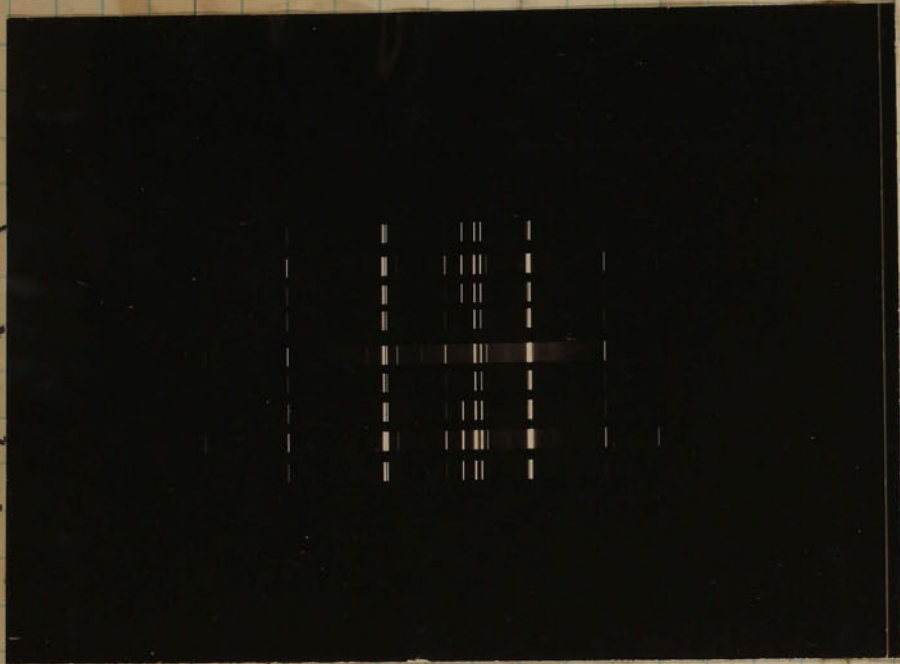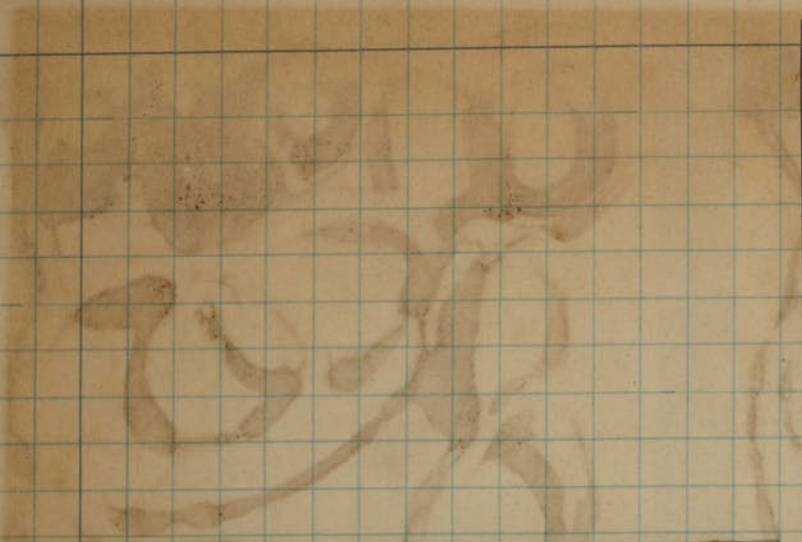

S
C
S

↑
S - Stroboscope
C - Ordinary arc 0.5 amperes ±.

↓ F 35

1 MIN



5 MIN

Notebook Number: T-1

Scanning and Separation Record


 unmounted photograph(s)

 2 negative strip(s)

 unmounted page(s)
(notes, drawings, letters ...)

was/were scanned where originally located ^{in envelope on page} ~~between page~~
65 and .

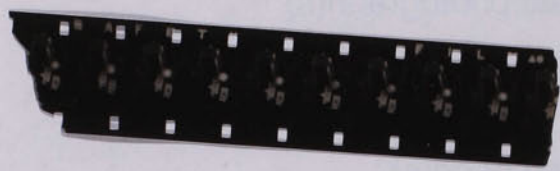Item now housed in accompanying folder in MC 25, box 166





Moving pictures taken
of Substation Generator
Dec 6 1930 by Henry Lane.
F 1.9 lens. Cinekodak .16 frames per sec
Panchromatic film. H.E. Edgerton
Chas Kingsley

Enlargement on page 85 of
some of these films. Still
photo on page 82.

Dec 4, 1930
H. E. Ziegler

Prevention of Hunting.

Method of making the quadrature excitation a function of the slip so that the excitation will help to stop angular oscillations.


Synchronous machines are as a rule not sufficiently damped as a consequence are subject to violent swinging at times of load changes.

This circuit endeavors to apply an auxiliary excitation in the quadrature axis, which is a ~~frequency~~ function of slip. DC in the quadrature field shifts the axis of the combined excitation voltage or the combined field ampere turns. This shift of the field is the same as changing the angular displacement. Consider a motor just after a sudden load has been put on the shaft. The deficiency of torque causes an acceleration and thus a slip. As the slip becomes appreciable an excitation is introduced into the quadrature field in such a direction that it shifts the resulting field axis towards its final value. This immediately reduces the acceleration and reduces the over swinging. If the rotor should swing too far the slip will be the opposite in sign and the excitation in the quad. field will reverse and thus shift the excitation axis back ~~again~~.

Method of obtaining voltage prop. to slip.

A small polyphase machine directly connected to the shaft is supplied by polyphase current from the large machine. The rotor of this small machine will have no voltage induced in it when the rotor is running synchronously. As soon as the speed departs from synchronism because of slip there will be an induced voltage.

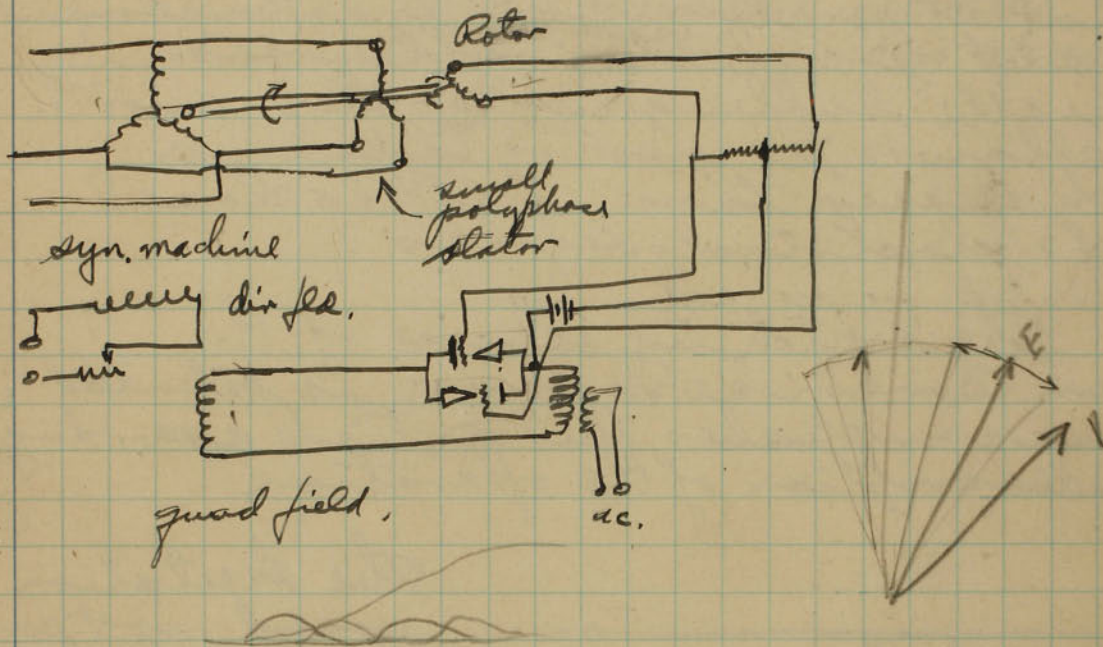The induced rotor voltage allows current to flow in the quadrature field by means of a thyatron. Two thyatrons are used so that the direction of current can be controlled.




Dec 15, 1930

Thyatron relay for switching
the excitation to a synchronous
motor at the most favorable angle.

An electrical device which can
close the field switch of a synchronous
motor at an angular displacement
of about zero electrical degrees
makes the pulling-in step smooth
and allows the motor to pull in
much easier than if it is closed
at 180 electrical degrees.

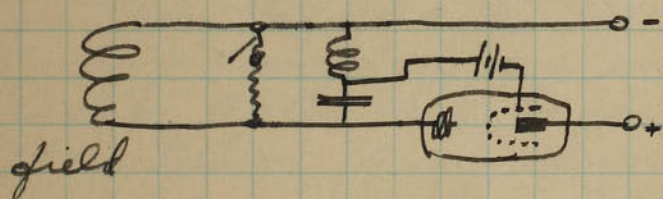
The switching scheme of the
Brown Boveri company is patented
and accomplishes this action according
to this description of the operation.



This circuit does not have enough good
features.


The excitation
would not come
on until the
frequency of
the induced
current in the
motor was small.


Dec 16 1930

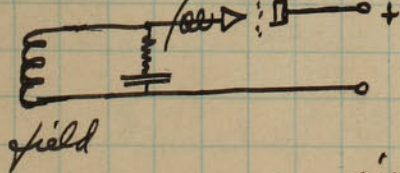

Field discharge in series
with a condenser so that
any ac can go through

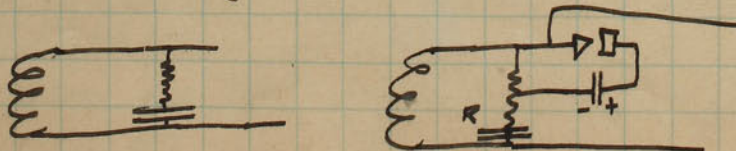I wonder what an
induction motor will
do if it has a rectifier in
its rotor circuit? This will
make a good experiment to try.




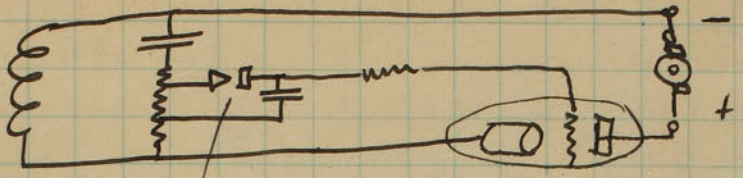

rectifier to give to grid neg. bias
and thus hold off the discharge in the
thyristor until the motor is up to speed.

Dec 17, 1930
 J. J. E. H. H.

A-C Thyatron Stroboscope Circuit

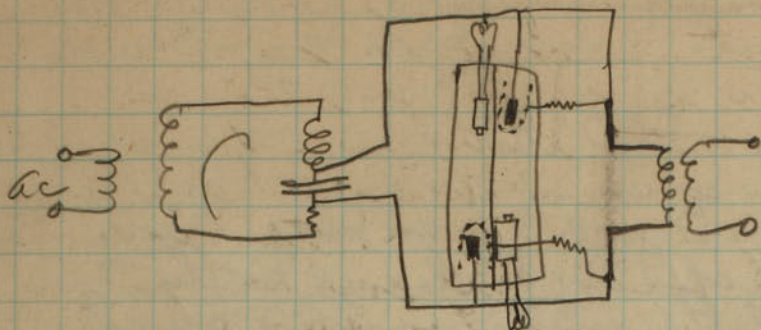

The condenser will build up a charge each half cycle and then discharge through one or the other of the two stroboscope tubes which are put in parallel but out of phase.


Dec 21 1930
H. E. Edgerton.

The intermittent speed of the film in moving picture cameras can be eliminated as well as the shutter by using stroboscopic light for illumination. Lansil and I discussed this last Friday at the P.E.E. problem section. The film would run through the camera at a continuous speed and the ~~film~~ shutter would be open all the time. The stroboscopic light would be synchronized so to speak with the film so that an intense light flash would occur when the film was in the right position.

This scheme would certainly be ideal for fast movies since the main difficulty as I understand is the mechanical movement of the film. The time of exposure is about 10×10^{-6} seconds, with the stroboscope circuit that I have now, I believe that this can be speeded up more if necessary.

Projection could also be made by reversing the process, a concentrated stroboscopic light would fall on the continuously moving film for so short a time that it would appear stationary.


Colored movies could be taken using two or more sources of light, for instance a red neon stroboscope and a blue mercury stroboscope. They would flash on ^{so that} alternate frames of the movie film ^{would be} ~~exposed~~ ^{the film} panchromatic stock. Projection would require also two lamps one red and the other blue which would operate ~~alternately~~ on alternate frames in the projector. The speed of projection would be 30 frames per sec or more so the eye could not detect the different colors.

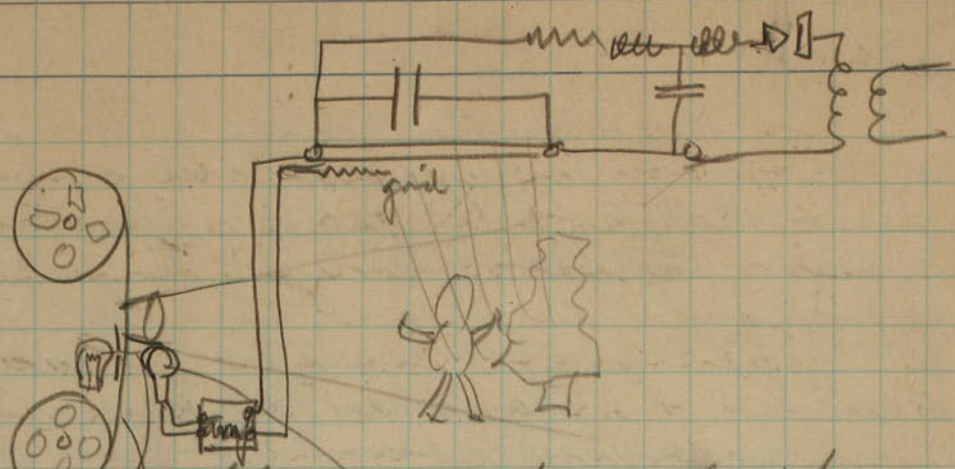

film runs at constant speed
no shutter

Photocell to flash light on object in synchronism with the frames of the film.

Double Color movies.

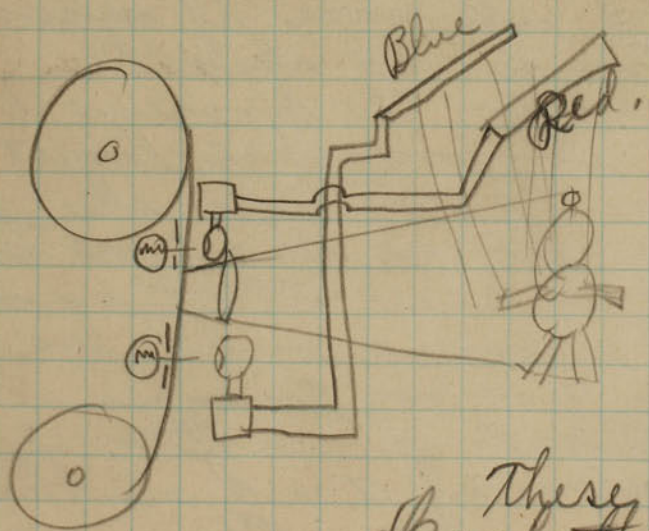

These photocells flash the lamps in synchronism with the frames. One cell flashes the red light every other frame and the alternate frames are flashed with the blue light on the object.

Jan. 17, 1931
 P. E. Elyator

Prof. Bowles helped take some more movies of the 160 hp motor in the dynamo laboratory on Thursday Jan. 15, 1931

These were taken on Panchromatic film at $f/1.5$ and at a film speed of 32 frames per second.

A telechron clock (1 r.p.s.) was photographed at the same time as the motor.

600-volts (or less) were used for the condenser.


Switching transients showing the pulling into step transients were taken. These were for a load of \quad kw on the 24 cycle machine.

The field current was 10. amps (\pm).

Jan 19, 1931


For the Popular Science lectures Prof Bowles used my stroboscope to show that communication could be sent by sending different ~~currents~~ frequencies down a line and having them light a tube which would stroboscopically stop a letter on a rotating disc.

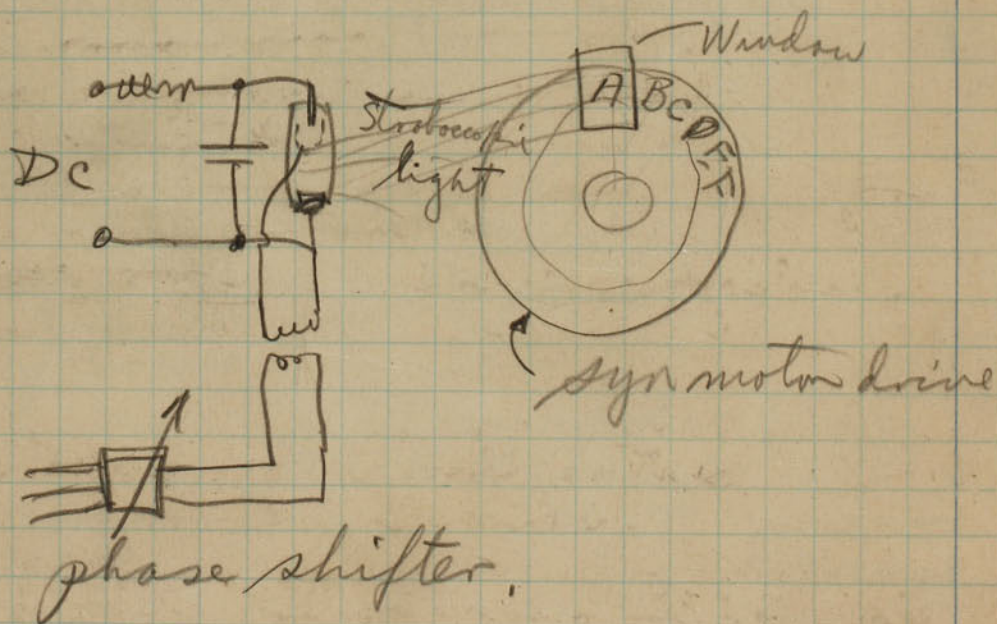Another way to do this would be to transmit phase. A disc could be covered by a screen and left open at only one place. A series of tellers driven by a synchronous motor would show eye letter through this hole depending upon the phase of the current sent down the line.



This scheme was disclosed to Carl Metzger and Prof Bowles.

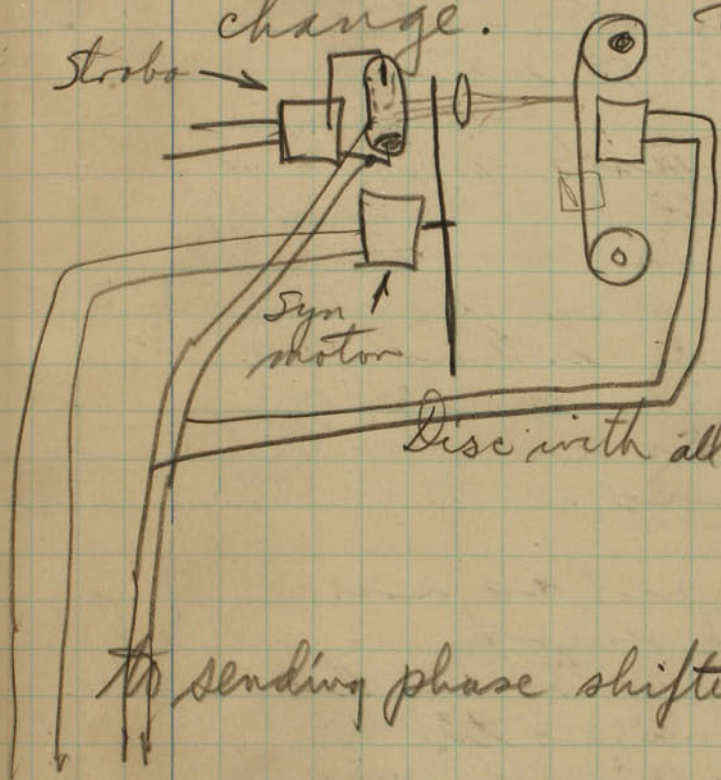The letters might be holes in the disc and the light focused on a piece of Bromide Paper. The paper would move intermittently at the same time the phase would change.



this could be done electrically quite easily with a relay device

Disc with all letters and numbers and a blank.

The message would come out in a strip and could be glued to some ordinary telegraph sheet.

During our experiments last week end we noticed that the light from the new tubes that Dr Hull and Mr Brown furnished us gave decidedly different colors during the main flash and the trailing ghost discharges.


I think that this might make a way in which to change the quality of light from a mercury-arc lamp. An electrical circuit that makes a fast violent transient would accelerate different colors from the tube. Other gases might help in getting the other colors also.

Jan 17 1930. Method of starting a
 S. Edgata mercury arc lamp (hot cathode).

One of the main difficulties of a mercury arc hot-cathode lamp is the difficulty of getting it started. Usually a high voltage is required.

Now if a high resistance wire is ~~be~~ put in the tube and brought down ~~to the anode~~ it towards the cathode from and connected to the anode, it will extend the electrostatic field of the anode so that it can start an arc with a rather small voltage.

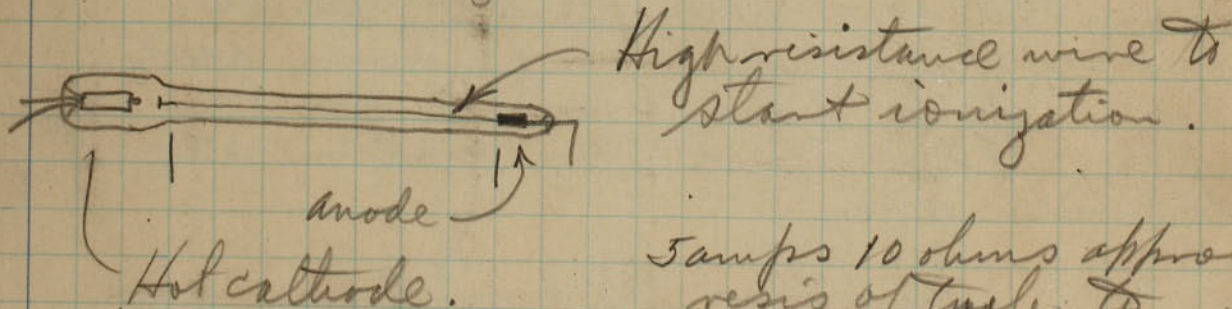
This will ~~will~~ act as an "accelerator" and will start ionization near the cathode. As the gas in the tube ionizes the main arc current will short the starting wire and it will not operate. The wire might be called a "pre-ionizer" since it starts the ionization.




5 amps 10 ohms approx.
 resis of tube to
 5 amps.

The resis. should be about
 50 to 200 ohms or more.

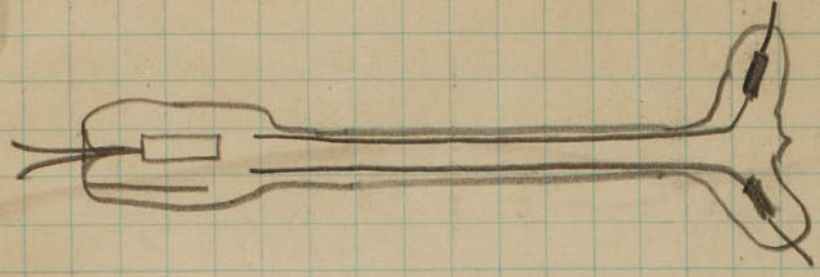
With a ac arc one ^{wire} would be put on each anode.



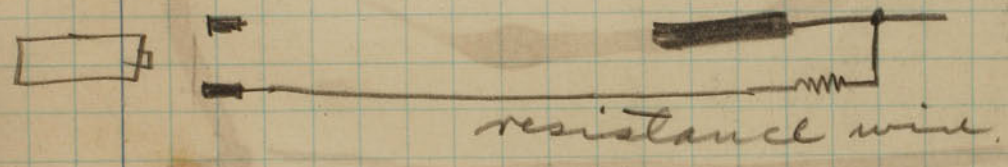It would be better to connect the wires to the back of the anodes



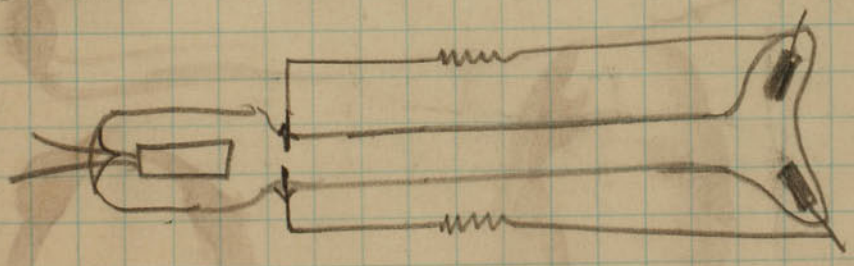
Another way would be to put ~~the~~ a small anode near the cathode and connect it with a high resistance to the main anode or two of them to the main anodes.



Glued Jan. 28, 1931.
H. E. Edgerton.

Jan. 29, 1931.
H. E. Edgerton.

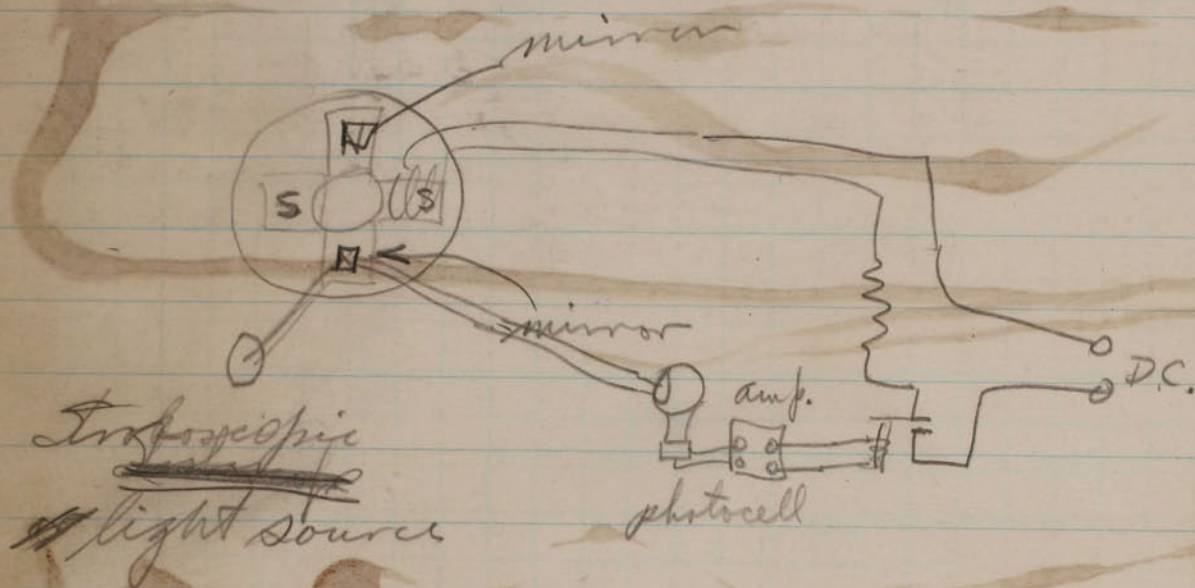
A method of synchronizing a ~~the~~ salient pole synchronous motor by switching the field current at a favorable angle.



A light beam from ~~the~~ a light would be reflected by a mirror on ~~the~~ a pole and so adjusted so that it would strike a light sensitive device at a favorable angle.

Feb 3/1931.

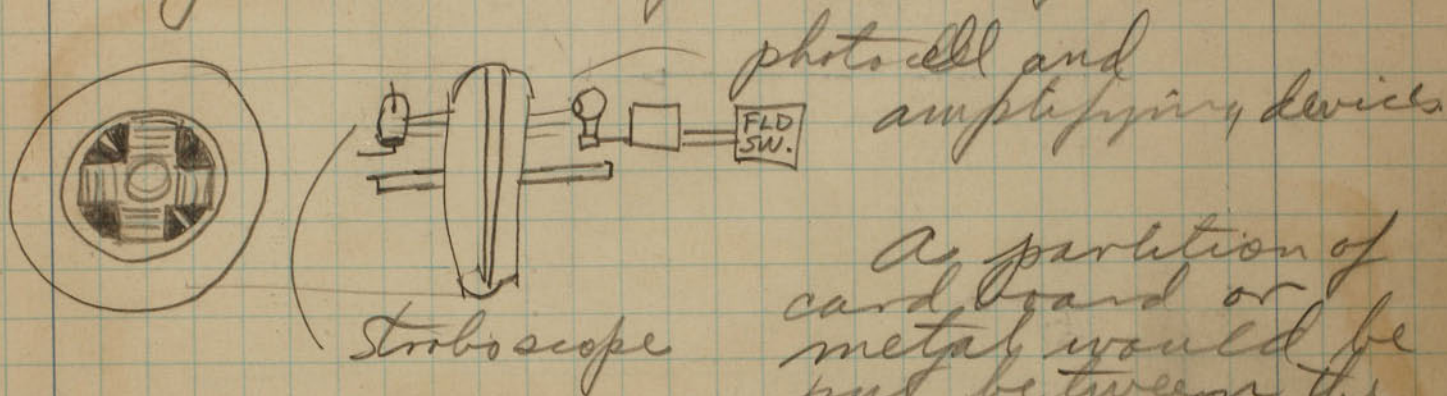Another way to switch the synchronous machine at the correct angle would be to allow the stroboscopic light to pass between the poles and then fall on the photocell.



A partition of card board or metal would be put between the poles and would allow light to only pass when the angle was favorable.




I remember having had this explained to me at about the date of above. I was then living with H. E. Edgerton.

J. S. Gray
Nov. 7, 1935


Feb 3 1931.

cont

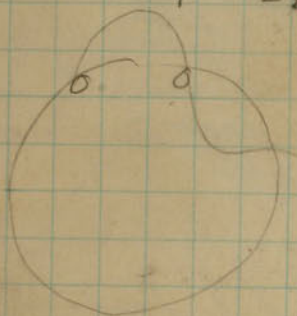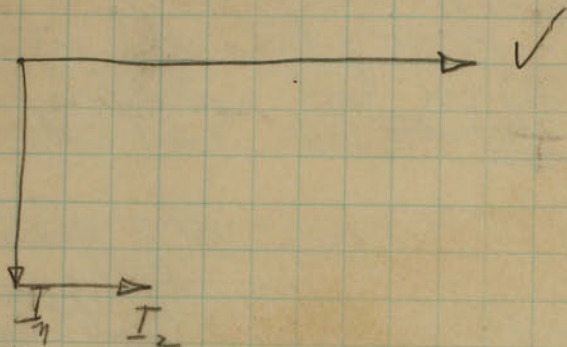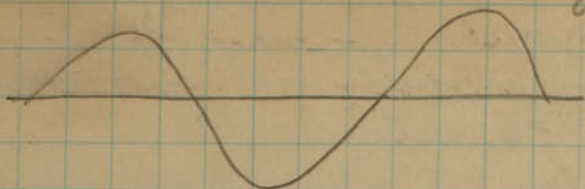
Method of exciting field of Syn Motor at a favorable angle.



slip rings

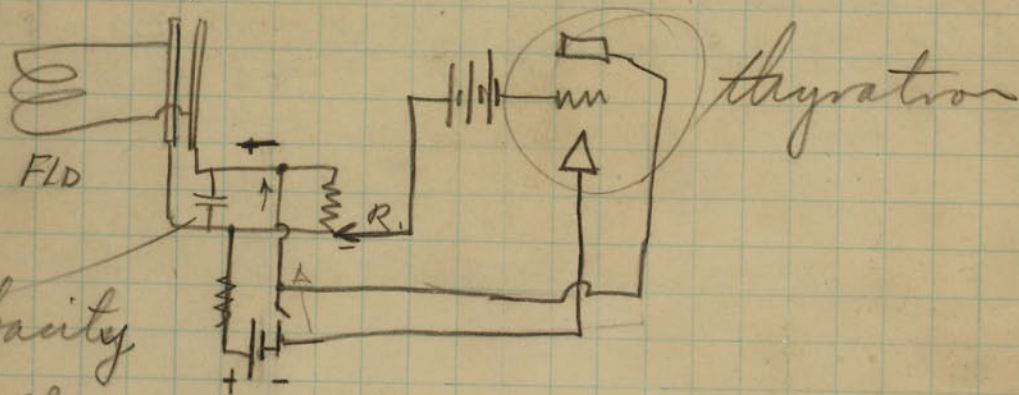


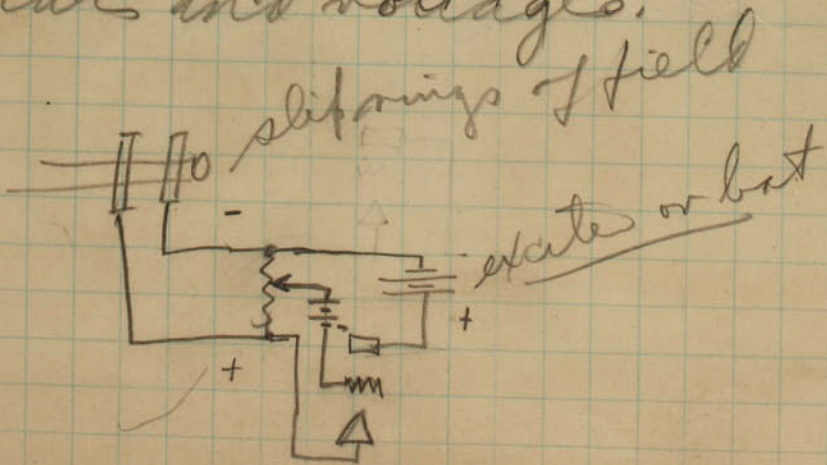capacity to reduce high frequency currents and voltages.




Feb 5 1931 H. E. Edgerton.

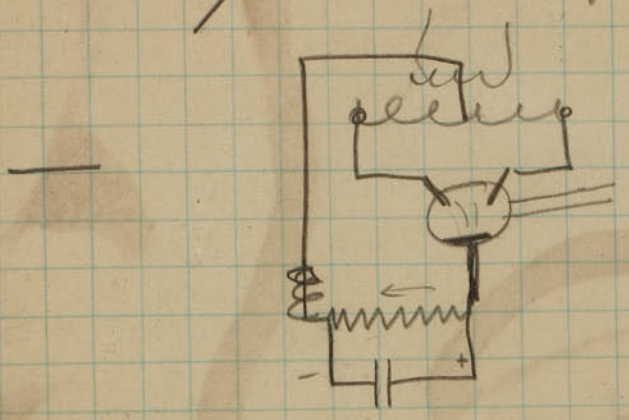Stroboscope circuits
using the holding arc
for a rectifier.



The polarity
comes up
wrong.

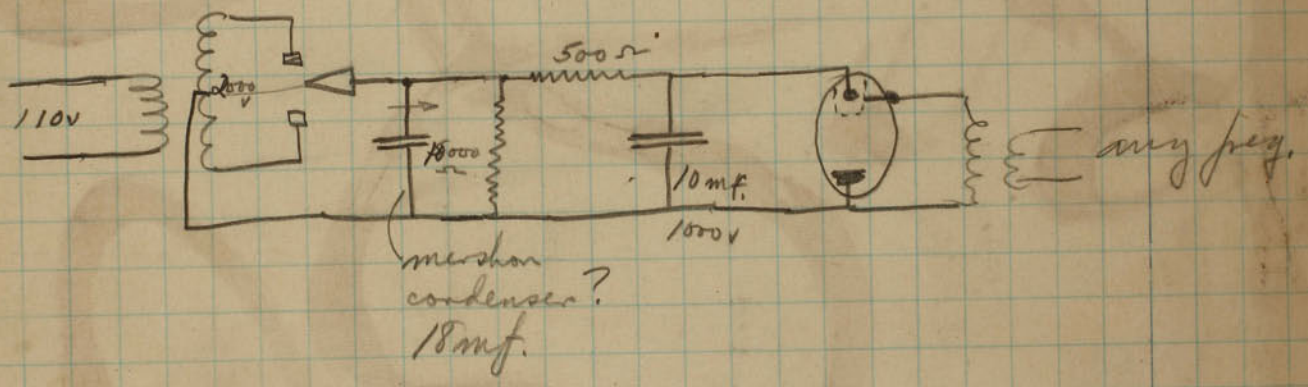


*Stroboscopic photograph taken by Conant,
of M. I. T. Photo Service.*




Circuit for M.I.T. Dyn Laboratory Stroboscope

Feb 6. 1931

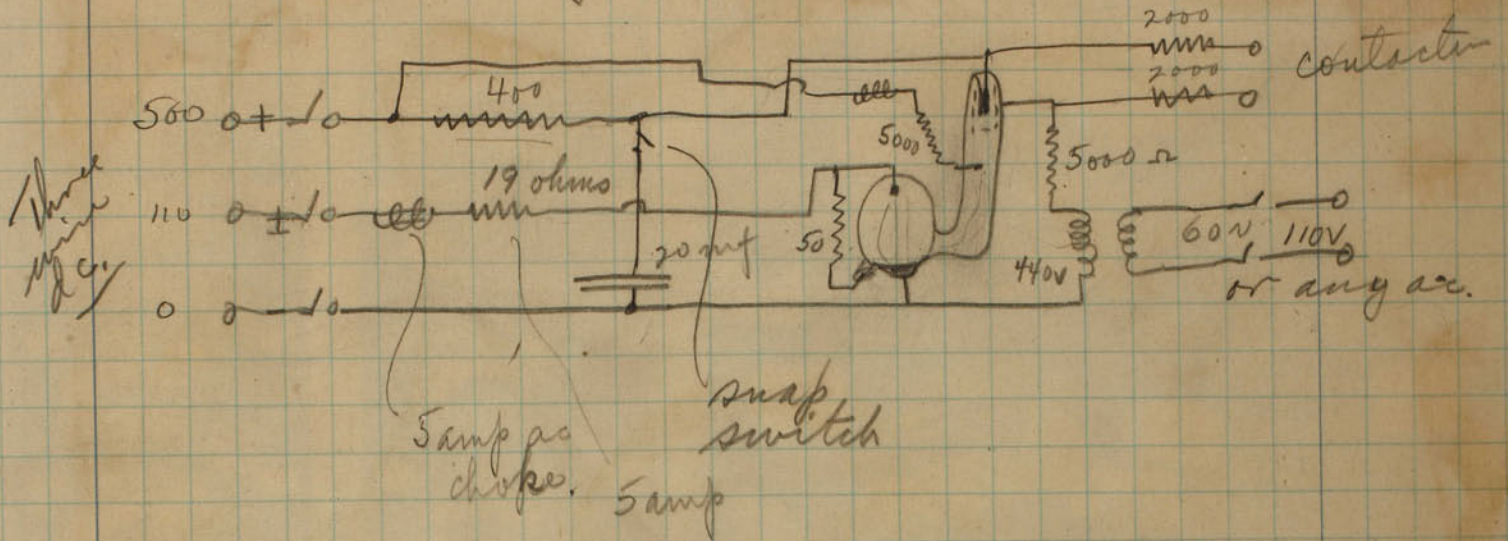

All ac model

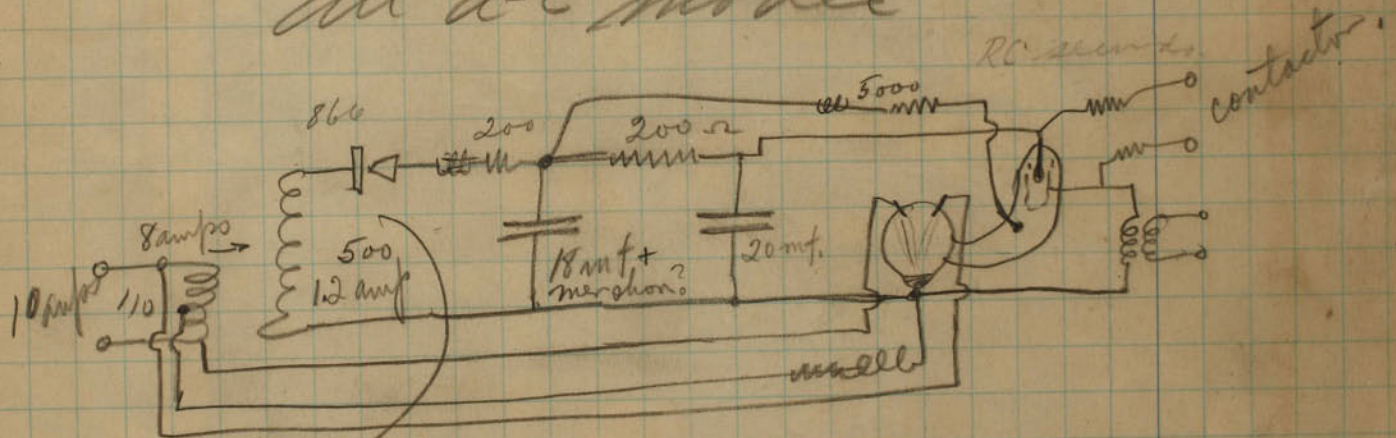


Hot cathode mercury-arc rectifier.

kick starts in combination with holding circuit


Feb 7 1931
H. E. Edgerton


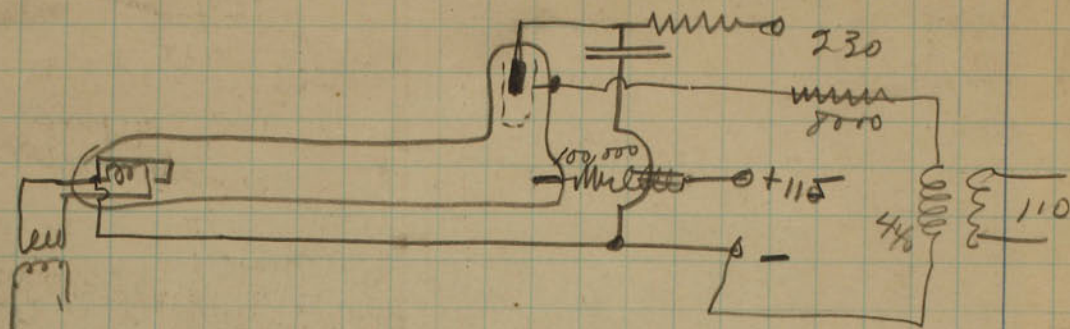
Stroboscope tests
with hot cathode thyatron
from Dr. A. W. Hull and G. A. Fouad.



This tube does not seem to work as well as the pool type. The images seem blurred when ~~the~~ attempts are made to push up the light intensity. Oscillations occur with no volts on the grid. Factors influencing the frequency are the condenser capacity, the charging resistance, the grid resistance and reactance, the reactance of the grid anode circuit ~~of the~~ undoubtedly will influence the freq also.

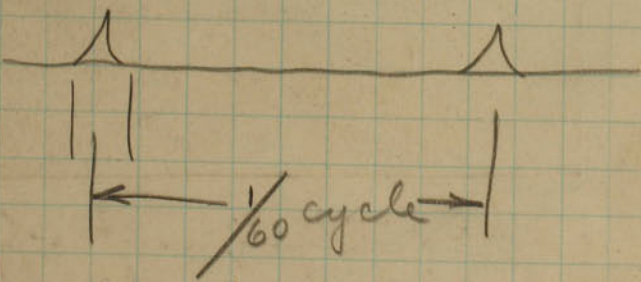Oscillographic observation of the plate or anode current when the violent oscillations discharges were made was as shown below. This illumination was unsatisfactory for most strobe purposes.



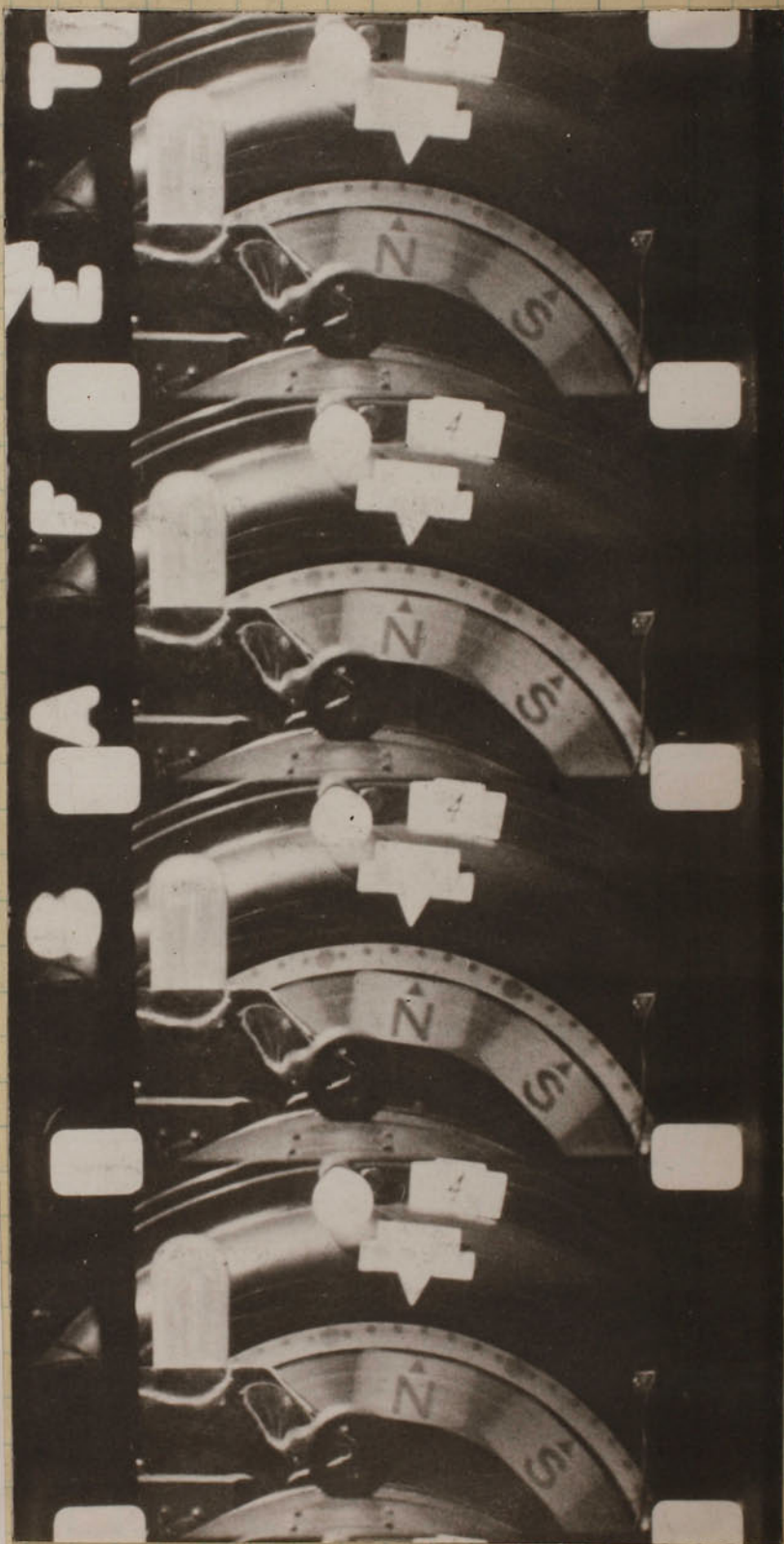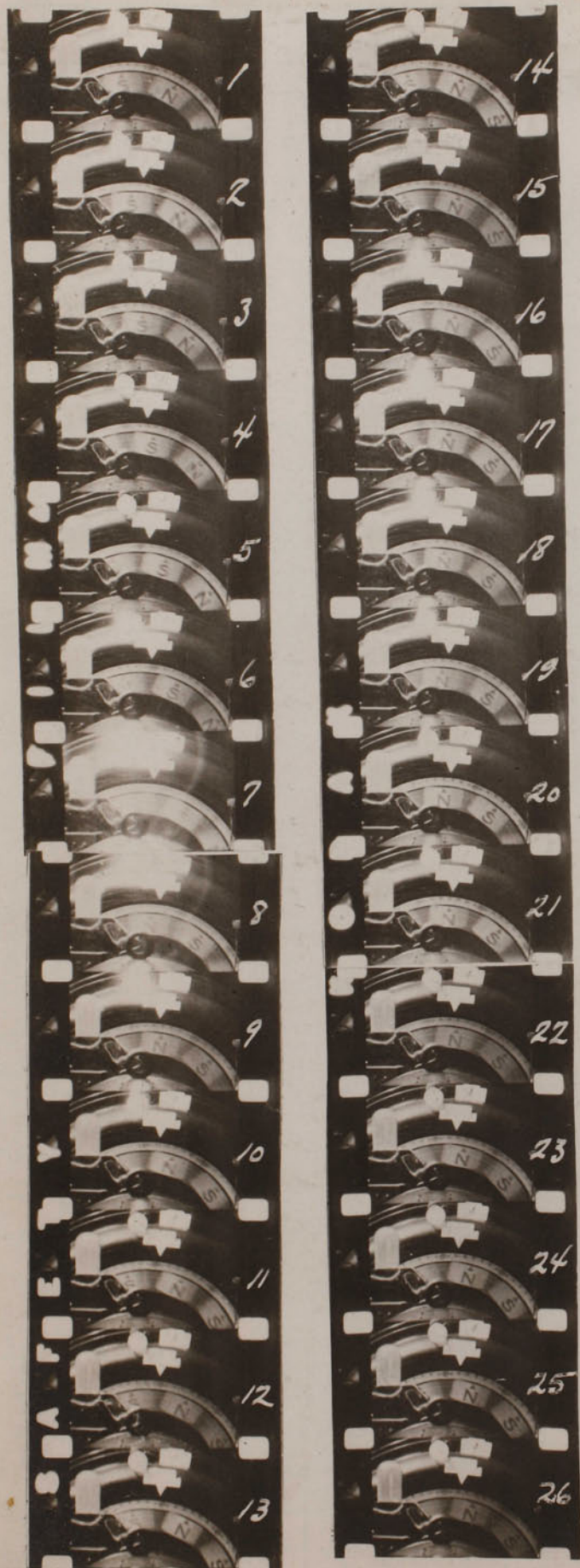

↑ 8x enlargement of 16mm film that was showed in New York at the AIEE Convention on Jan 30 1931.

Feb. 10, 1931.
H. Edgerton

Dynamic volt-
ampere characteristics
of oscillations of mercury
arc tube with condensed

Factors influencing phenomena.

E - dc supply voltage.

R - charging resistance.

C - capacity across tube.


R_g - res in grid circuit.

temperature of tube.

L_1 in chg circuit (inductance)

L_g in grid circuit.

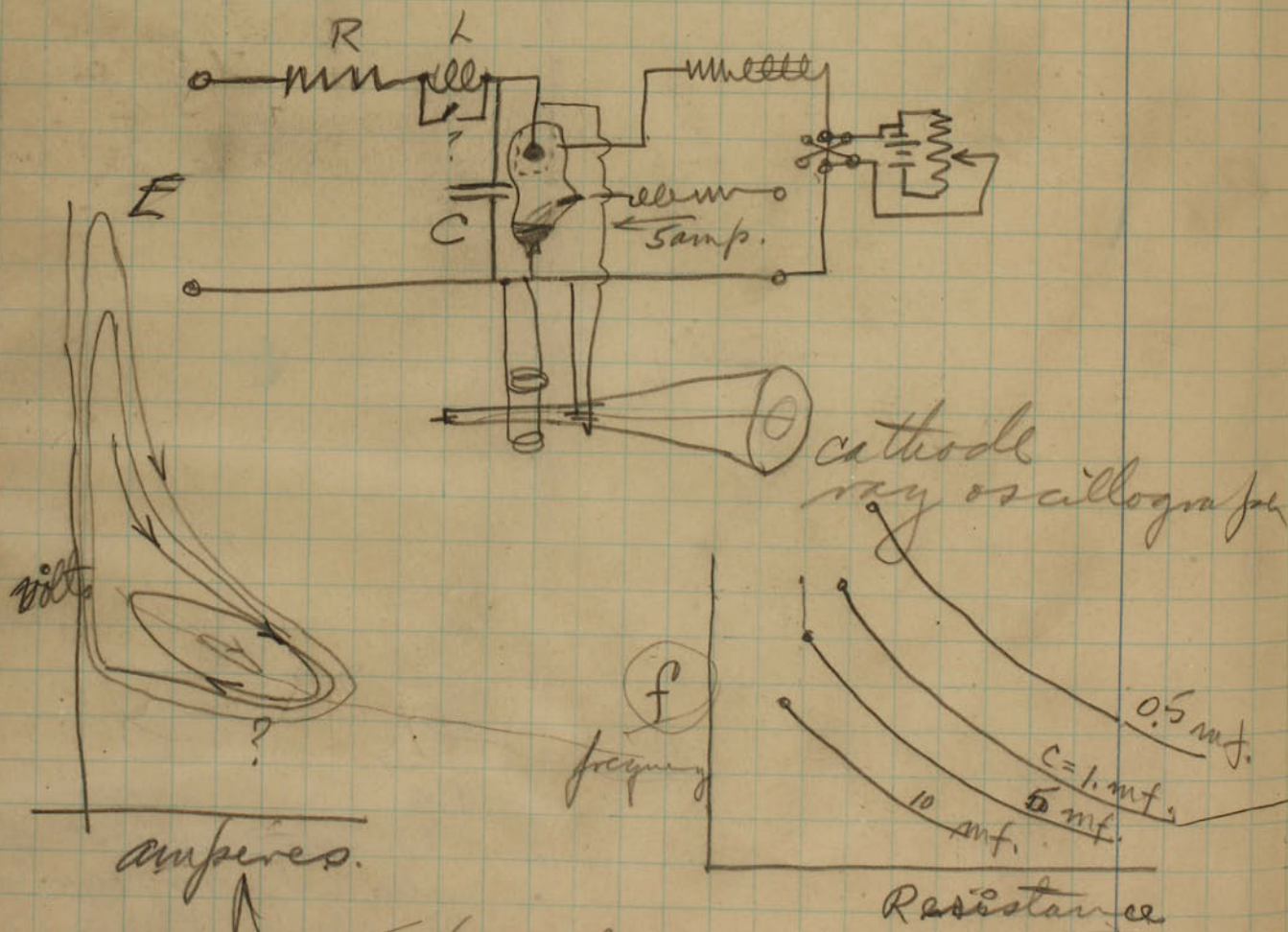Other factors might be R and L
in the discharge circuit.




Expected results
The light from these oscillations are shown
on pages 62 and 63, 61, 64.


Feb 10 1930

I had a talk with Tom Kilham today. He wants to use my spectroscope ~~to~~ for the aluminum spectrum of M. I. The Physics glass blower is going to make the tube and ~~then~~ they will exhaust it too. Two of them will be made, one spare.

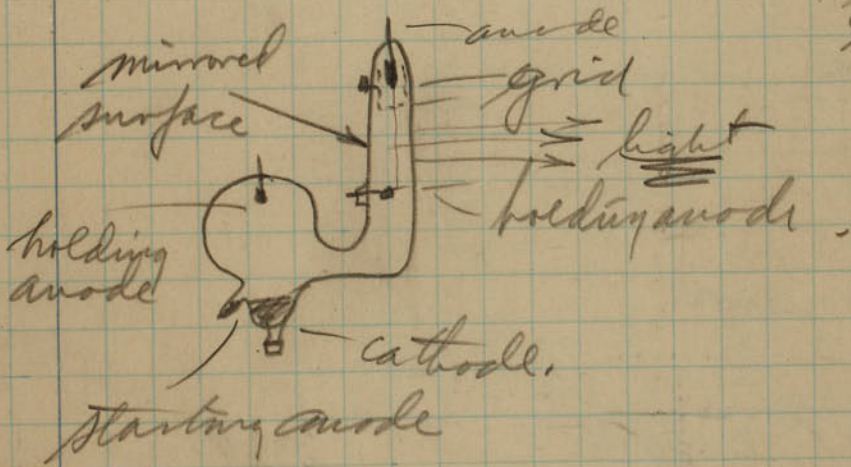Kilham suggested that the tube might be mirrored, this will be great, I think. The tubes we are going to make are like this. The mirrored surface will be connected to the grid and will help sweep over the tube.




Feb 11 1930

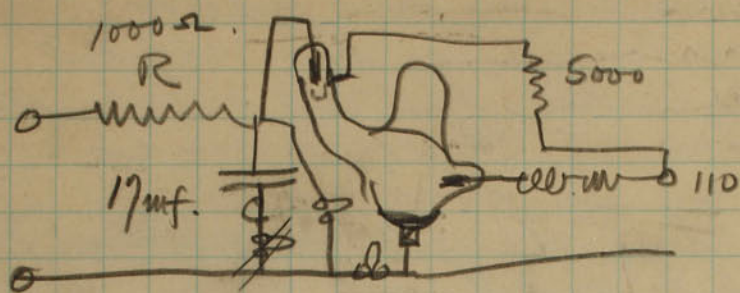


Grid
settings on osc.
volts, amps.

	V	R	C	volts,	amps.
Osc. No. 1.	230	1000	17mf.	1.5	.075
fast	2	230	"	"	"
"	3	430	"	"	"
slow speed.	4	430	"	"	"
fast	5	"	"	"	"
slow	6	330	"	"	"

Appearance of oscillograms

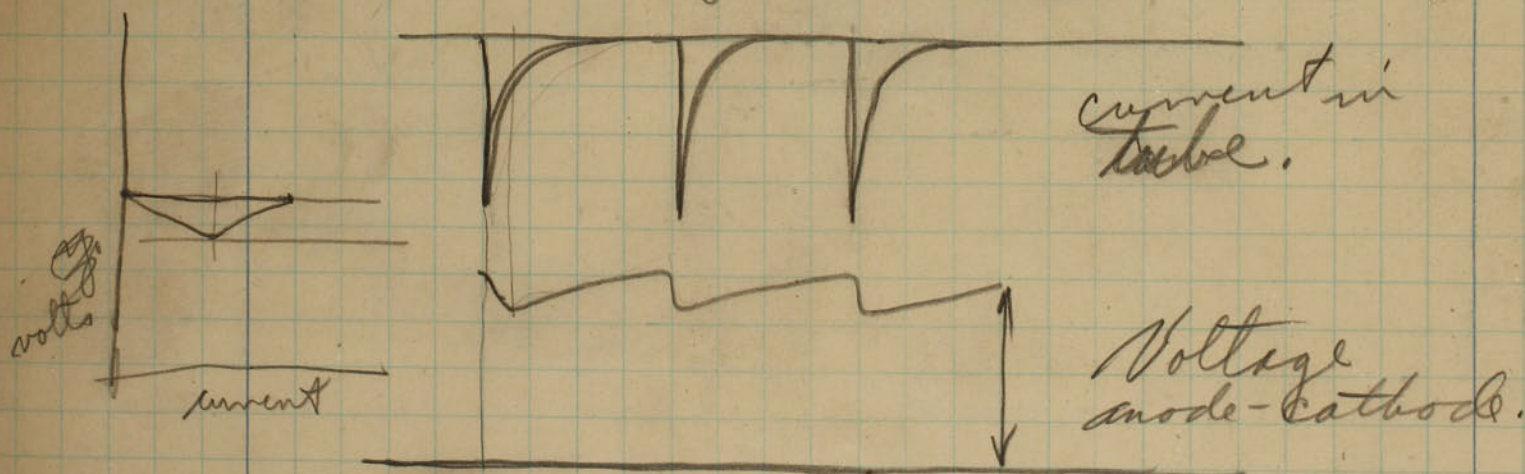

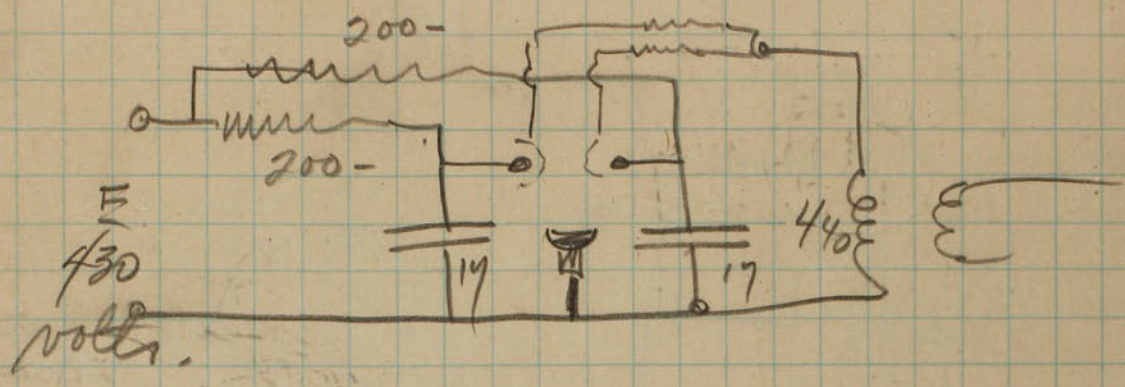
The frequency increases with the dc voltage and ~~the~~ the decrease of charging resistance.




$$RC = 200 \times 17 \times 10^{-6} = 3400 \times 10^{-6} = .0034 \text{ sec.}$$

$$\frac{1}{120 \text{ sec}} = .0083 \quad 230+$$


120 $\frac{1.00}{1.00}$

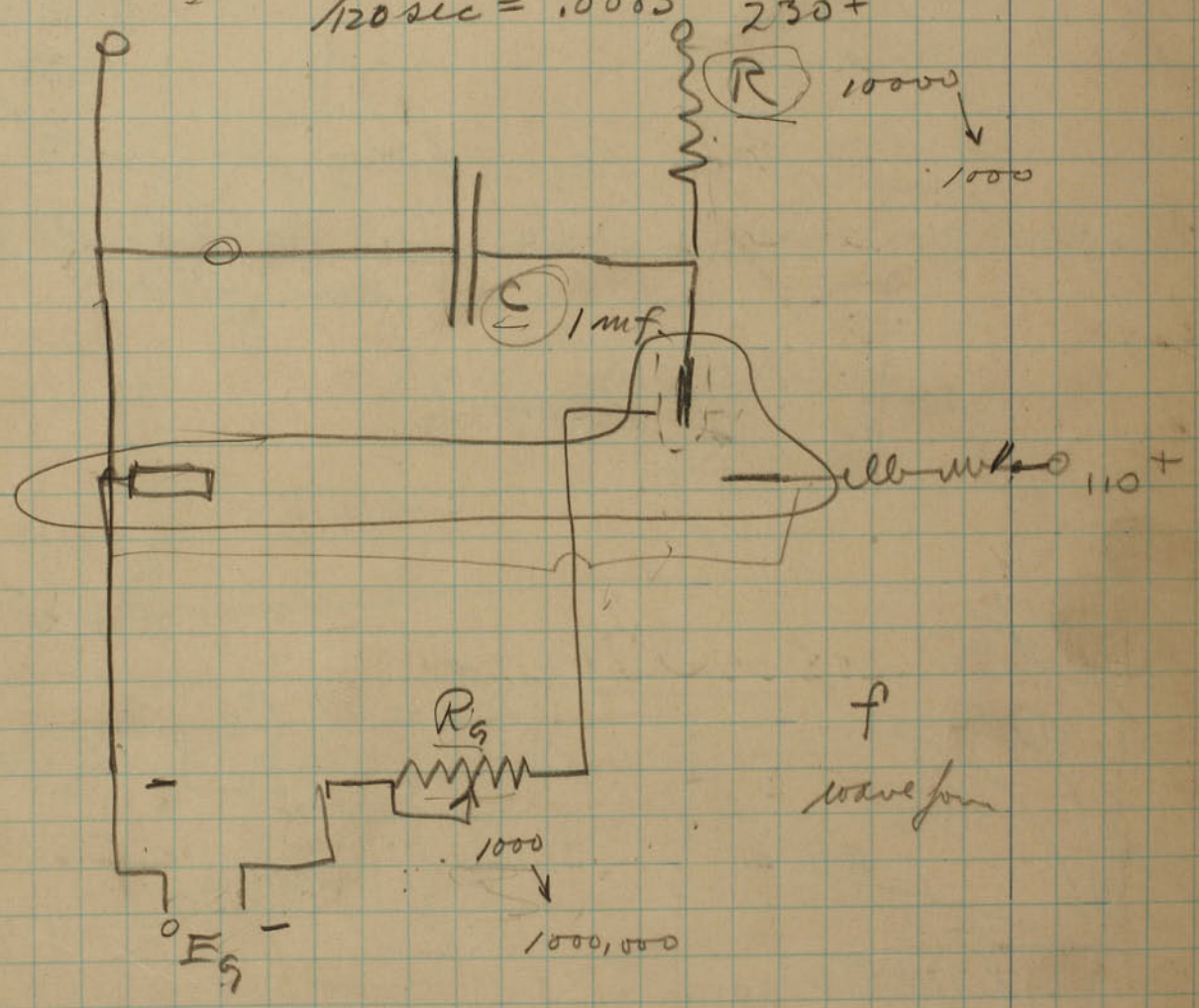




Hollughan's lecture Feb. 11, 1931.

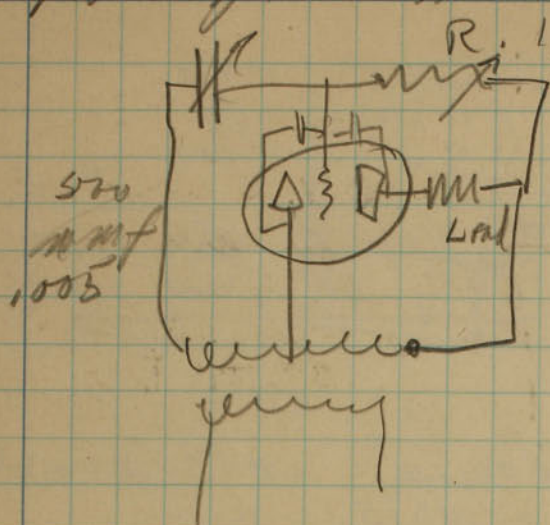


Phase shifter

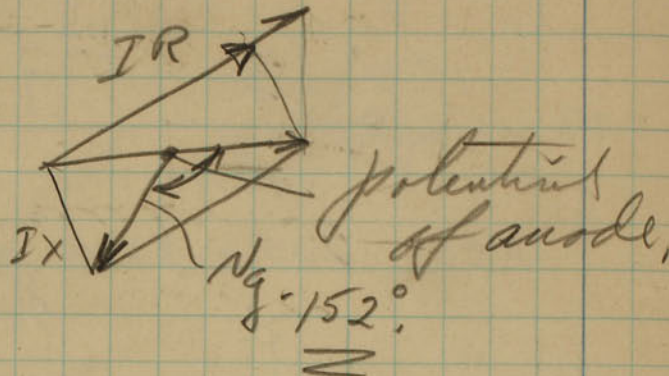

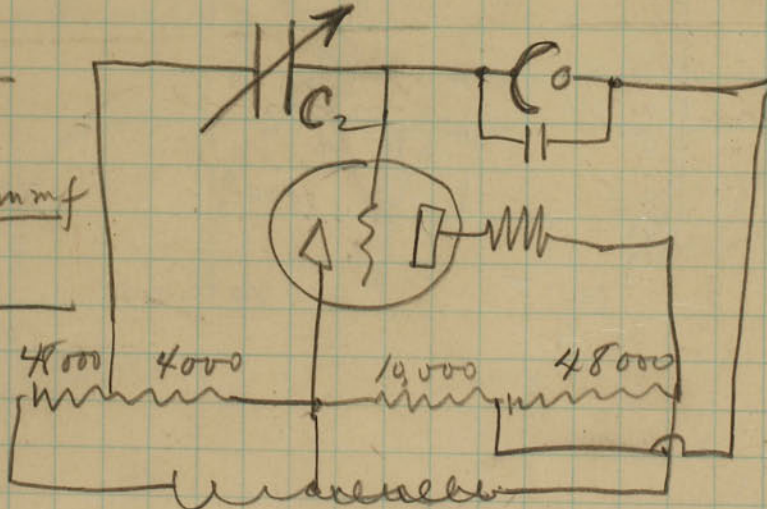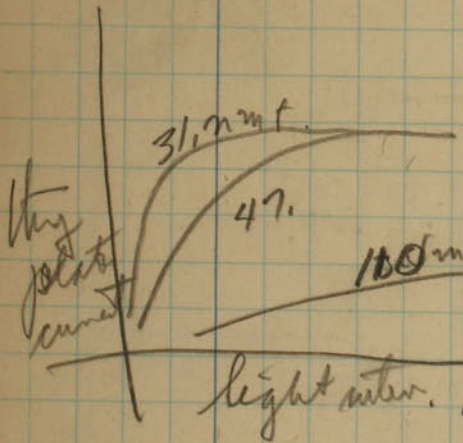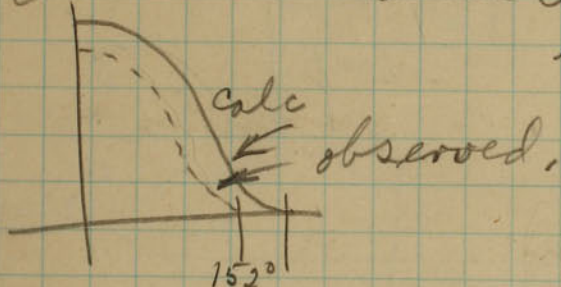1/100 sec time lag in volt-angle curve. Due to buildup of ionization.




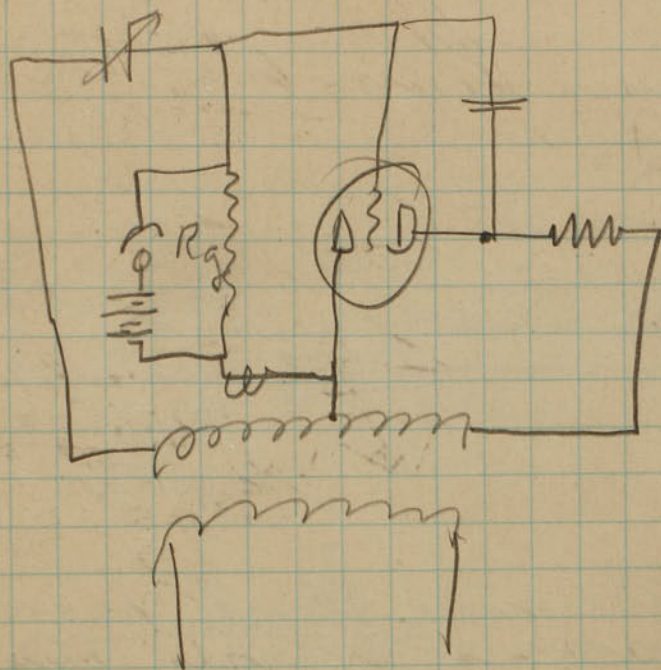Proportional
Arc unit.
Thy. current is function of light.



10×10^{-9} current
in amperes
gives on and
off control
of the thyristor.

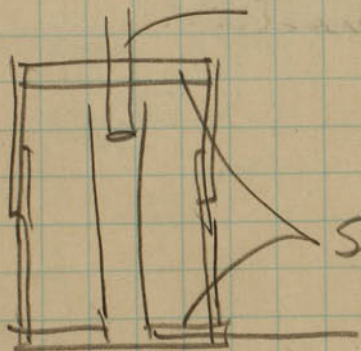Condensers set in sulphur for low leakage,





1×10^{-2} farads, \pm


Sulphur,

10^{-11} amp of photoelectron current
to a 1:1 tube of the G.E. Co.
This is enough current to
control a large thyristor

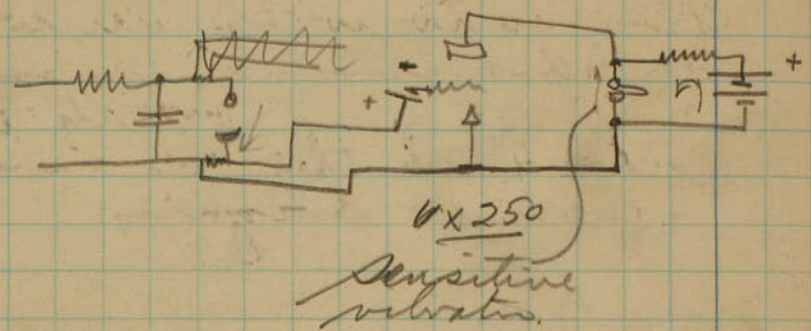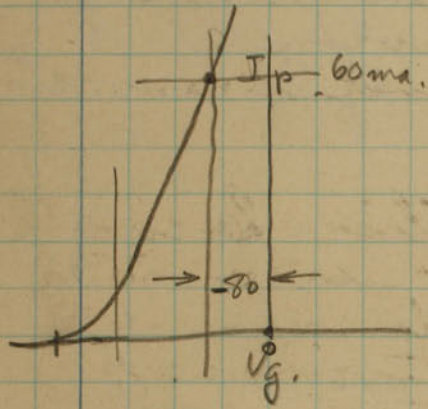Measure of current
 after main discharge
 by means of oscillograph and
 U.F. amplifier. (Suggested by Nottingham)



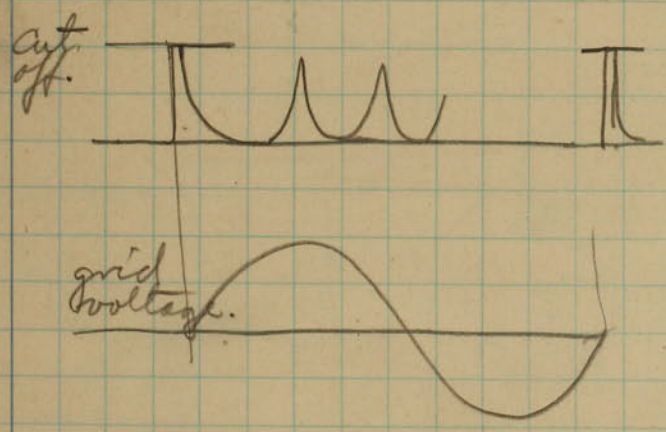
The main flash would
 increase the neg bias
 to cutoff or more. Then
 the rest of the phenomena
 would come through.



Feb 17 1931.
H. E. Rutherford.

One experiment I wish to try is to wrap the wire carrying the discharge around the tube. I think this will speed up the discharge and possibly make it brighter.

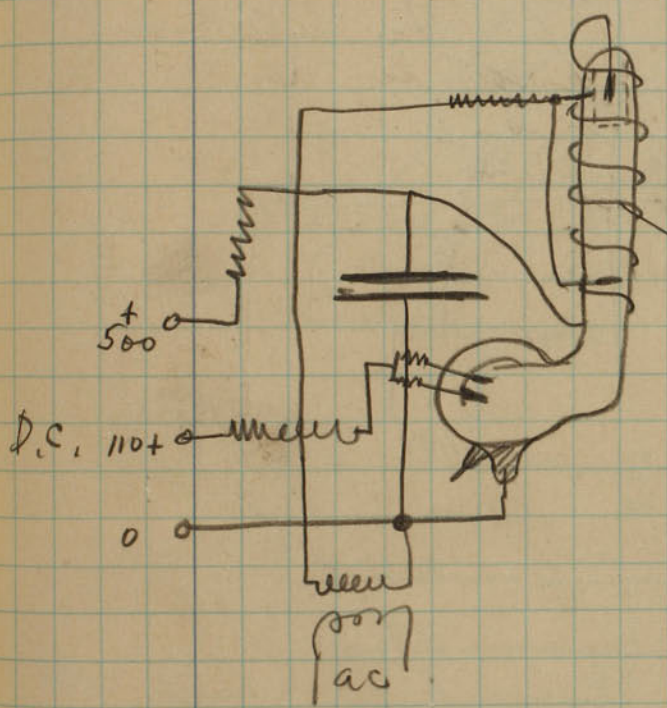
William Gray and I exhausted the special stroboscopic tube last night.



wire wrapped around the positive column to make the flash more intense and quicker?

Mar. 2, 1931

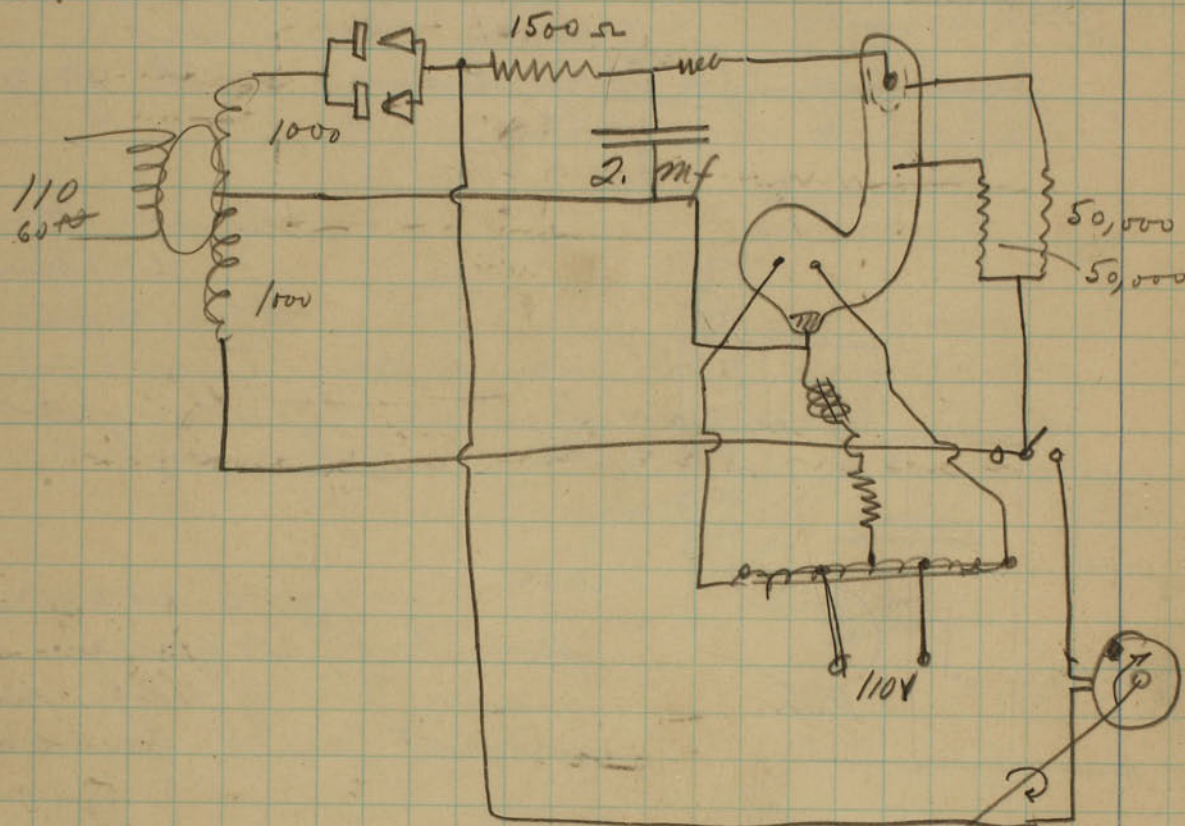
The demonstration at the hotel Statler for the M. I. T. Alumni went off fine last Saturday night. I had the stroboscope on all a.c. and it worked fine.




Driven by a variable speed motor

Mar 9, 1931.

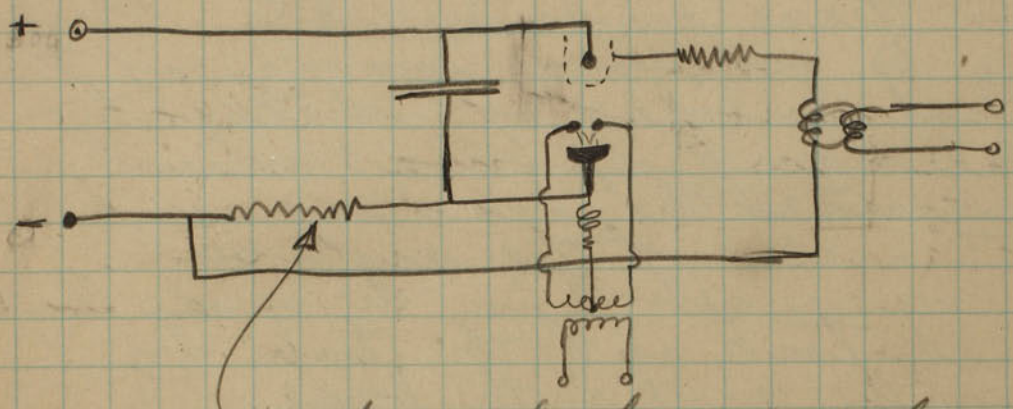
Methods of eliminating
ghosts that trail the main
discharge.



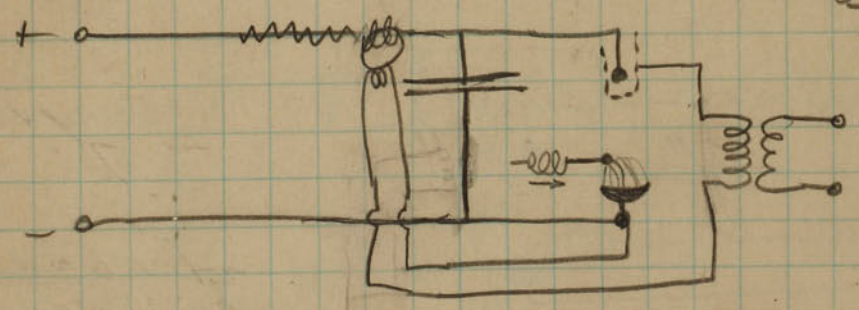The drop through this resistor
acts as a bias on the grid circuit.



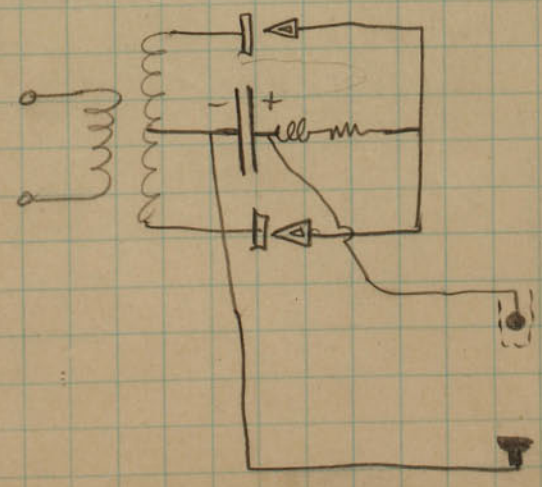
In this circuit
the charging
current
gives a neg.
bias to the
grid.




Mar. 15, 1931

On last Saturday I connected up the stroboscope to take some movies of the vibrating molecule of benzene which Prof. Andrews of Johns Hopkins had ~~had~~ at Harvard. Reissner helped me in these experiments. We were trying to get some movies of the critical modes of oscillation the balls and springs which represented the masses and distances of the molecule. There was a short in the anode lead and it took out the tube by cracking the seal in the base.

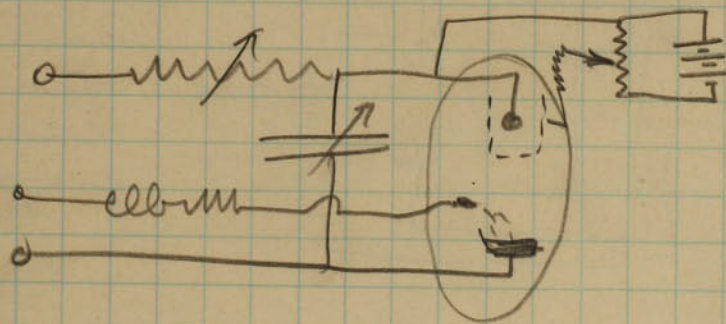
Scheme showed to Reissner to make a tube oscillate. This thyatron had a grid with a large spacing and it was very hard to control.



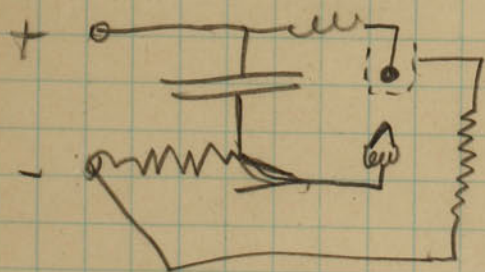Controlled grid
of thyatron
and bias
by means of
a battery.




Oscillator.

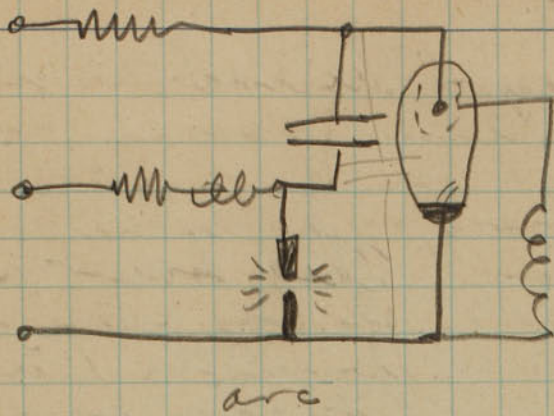


Thyristor as a
switching arrangement
for an arc

March 30, 1931.


Stroboscope for the lab.



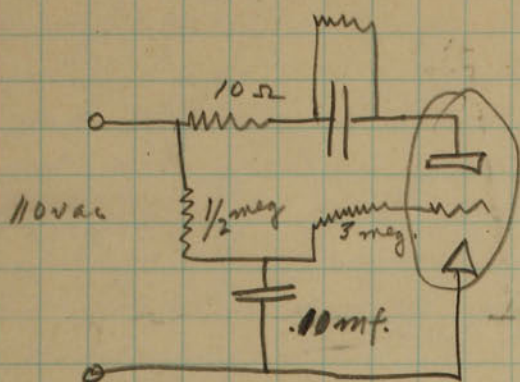


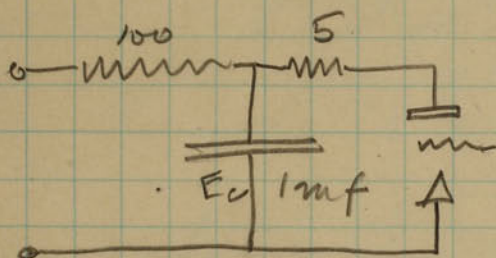This draws a large current from the line to charge the condenser and the current gives light as it passes through the tubes.




1000 2000
2000 110.00
05 amper
5 volts

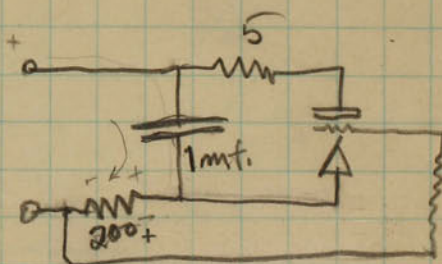



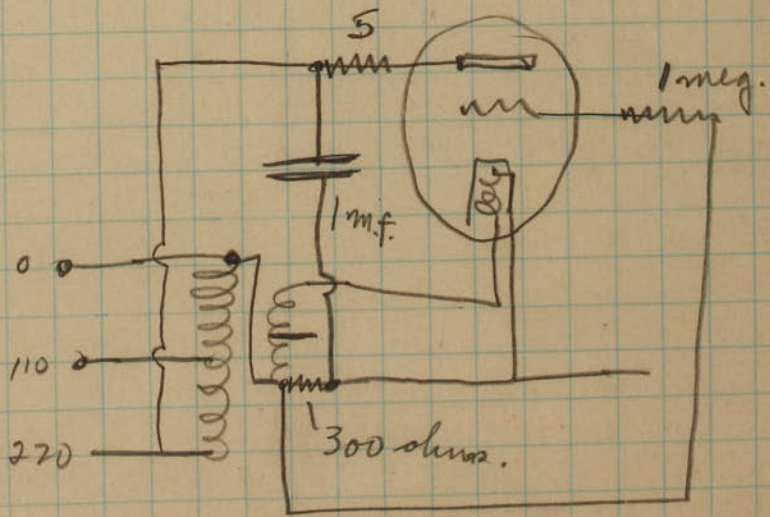
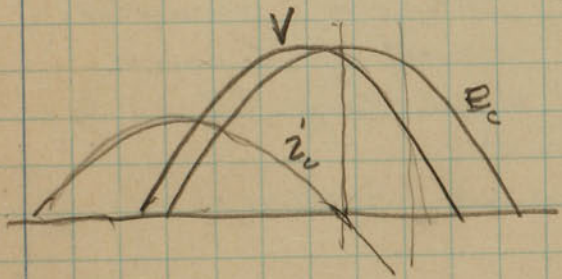
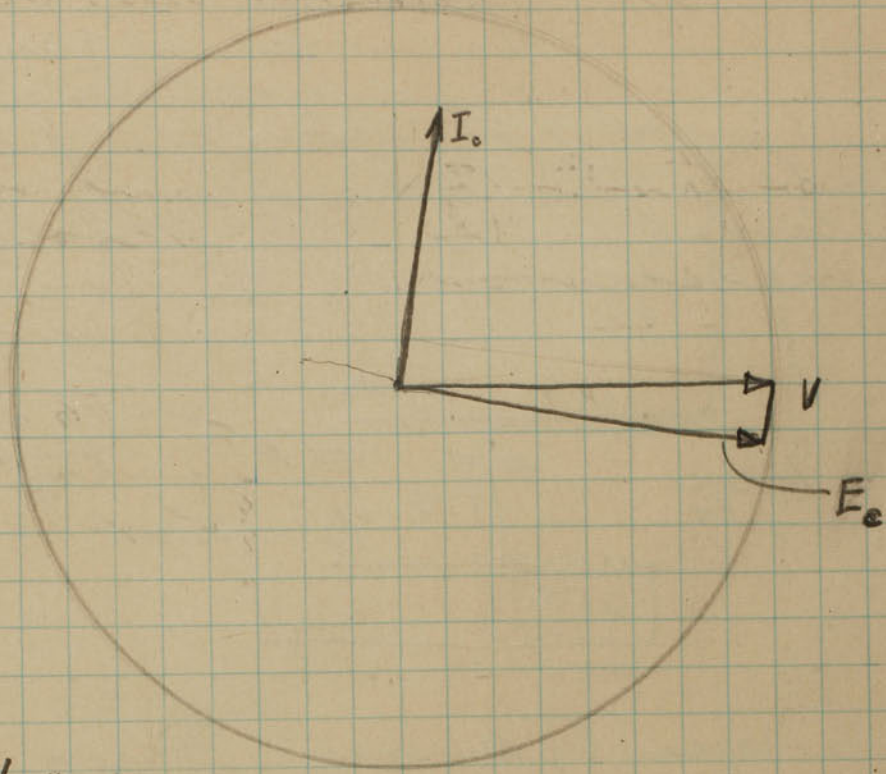


April 1, 1931
H. G. G. G. G.

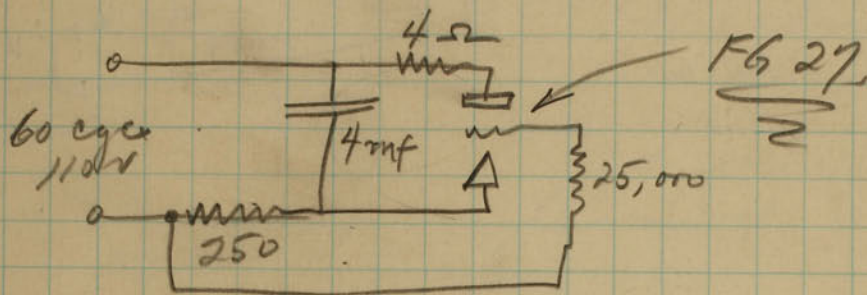This scheme shown on the preceding pages gives a very convenient stroboscope. In the lab tests today and yesterday I ended with the following arrangement.




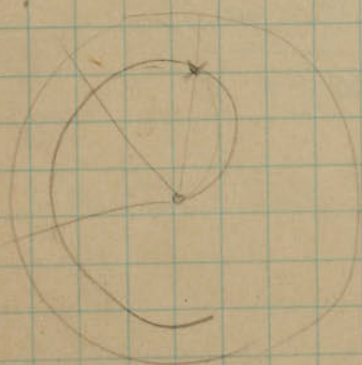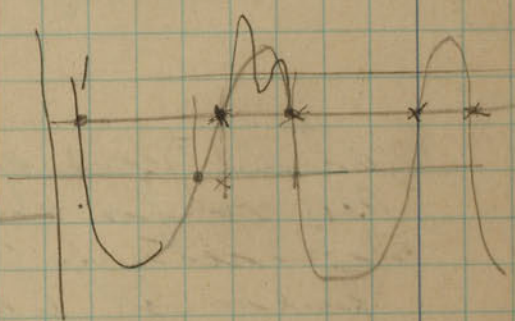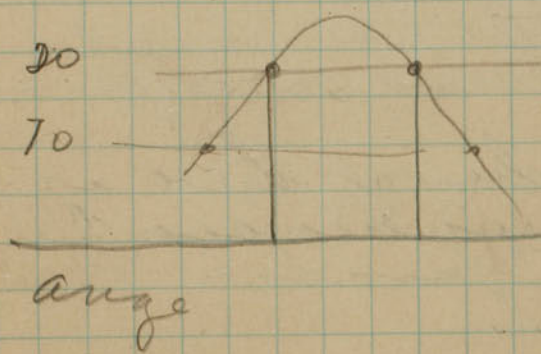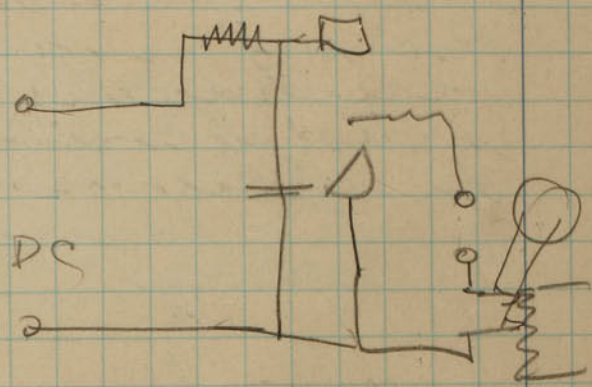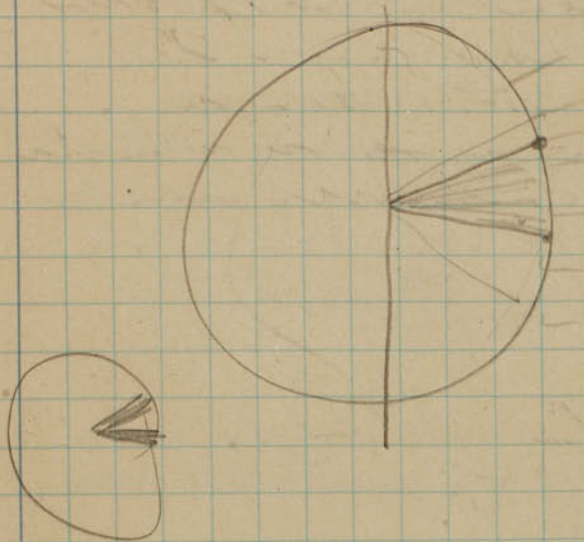It was seen by Amey, Gager, Dawes Lane, Bitchard, Outh, and others. I am planning to put one together permanently for the lab. Tucker and Henty saw it. Rose also.



April 16 1931

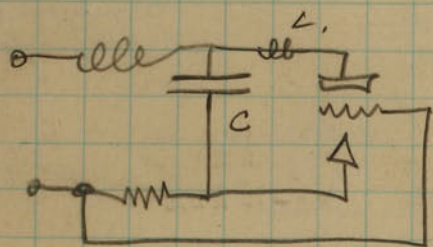
The efficiency of the circuit on page 100 can be improved by using an inductance in the discharge circuit instead of a resistance. also an ~~series~~ inductance in the charging circuit will make the voltage across the condenser greater as well as improve the efficiency.



Calculation to give size of inductance.

The current through the tube should not exceed 25 amperes.

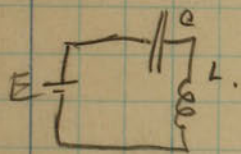at the time of discharge there is 150 volts on the condenser. The capacity is 6.0×10^{-6} farads in the present hookup.



$$EI = (Lp + \frac{1}{Cp}) i'$$

$$i = \frac{EI}{Lp + \frac{1}{Cp}} = \frac{Ecp I}{Lcp + 1} = \frac{E(p I)}{L(p^2 + \frac{1}{cL})}$$

We know from operational calc. that

$$\frac{p}{p^2 + \frac{1}{cL}} I = \frac{\sin \omega t}{\omega}$$

therefore

$$i' = \frac{E}{L} \frac{1}{\sqrt{\frac{1}{Lc}}} \sin \omega t$$

The max current occurs when $\sin \omega t = 1$

$$i'_{\max} = \frac{E}{L} \sqrt{\frac{c}{L}} \text{ amperes.}$$

with $E = 150 \text{ v}$
 $C = 6. \times 10^{-6} \text{ farad}$
 $i_{\text{max}} = 25 \text{ amp.}$

Solve for L .

$$L i^2 = \frac{E^2 C}{2}$$

$$L = \frac{E^2 C}{i^2}$$

$$L = \frac{150^2 \cdot 6.0 \times 10^{-6}}{25^2} = 0.00215 = 0.215 \text{ mh.}$$

The discharge frequency.

$$f = \frac{\omega}{2\pi} = \frac{1}{\sqrt{LC} \cdot 2\pi} = \frac{1 \cdot 10^6}{2\pi \sqrt{215 \times 6.0}} = \frac{10^6}{2\pi \cdot 36} = \frac{10^6}{226} = 4500 \text{ cyc/sec.}$$


April 18 1931
 J. S. Edgerton

When in Schenectady yesterday I disclosed to Mr. P. F. Alger and Mr. Rich the stroboscopic switching scheme shown on page 78 and 79 of this book.

I plan to write them a letter giving the details of the scheme showing how it can be accomplished.


When riding from the plant with Mr. Alger and Mr. Emmet there was discussion by Mr. Emmet regarding the electrical drive of the large battleships. He was interested mainly in the torques that are necessary to reverse the propellers.

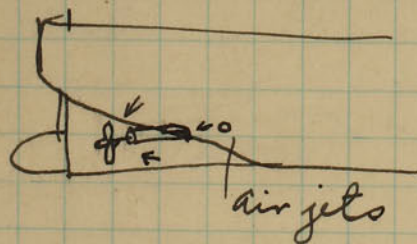It occurred to me that the propellers might be reversed more easily if compressed air was blown into the water ahead of them so that it struck the propeller. This might help the propeller break ^{through} into turbulence so that it could reverse more easily.




Apr. 29 1931
H. E. Edgerton.

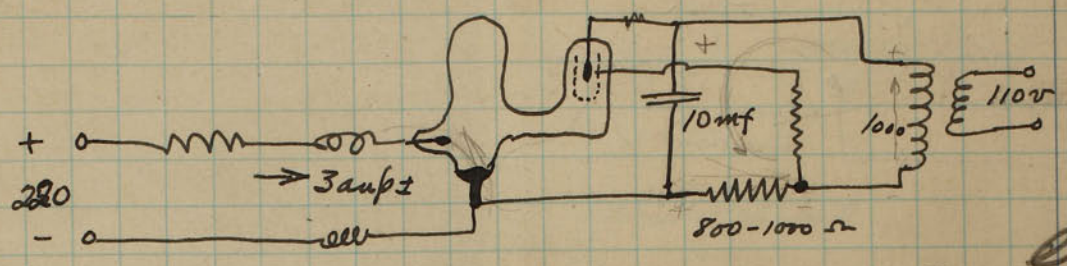Circuit for Stroboscopic observation of 160 HP motor in Dynamo Lab.



April 29 (Wednesday) 1931
E. L. Bowler


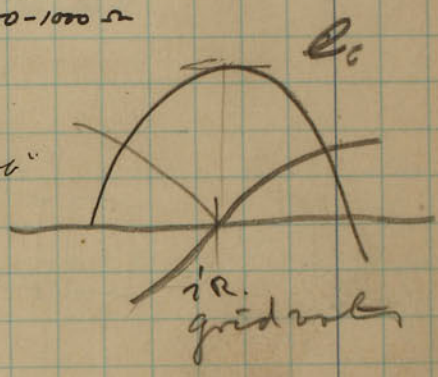
Witnessed actual operation
of this circuit in "dynamo-lab"
W. D.



After seeing the above circuit work Bowler and I went over to the Engine Lab. and saw the indicator that Draper and Taylor set up. This used a circuit that I showed Drope several months ago which discharges a condenser through a spark coil. The circuit is actuated by a grid contact made by a pressure membrane inside the cylinder. The thyatron circuit regains control because of action of the parallel condenser across the tube.

May 4/1931

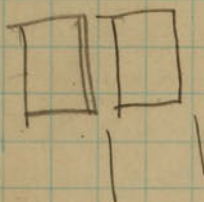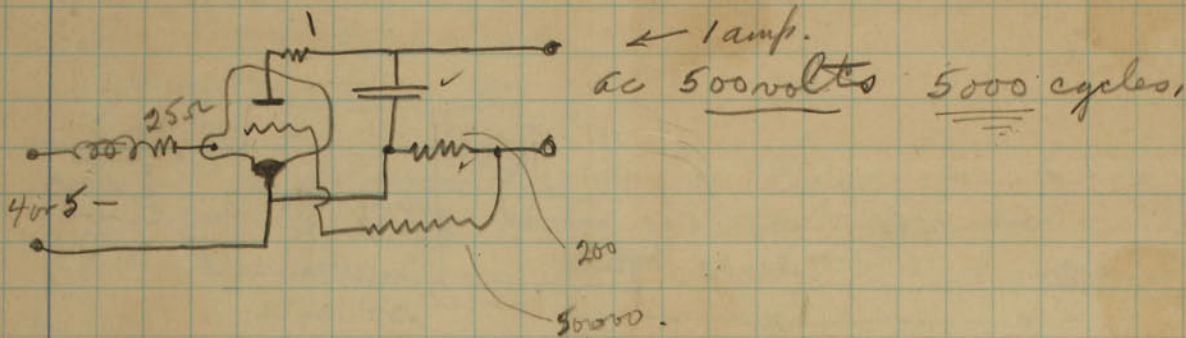Talked with Draper about photographing jet of vapor.



$\frac{1}{5000}$ sec to mov. 8mm.

1 sec


$$8 \times 50000 = \frac{40,000 \text{ mm}}{25} =$$

1500 in sec.

100 ft sec.


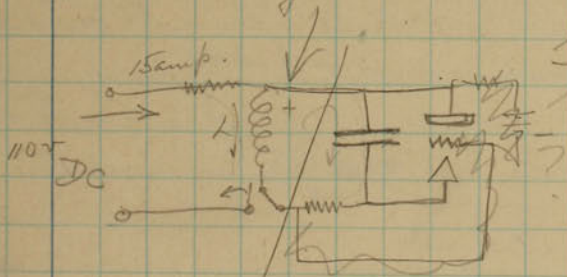
1.9 lens.

Scheme from Dr. Bush. which came up when talking with Draper. Choke to store the energy for a series of flashes. The freq. will be const and the light const.






May

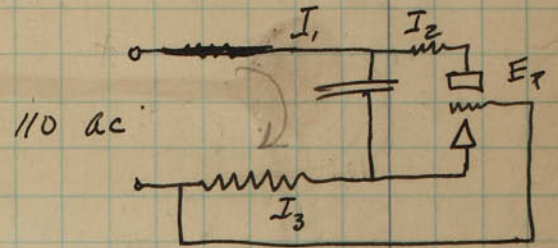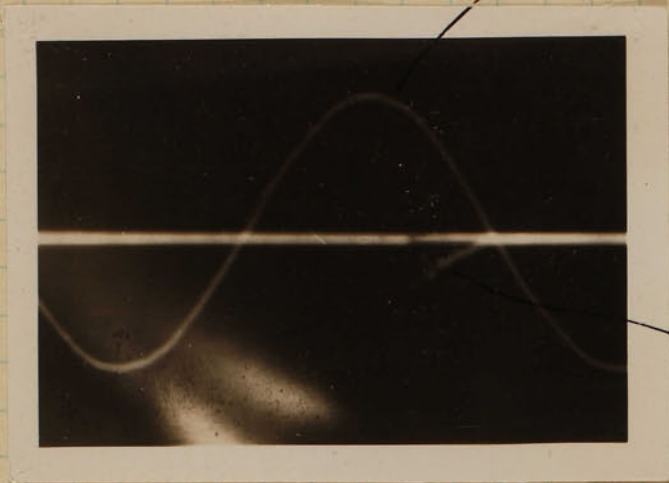These were taken by two junior
Wagner and



discharge current
 I_2

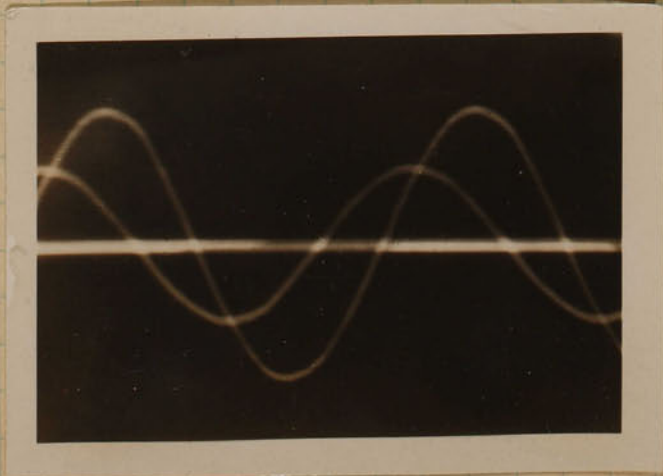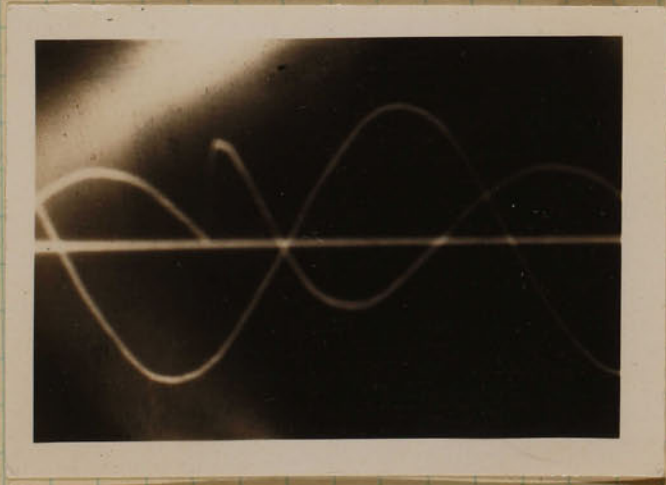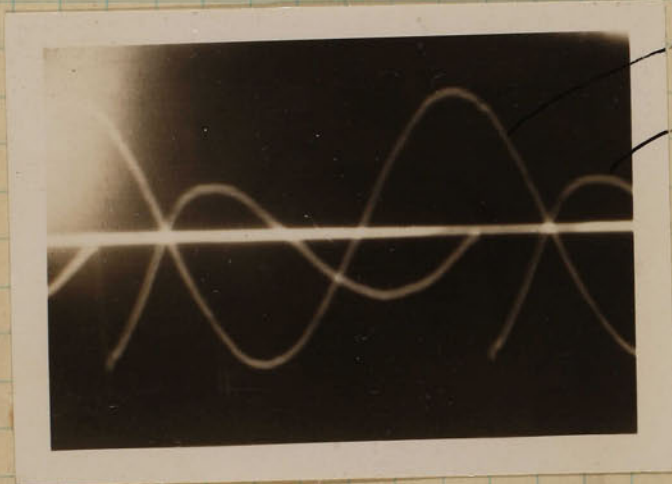

Notebook Number: T-1

Scanning and Separation Record


1 unmounted photograph(s)

 negative strip(s)

 unmounted page(s)
(notes, drawings, letters ...)


was/were scanned ^{in place on page} ~~where originally located~~ between page
108 and .

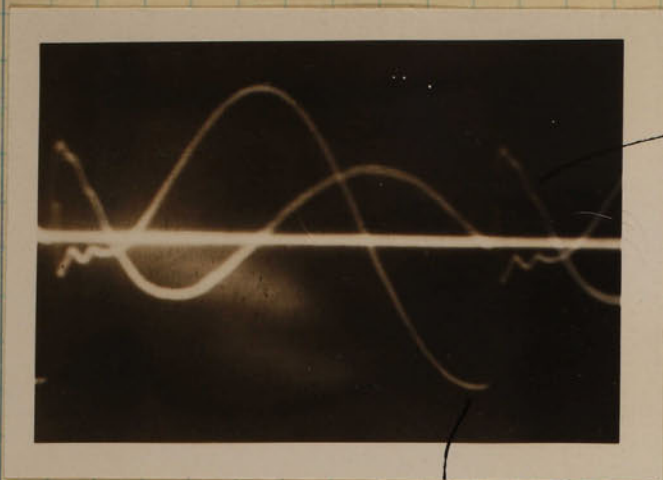Item now housed in accompanying folder in MC 25, box 166



charging current or
grid voltage.

voltage E_p (anode to cathode).

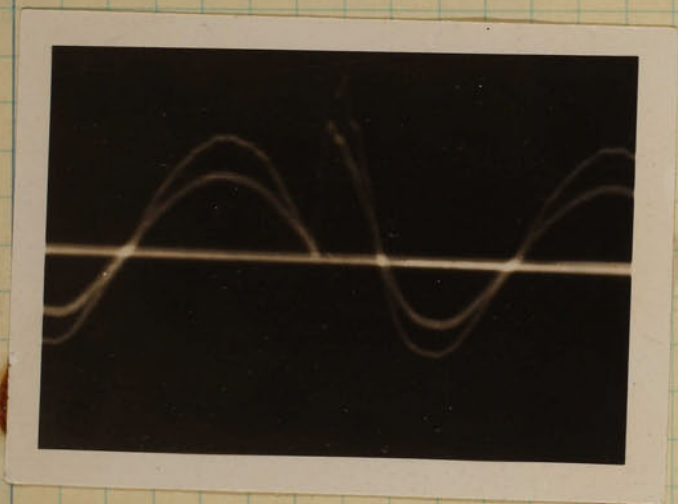

Stroboscopic Moving Pictures

By means of moving pictures taken stroboscopically it is possible to see the rotor of a synchronous machine just as though one were actually revolving at synchronous speed with the rotating field of the stator windings. Newly developed thyatron tubes provide sufficient light for taking the pictures.

By H. E. Edgerton

Associate A. I. E. E.

Massachusetts Institute of Technology
Cambridge

OF THE SEVERAL different methods of determining the very important, but rarely measured angular displacement of a synchronous machine, stroboscopic observation is the most direct and straightforward. This method requires a minimum of apparatus; namely, a disk rigidly attached to the shaft of the synchronous machine, a suitable stationary scale for recording the displacement, and an intermittent light source operating in time phase with the terminal voltage of the machine. The disadvantage of the stroboscopic method in the past has been that the measurements had to be recorded visually, and thus the accurate measurement of transient variations of angle has been practically impossible because of the inability of an observer to record the phenomena during the short duration of most transients.

With the stroboscopic device described in this article, enough light is produced so that a motion-picture record can be made of the angular displacement of a synchronous machine. A mercury vapor arc is used which produces the characteristic blue light well known for its powerful actinic properties. The tube used to produce the arc is a thyatron containing grids that control the electrical transients which are the source of the stroboscopic light.

Stroboscopic moving picture records will provide important observations for those who are concerned with the operation of synchronous machines. These moving pictures will be especially valuable when correlated with oscillograms taken simultaneously. The "strobograms," as these pictures may be called, will furnish power engineers with information regarding the angular displacements of their generators, con-

densers, and lines during switching and short-circuit disturbances. They will tell the users and designers of synchronous motors exactly how far the rotors swing, their period of motion, and the damping of their oscillations for violent, sudden load changes such as are common in the steel industry. Photographic records will be valuable also in studying the steady-state time-angle variations.

In addition this method of photographing stroboscopically illuminated objects will provide research workers with the means whereby many experimental investigations may be made. It is especially adapted for studying the motion of mechanical objects such as springs, cams, valves, and other devices.

Among the important requirements for a stroboscope suitable for photographic purposes, are:

1. Short duration of the light. If the illumination extends over an appreciable period of time the image will be blurred. A rough calculation shows that the duration of the main flash should not be longer than about 10 microseconds.
2. Rich actinic light. Photographic film is much more sensitive to ultra-violet and blue light than to red. For this reason a mercury discharge tube is used in place of the commonly used neon tube. The light from a mercury arc is composed of strong blue and ultra-violet colors. Some of the ultra-violet radiations are, however, absorbed by the glass walls of the tube.
3. Reliability of light-flash control. A synchronously rotating object viewed by a stroboscope will not be stationary if there is any variation in the interval of time between discharges in the stroboscope circuit. This time interval can be controlled very accurately by applying sufficient voltage to the thyatron grid.

THYRATRON CIRCUIT

An arrangement of apparatus capable of producing a powerful stroboscopic light is shown in Fig. 1. Current waves for various branches of the circuit are included also in this illustration. Light is obtained from a condenser discharge through the thyatron tube; and since the only impedance in the circuit besides the thyatron is that of the leads connecting the tube to the condenser this discharge is very rapid, lasting only about 10 microseconds or even less. An intense momentary light flash is thus obtained.

The sequence of events through a cycle of operation will be described in detail. When the grid is negative no current is flowing from the main anode because the grid has the property of extinguishing the arc. Such grid action is contrary to the usually explained rules of thyatron operation but occurs here because of the low density of the anode current and the large condenser

207
000

57/h
=

ro mf.

S.M.R.E.

June 31

in parallel with the arc. During this half cycle, current flows from the 500-volt d-c. source through the resistance into the condenser in the well-known exponential relationship. The resistance and capacity are adjusted so that the potential across the condenser becomes practically 500 volts during the half cycle that the grid is negative. Replacing the resistance R with inductance L , or using both in series with the condenser, will give a still higher voltage across the condenser, if R , L , and C have proper values.

At the end of the charging half cycle, the grid becomes sufficiently positive to allow current to flow from the anode. The charge that has been accumulated in the condenser will then be discharged through the tube. If short, heavy-stranded leads are used to connect the condenser to the tube the holding arc may be extinguished at this time by the condenser discharge, but this difficulty may be overcome by introducing a choke coil into the holding circuit and a small resistance in series with the condenser. From a recent study by Krug, (of the arc striking speed of a mercury arc rectifier), (*Arch. f. Techn. Physik* 11, 1930, 6 p. 227, and *E. u. M.* 48, June 8, 1930, p. 567), it is known that only 0.01 to 0.1 microsecond is required to start the arc. Thus the thyatron acts virtually as a short circuit across the condenser.

For the remainder of the half cycle following the condenser discharge the grid is positive and the main anode carries a current which is limited in value by the resistance R . The light from this current is not intense and is negligible in comparison with the condenser flash. With the pool-type of thyatron this current is oscillatory under some conditions, giving faint ghosts trailing behind the main discharge. A negative bias and a peaked a-c. voltage on the grid eliminates these oscillations.

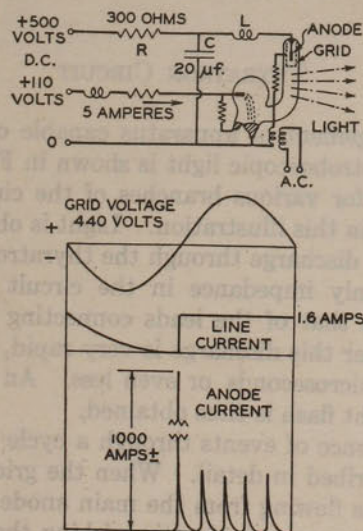


Fig. 1. Schematic diagram of thyatron circuit; voltage and current relations in various parts of the circuit are shown below

At the completion of the operating cycle the grid again becomes negative thereby extinguishing the anode current. The condenser then begins to accumulate a charge for the next flash.

STROBOGRAMS TAKEN

With the thyatron and other apparatus just described, a 160-hp. synchronous motor was photographed stroboscopically as it pulled into step. The tube was hung on a framework so that its light would fall directly upon the field structure. White cardboard collars were tied around the poles and alternately marked "N" and "S." The amortisseur rings were painted white and the protruding bars black. A general view of the arrangement in operation is shown in Fig. 2.

Strobograms taken during the transfer from operation on half voltage, which was used for starting the motor, to full voltage, are shown in Fig. 3. These consist of a sequence of enlarged, 16-mm. moving picture frames and were taken on panchromatic film at 16 frames per sec. with a lens opening of f-1.9.

The particular thyatron used for these tests had two anodes, each was connected to a circuit such as shown in Fig. 1 but the grids were supplied from a common transformer. No apparent difference in the

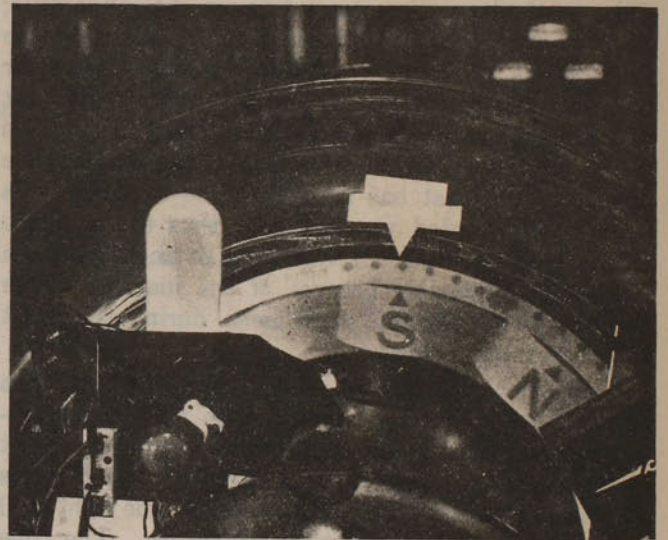


Fig. 2. Thyatron arranged for taking stroboscopic movies of a 160-hp. synchronous motor

time of discharge was experienced, except when the tube was cold.

A special camera which would record the rotor displacement angle for each cycle could easily be made. This camera would require no shutter and no mechanical framing movement. The film could be run through

the camera at a constant speed and just fast enough so that the exposures would be spaced correctly.

A simultaneous reading of time could also be taken with the angle on the strobograms by photographing a clock hand driven by a telechron clock motor running

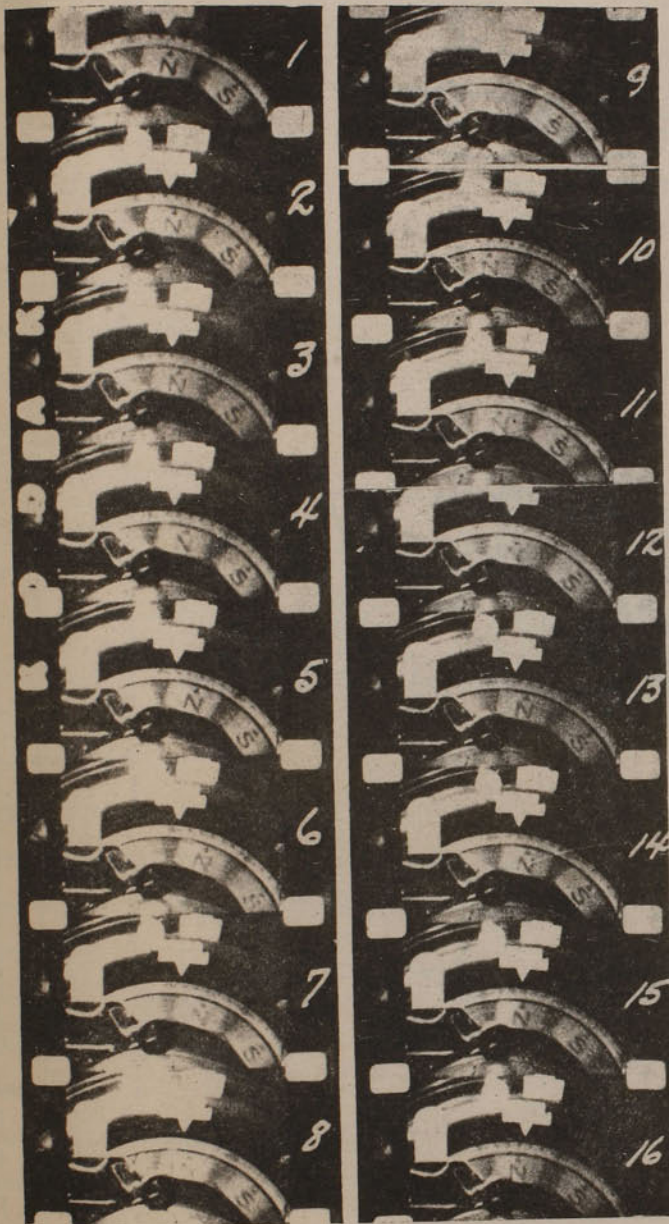


Fig. 3. "Strobograms" of a synchronous motor as it was switched from half to full voltage. Increased angular displacement may be noted as the supply switch was momentarily open during changeover (4-7)

at one revolution per second. This would be quite necessary for accurate testing since there is no definite relation between the frequency of the camera shutter and that of the intermittent light.

May 1931

008
000

07/16
Z

70 mf.

This is a reprint from

Electrical Engineering


Published monthly by the
American Institute of Electrical Engineers
33 West 39th St., New York, N. Y.

M
D
m

32

2

May 21


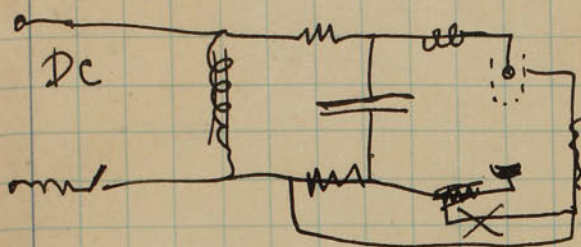


won't work?

$$\begin{aligned} \text{Energy} &= \frac{E^2 C}{2} \\ &= \frac{400 \cdot 400 \cdot 40 \times 10^{-6}}{2} \\ &= 3.2 \text{ joules.} \end{aligned}$$

$$\frac{LI^2}{2} = 3.2 \text{ joules. } I = 15 \text{ amp. } L = \frac{3.2 \cdot 2}{15^2} = \frac{0.07}{1.000}$$
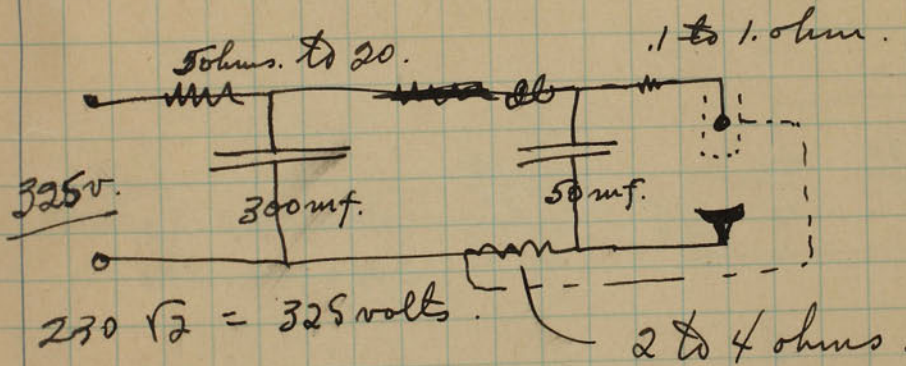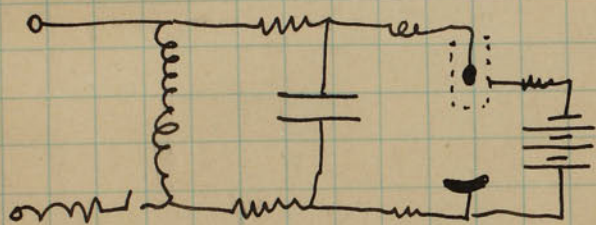
$$L = \frac{3.2}{2 \times 15^2} = \frac{3.2}{2 \times 225} = \frac{0.07}{1.000} \text{ H}$$






$$8 \times 100 = 800 \text{ mf.}$$

May 22, 1931.

Talked to Prof Taylor and to Draper about stroboscopes for photographing jets from a diesel engine.



Other circuits.

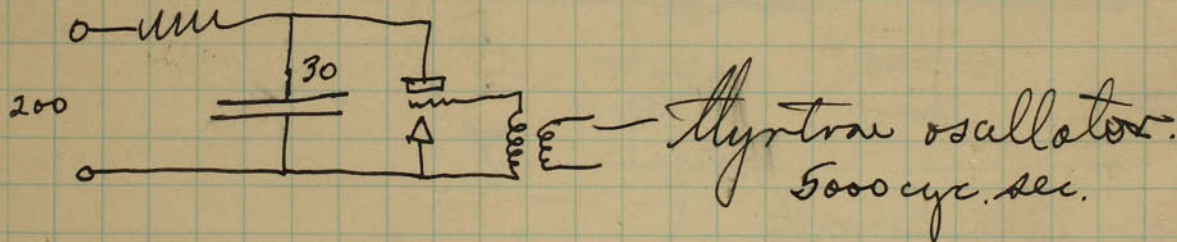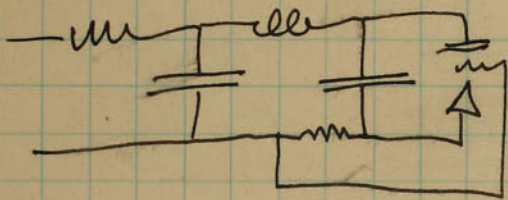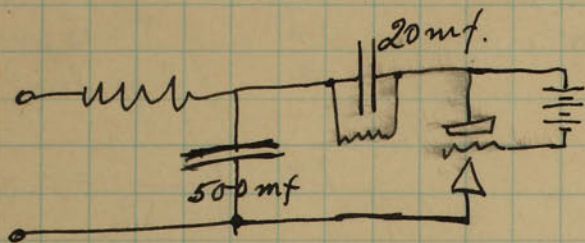

$$RC = \frac{1}{.5000} = 2 \times 10^{-4} = .0002 \text{ seconds.}$$


$$30 \text{ mf. } RC = .0002 = 2 \times 10^{-4}$$
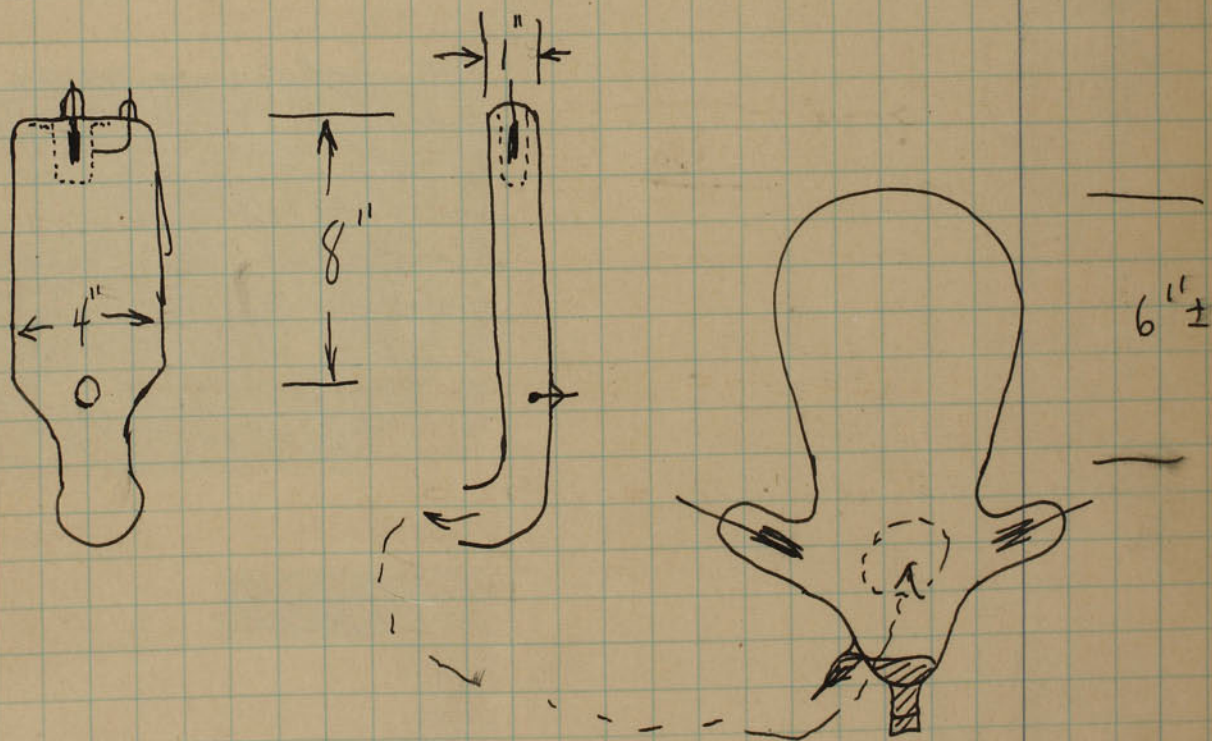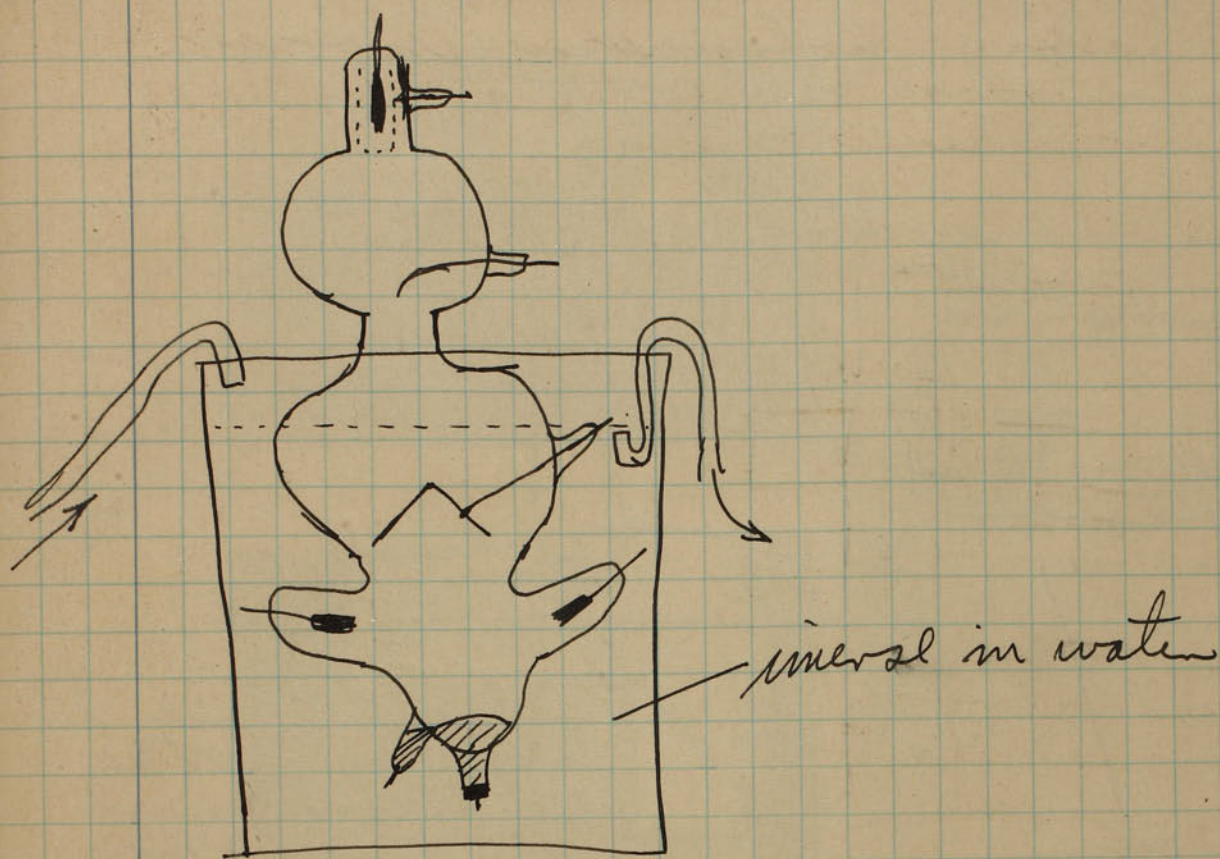
$$R = \frac{2 \times 10^{-4}}{30 \times 10^{-6}} = \frac{10^2}{15} \approx 15 \sqrt{100} \approx 7 \text{ ohms.}$$



May 23 1931
H. E. Edgerton.

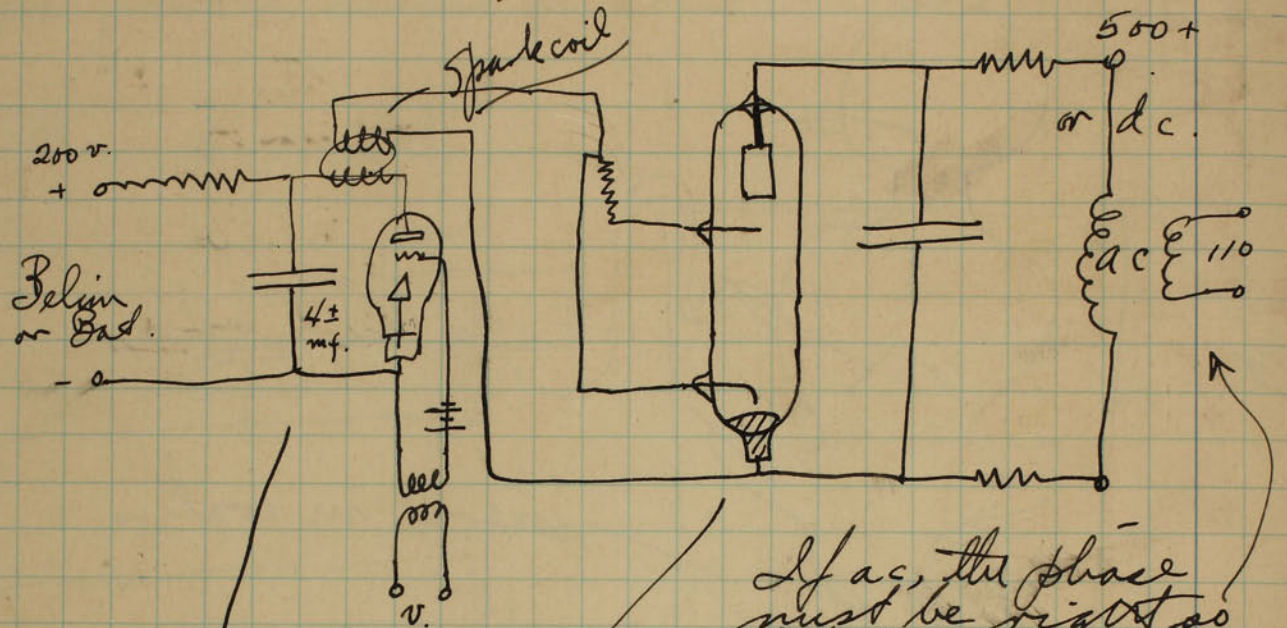High-Power Stroboscope
for Photographic Purposes.
at 60 cycles per sec.



The all ac
circuit can be
used here.

If ac, the phase
must be right so
that the condenser
is charged + for
the flash.




No holding arc is
needed. The discharge
is started by the spark
from the condenser
discharge through the
spark coil.

May 28, 1931.

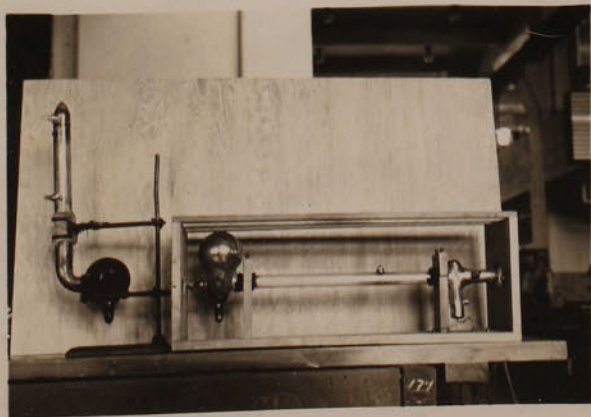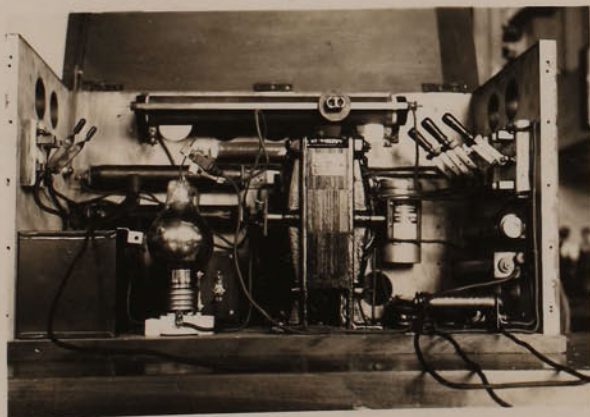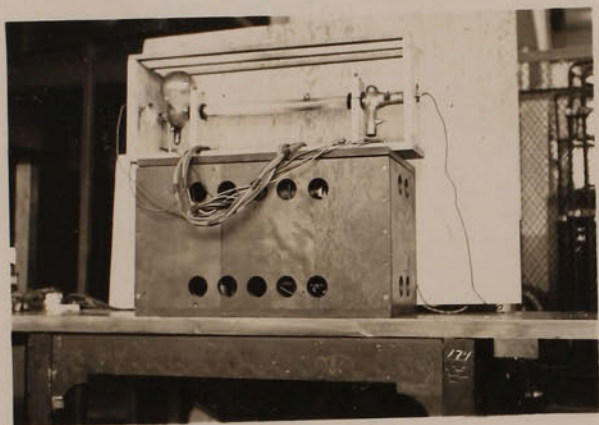H. S. Edger tows
20 sec exposure. of 160 ft meter.


These pictures were
taken by

McClure and Stauder
and were put in
their thesis. 1931.



May 28 1931

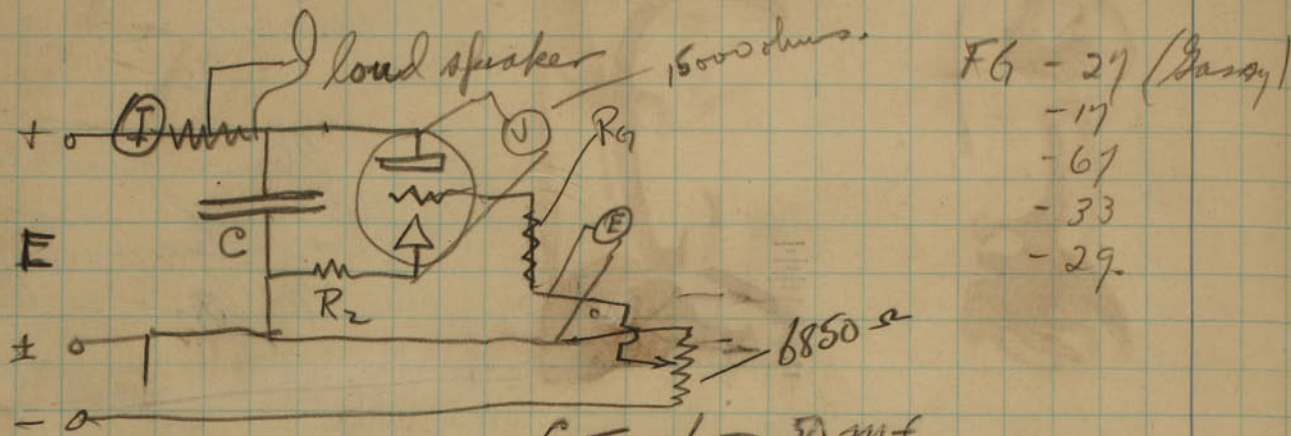Thyatron Osc. Char. with Parallel Condensers.



May 29, 1931

FG-17

C - .1 - 50 muf.
R2 - 4 - 30 ohms
Rg - .01 to 10 megohms.

E	SOCKET temp.	R1	R2	Rg	C	E _{amp}	E _g	E _m	I	freq.
110	61.5	-	7	30,000	.1	13.5	-84	(-4)	.1	-
110					.2		79			
					.3		75			
					.5		85			
					.7		92			osc.?
					.9		100			
	63.0				.1		-92			
					2.2		req more than -112v			
112	63.9	-	7	10,000	.9		-105			
		Cannot find out arc			.1	14.9	-		.2	
	63.				.5		-			
	65.8	-	5	10,000	.3	16.9	-28		0.1	
			5	20,000	.3	"	50		.1	
			5	30,000	.3		77		.1	
			5	40,000	.3		101		.1	
	65.7		5	50,000	.3		more than 112		.1	
			5	10,000	.3		" " 112.		0.2	
			2	10,000	.3		" " 112.		0.2	
			1	10,000	.3		" " "		0.2	
			1	10,000	.3	17.5	112		.06	
			1	10,000	.3	12.7	-16		0.1	
			1	30,000	.3		-40		0.1	
			1	60,000	.3		-80		0.1	
	65.9		1	10,000	.6		-14		0.1	
			1	30,000	.6	13.5	35		.1	
			1	60,000	.6		67		.1	
			1	60,000	.6		-24.5		.175	


Nothing of particular importance.
 By load speaker
 any gas from bottom of grid.

→ unstable. →

$R_2 = 4 \text{ ohm.}$


Expected Results.
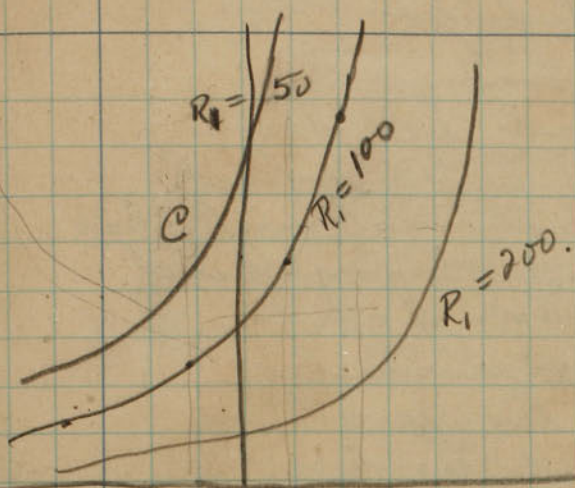
$$\frac{\frac{4V}{25}}{\frac{1.9 \text{ w}}{4000}} = .05 \text{ ma.}$$



Eg.

E	Z	R ₂	R _G	C	E _{drop}	E _g	E _{out}	I	Remarks.	I _g
112	93.2	1	10,000	.3	14.	112	much less	0.10	did not go out.	T
				.3		-40		.08		
				.6		-40		.08		
				.9		-76		.08		
				.9		-48		.10		
71	1	10,000		.99-3.1		-112		.20	oscillates	
		20,000		"		"		.20	does not ..	
69.3	1	9,990		.99		-45		.10		.05 ma.
		8,990		.99		40		.10		
		7,990		.99		36		.10		
		5,000		.39		12		.10		
		"		.39		112+		.15	did not go out	
		"		.99		25		.12		
69.1		9,000		.99		44		.12		

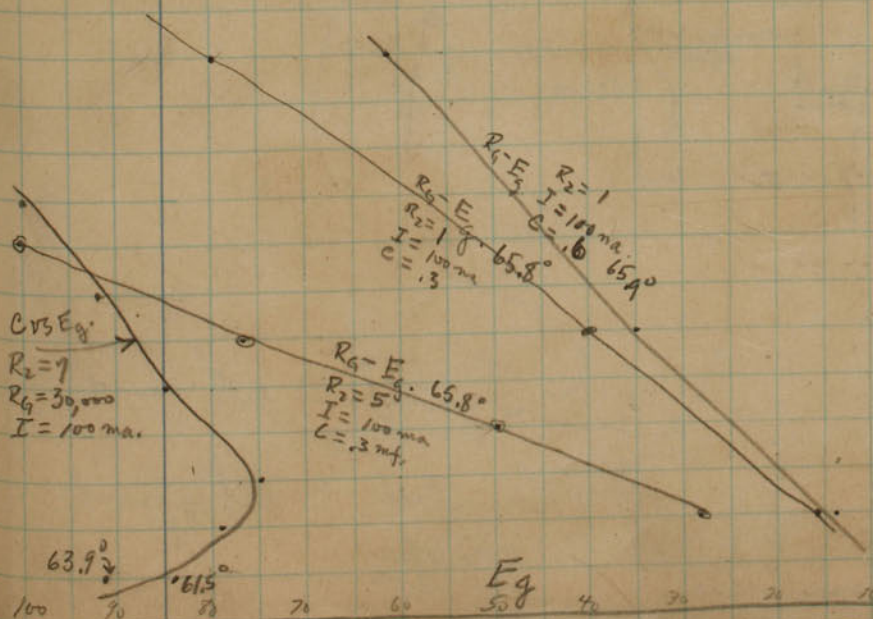



- C
- mf.
- 2.1
- 1.6 5R_G
- .9
- .8 40,000
- .7
- .6 30,000
- .5
- .4 20,000
- .3
- .2 10,000
- .1
- 0

These tests to be repeated with the spark coil in the secondary circuit.

May 28 1931
H. S. Denton

Indicator - Card Apparatus.

Draper of the engine lab. has been using a circuit I showed him which allows a very small electrical impulse to control considerable energy and make a record on carbon paper. He has experienced considerable trouble because of the temperature of the tube. The device only works over a definite range of temperatures which is rather small. I showed him some circuit on May 22 which I hope will overcome this difficulty.

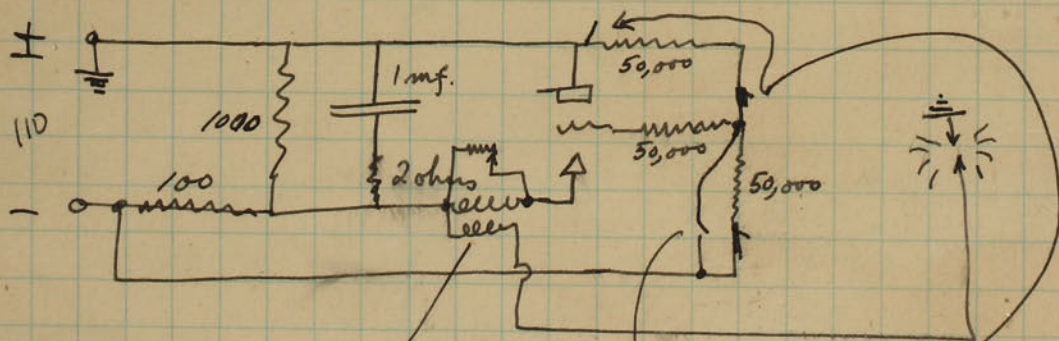
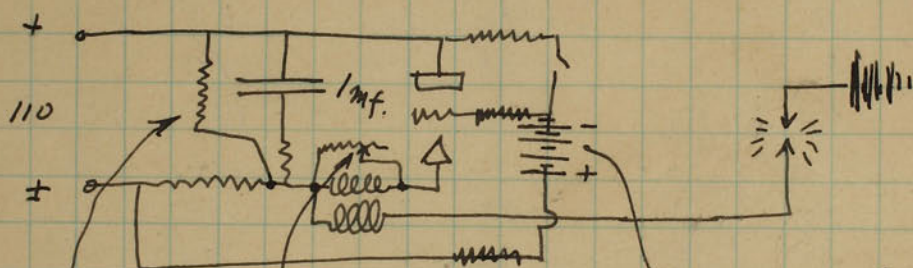


Switch to get spark
on close.
Switch to get spark
on open

May 29, 1931.
 H. S. Skipton

Stroboscope.

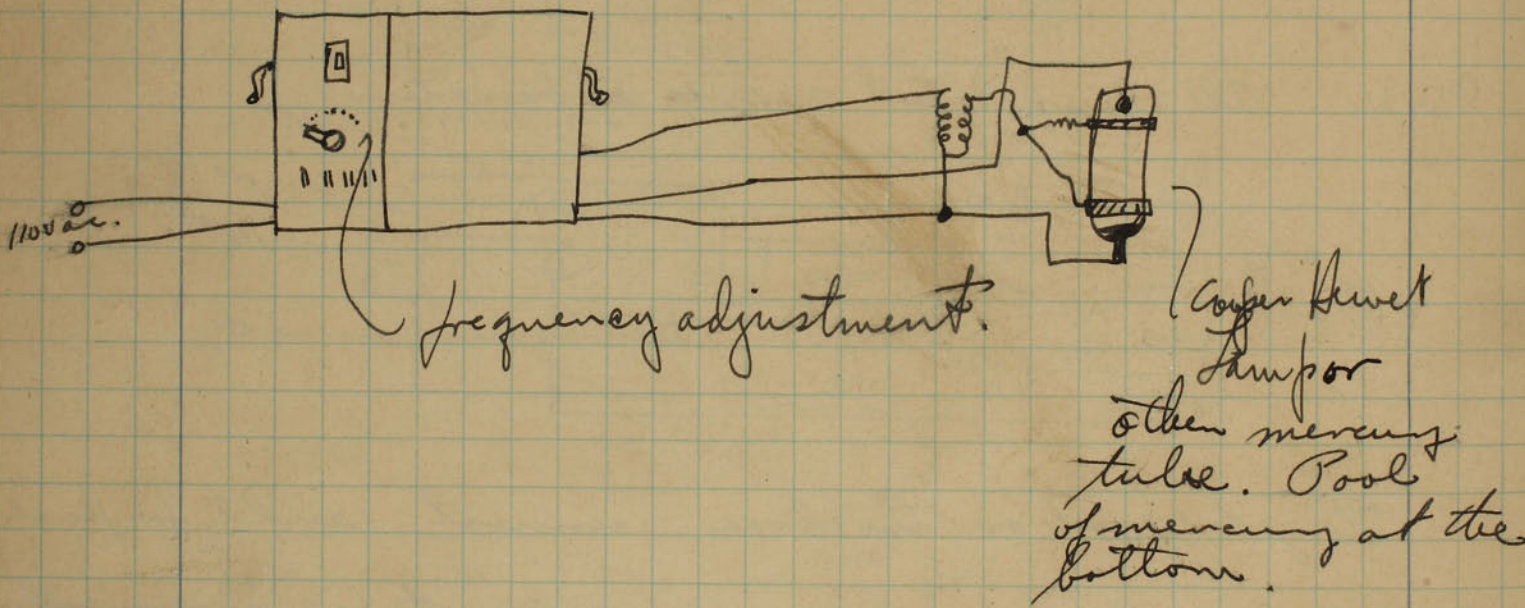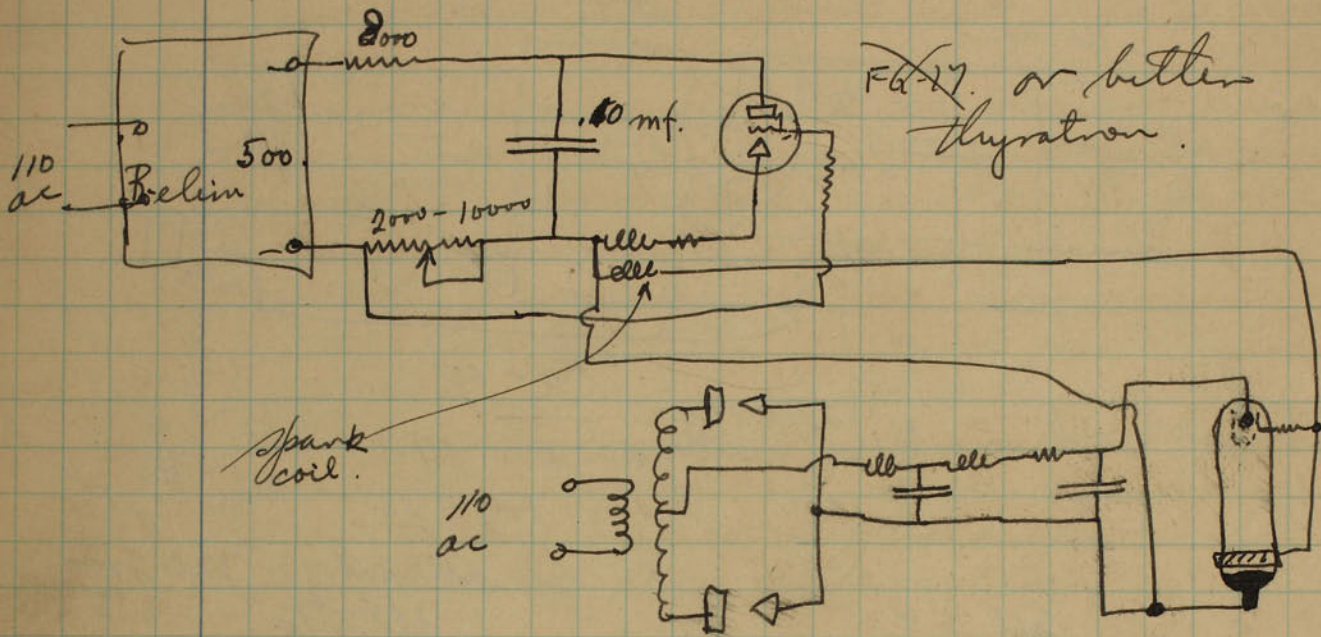
Also see notebook 3. on synchronous machines



Stroboscope


May 31 1931
H. S. Egerton

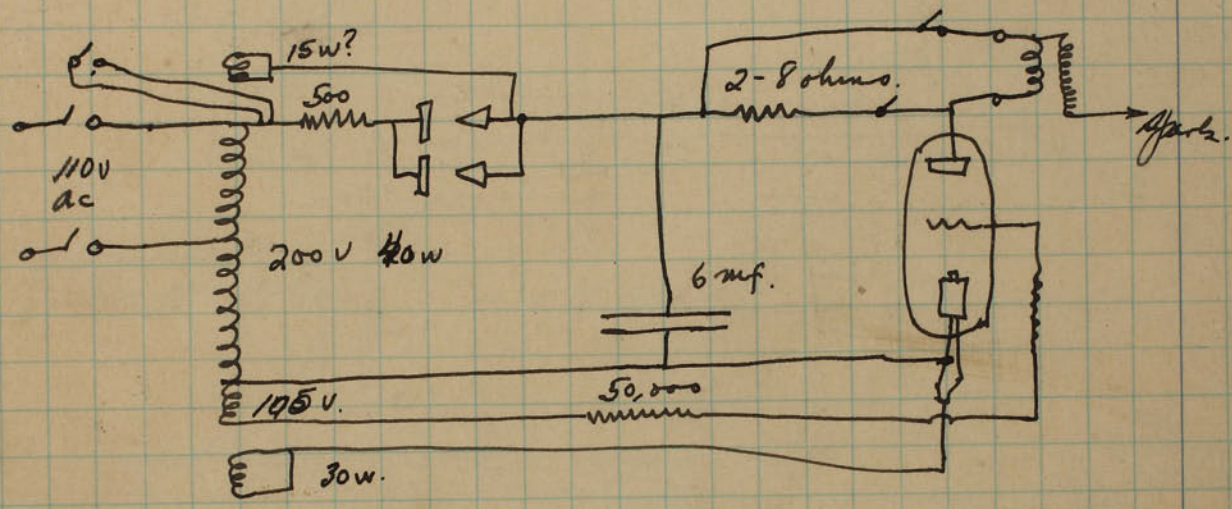A stroboscope for visual work will be a very convenient piece of apparatus. The one designed below is to be a cheaply made outfit which will be operated from any a-c 110 volt circuit (from 25 to 133 cycles per second). It will give sufficient light for observation ~~and~~ and may be good for shadow photography.




- 1- transformer 100 watts.
- 1- condenser 6 mf. 300v d-c.
- 1- resistance 500 ohms 200 ma.
- 1- resistance 2-8 ohms. 200 ma. adjustable.
- 1- resistance 50,000 ohms.
- 2- sockets for rectifiers.

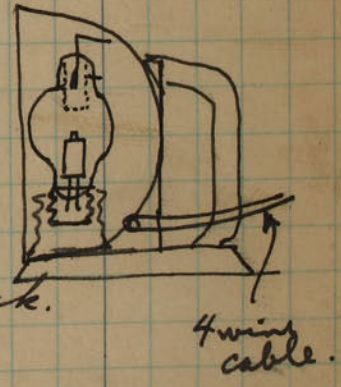
Tubes 1- special thyatron. 100 amp. peak.
2- rectifiers.



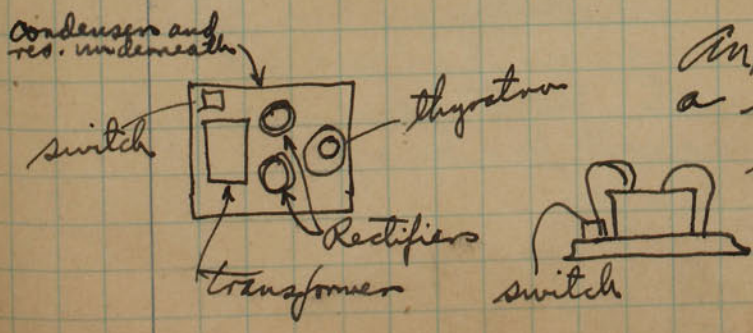
15ft
Insulation cord with a socket and a shade so that the light can be directed without carrying around the entire outfit.



June 2 1931
H. S. Edgerton

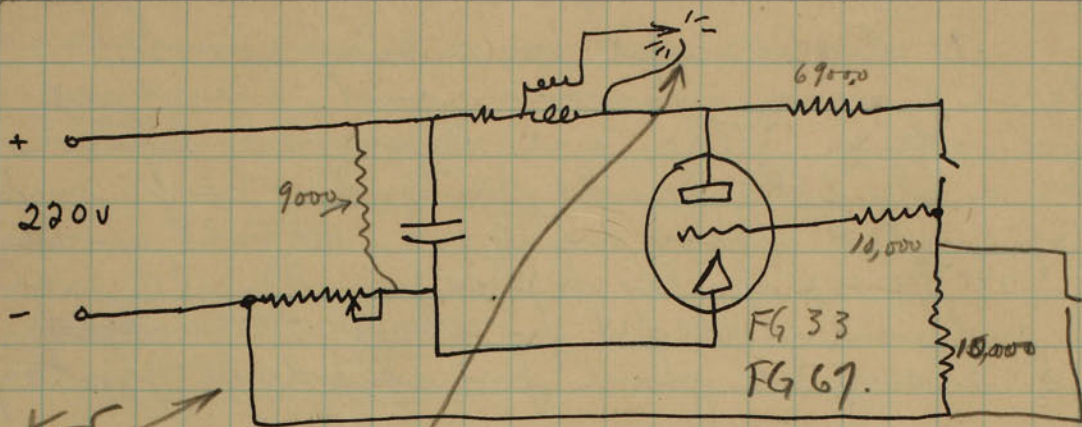

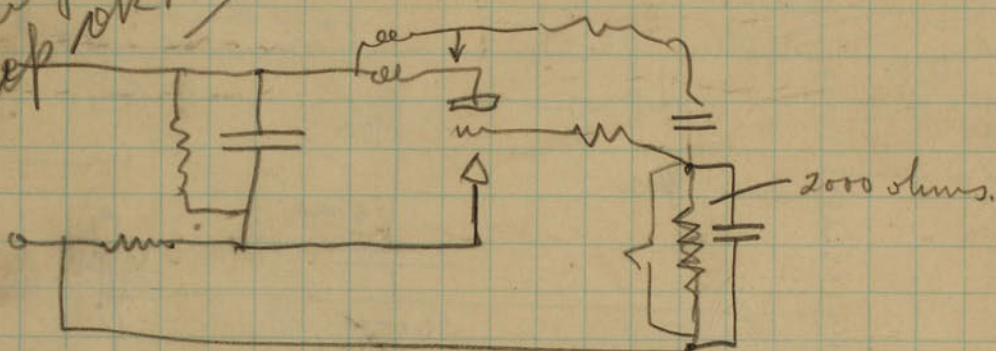Good oscillator
A neon tube was
put on the output
and it lighted up ok.



This was seen in
operation by
Carl Nuttger
Harry Lawrence


$$RC = .0001 \text{ sec}$$

$$R = 2000$$




$$C = \frac{.0001}{2000} = \frac{10^{-4}}{2 \times 10^3} = 5 \times 10^{-7}$$

$$= .5 \times 10^{-6}$$


$$= .5 \text{ farad.}$$

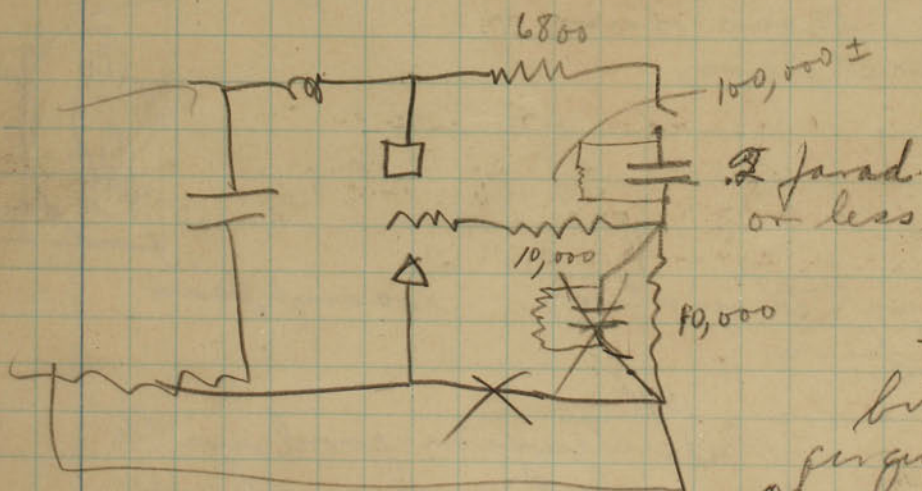

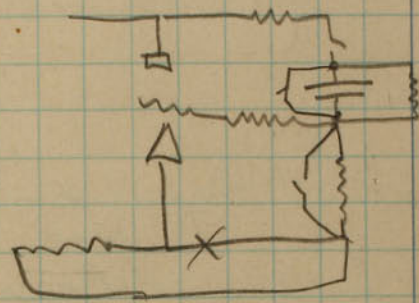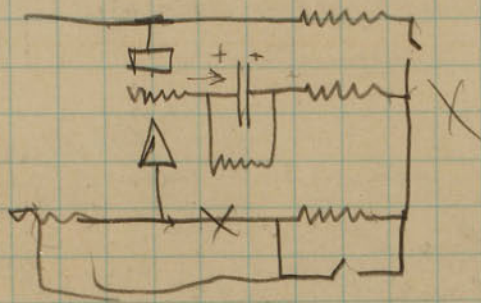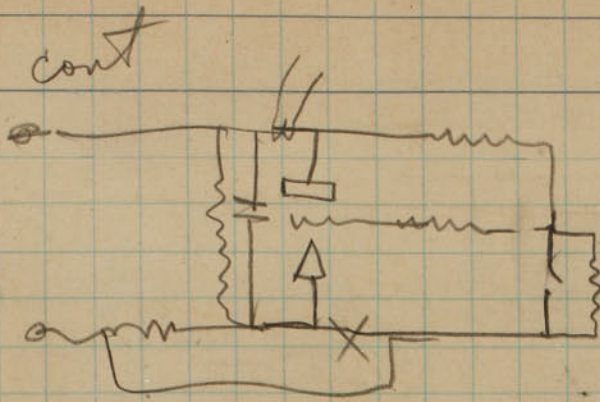Condenser
to cut out
buzz after the
circuit is made.
Ok but the charge
must leak off.
Works fine.




Good osc. circuit

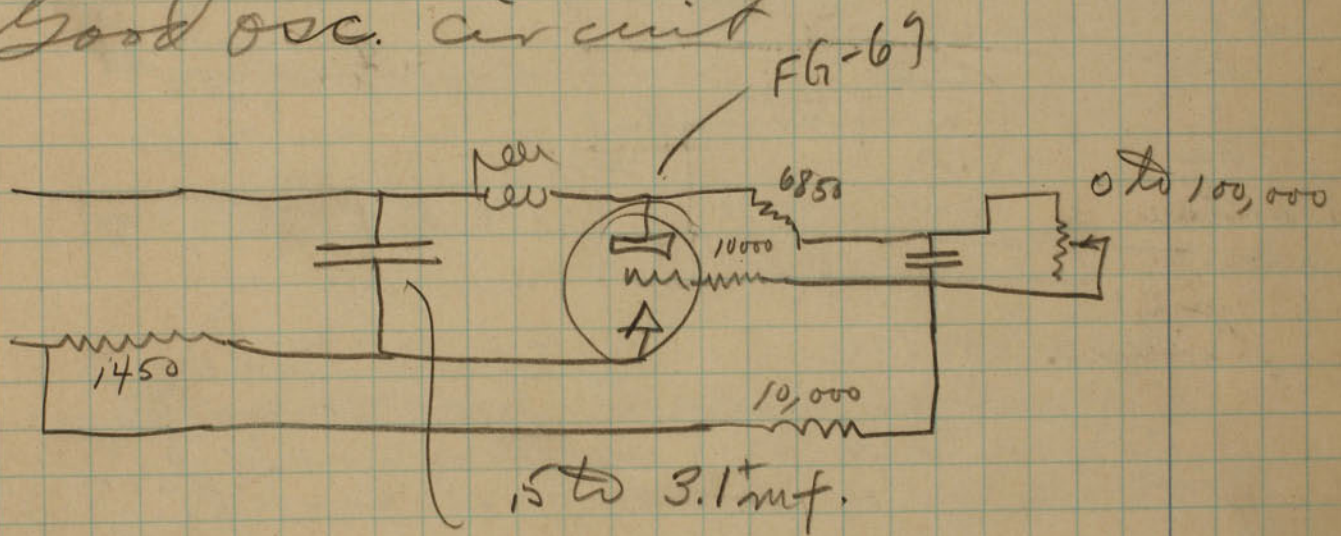


3.1 mf charged to about 200 v
and discharged through the FG 67 gives
about a 1/2 inch spark.

cont.

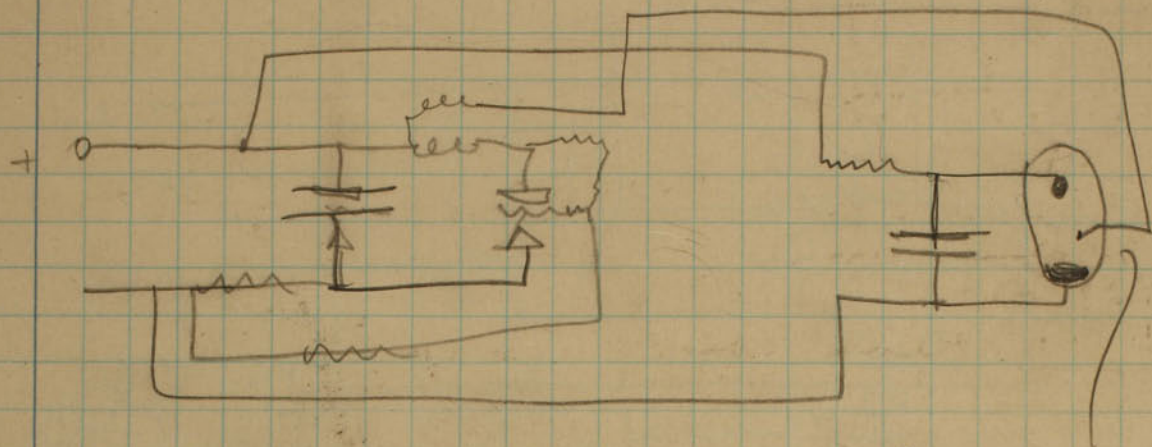

Not very satisfactory operation of this Mercury Pool tube. A special type of pool tube is needed.

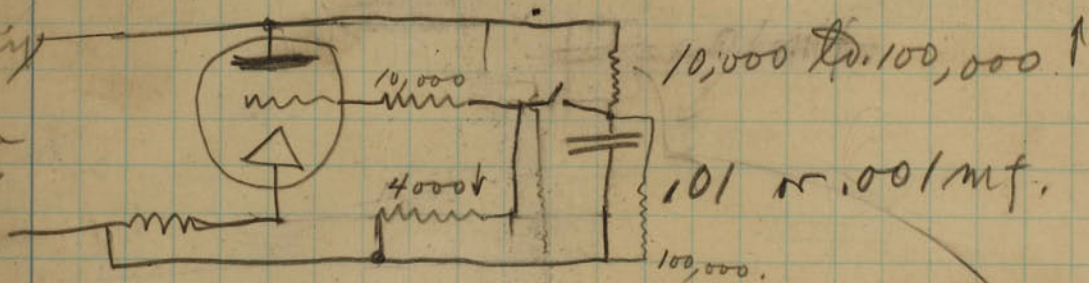Scheme for turning on the thyristor with a make.





$$RC = .000 \text{ sec}$$

$$R = \frac{.0001}{.1 \times 10^{-6}} = 1 \times 10^4 \times 10^9 = 1000 \times 10^3 \text{ ohms} = 10^6 \text{ ohms}$$

$$10^6 \times .1 \times 10^{-6} = .000001$$


Adjust resistances so that the discharge is out both when the switch is open or closed. The tube will flash when the switch is closed.

cont

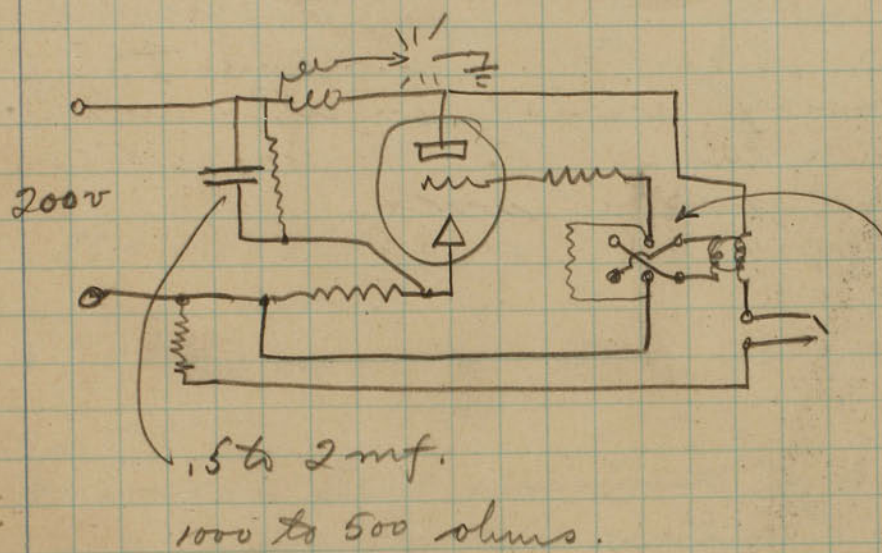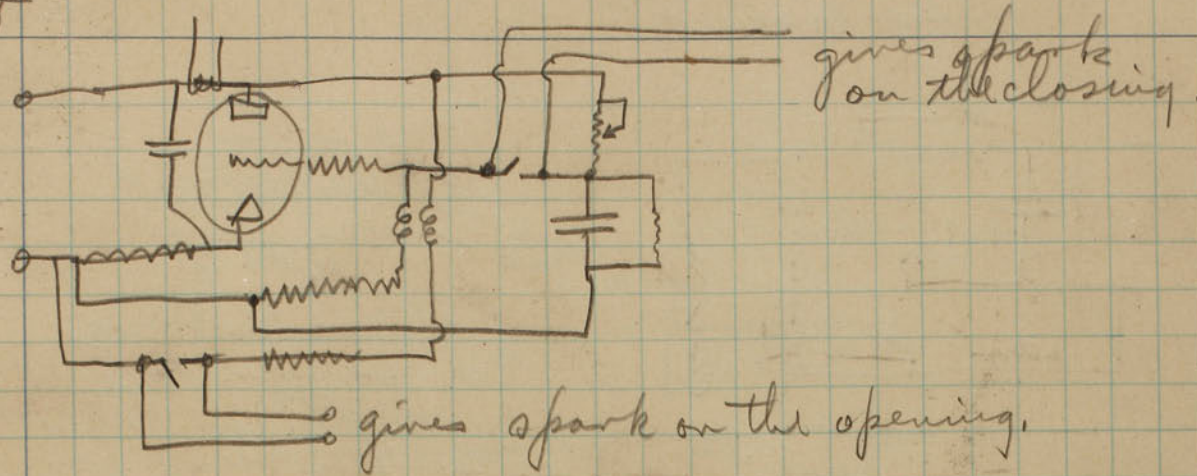

June 3 1931.

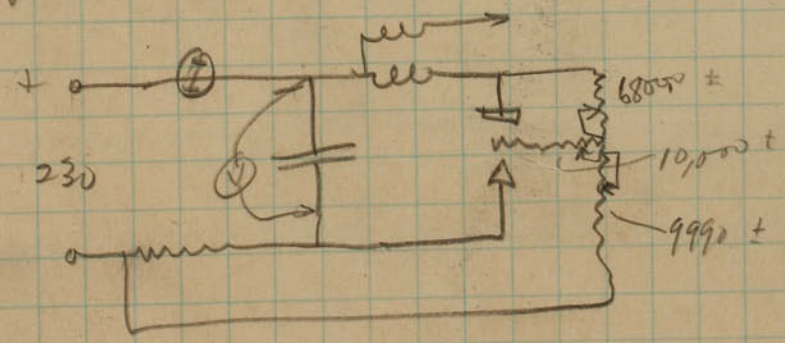
I tried the circuit shown on the top of page 120, working as an oscillator up to an input of 16 amp with an FG-67 tube as the valve. Refuses to oscillate above 1.08 amperes input



June 3, 1931.

Trip circuit

4x4 = '16

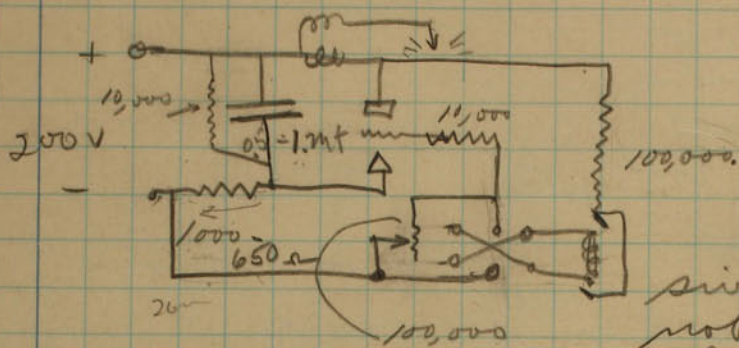


This circuit works fine.

The reversing switch is really not needed?!! When contact is broken or made apparently there is sufficient variation of contact resistance to give enough voltage in either direction to trip the tube. Eddie Taylor came over and saw it work.

.0001 sec.

June 17, 1931.

All A-C thyatron Oscillator.

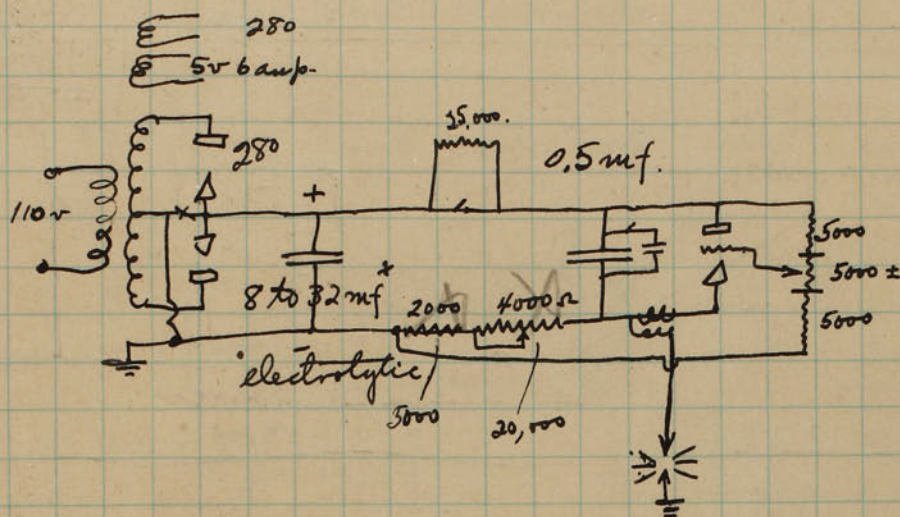

$$RC = 0.5 \times 2000 \times 10^{-6} \text{ sec to } 0.5 \times 6000 \times 10^{-6} \text{ sec.}$$

$$1000 \times 10^{-3} \text{ .. to } 3 \times 10^{-3} \text{ sec.}$$

$$\frac{1}{\pi} = f = 1000 \text{ to } 330 \text{ cycles per sec.}$$

Increase fixed resistance to 5000 ohms.
 " variable resistance to 20,000 "

$$\frac{1}{RC} = \frac{10^6}{5000 \times 5 \times 10^{-6}} = \frac{10^3}{2.5} = 400 \text{ cycles sec.}$$

$$\frac{10^6}{25,000 \times 5} = 79 \text{ cycles/sec.}$$


With a capacity of 0.05 mf. 50. mf.

$$f = \frac{1}{2\pi RC} = 40. \text{ to } 79 \text{ cycles/sec.}$$


Energy may not be enough? $79 \times 60 = 480$ r.p.m.

Insert a fixed resistance of ~~5000~~ 25,000. 39.5 cyc./sec.

Thyratron vibrator

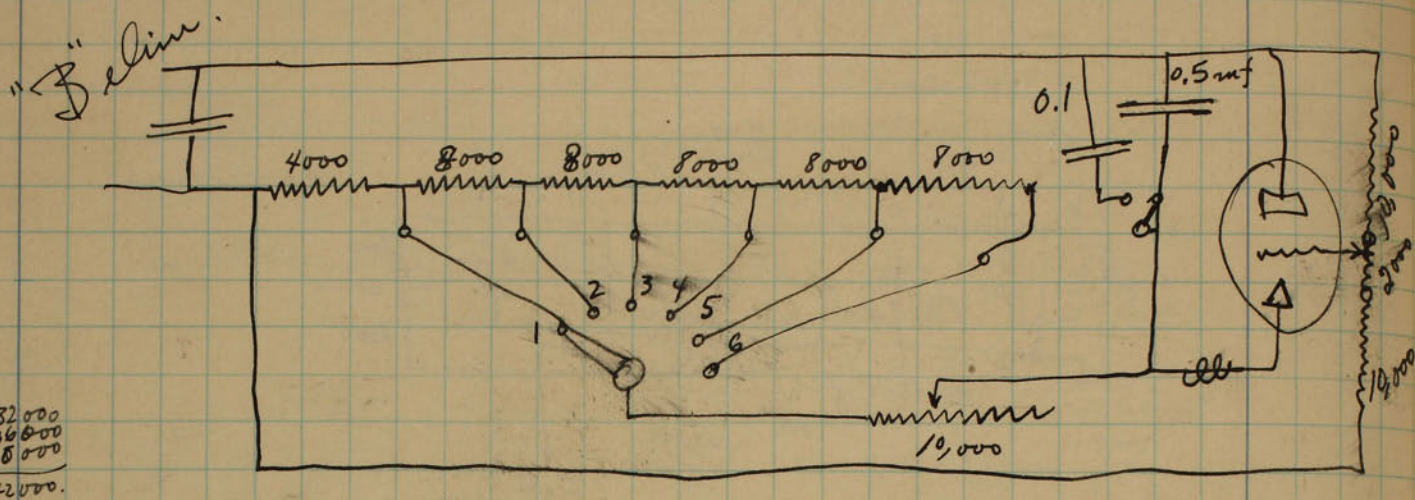

32,000
36,000
18,000
42,000.

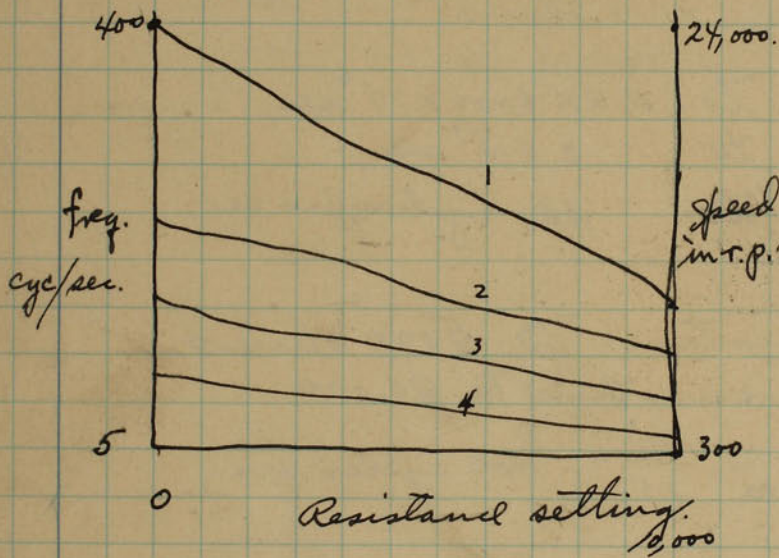

$$\frac{10^6}{14,000 \cdot 5} = \frac{200}{1F} = 143.$$

calibration chart.
two charts
one for each
capacity.

$$\frac{400 \cdot 60}{24,000}$$

$$\frac{400^2}{4 \cdot 400} = \frac{16}{4} = 40 \text{ watts}$$

$$\frac{400 \cdot 8000}{12000} = 260 \cdot 12.5$$



1	- 4000	- 50 watts.
1	- 8000	- 25 watts
1	- 8000	- 5 watt
4	- 8000	2 "

1 - 10,000 a variable 100 ma. at one end.


.01

June 19, 1931.

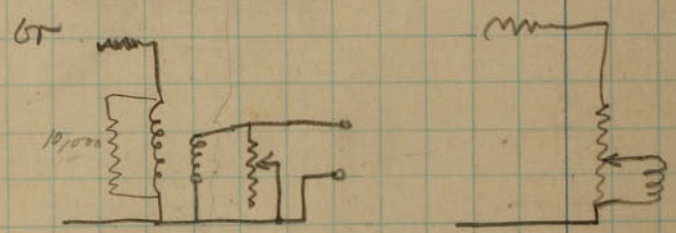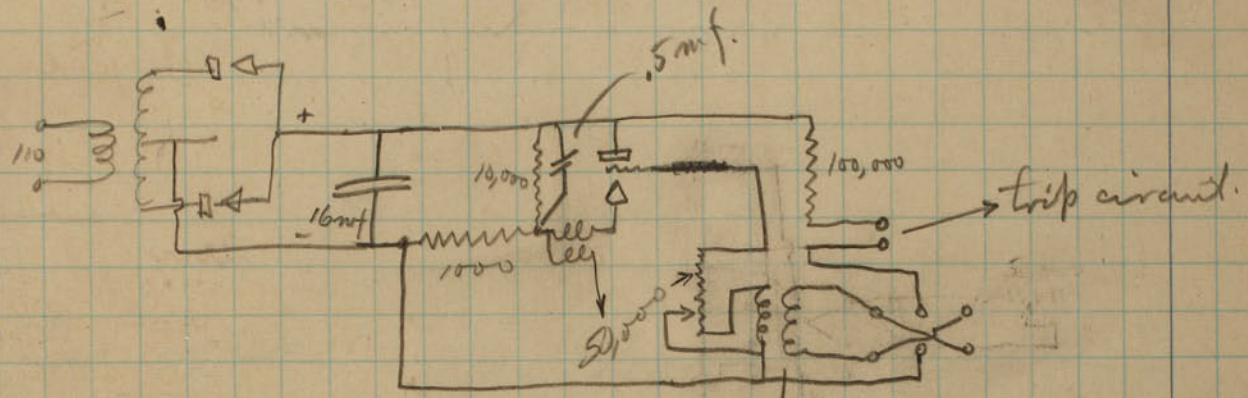Purchased supplies for the indicator apparatus for Engine Lab. yesterday.




actual circuit used,

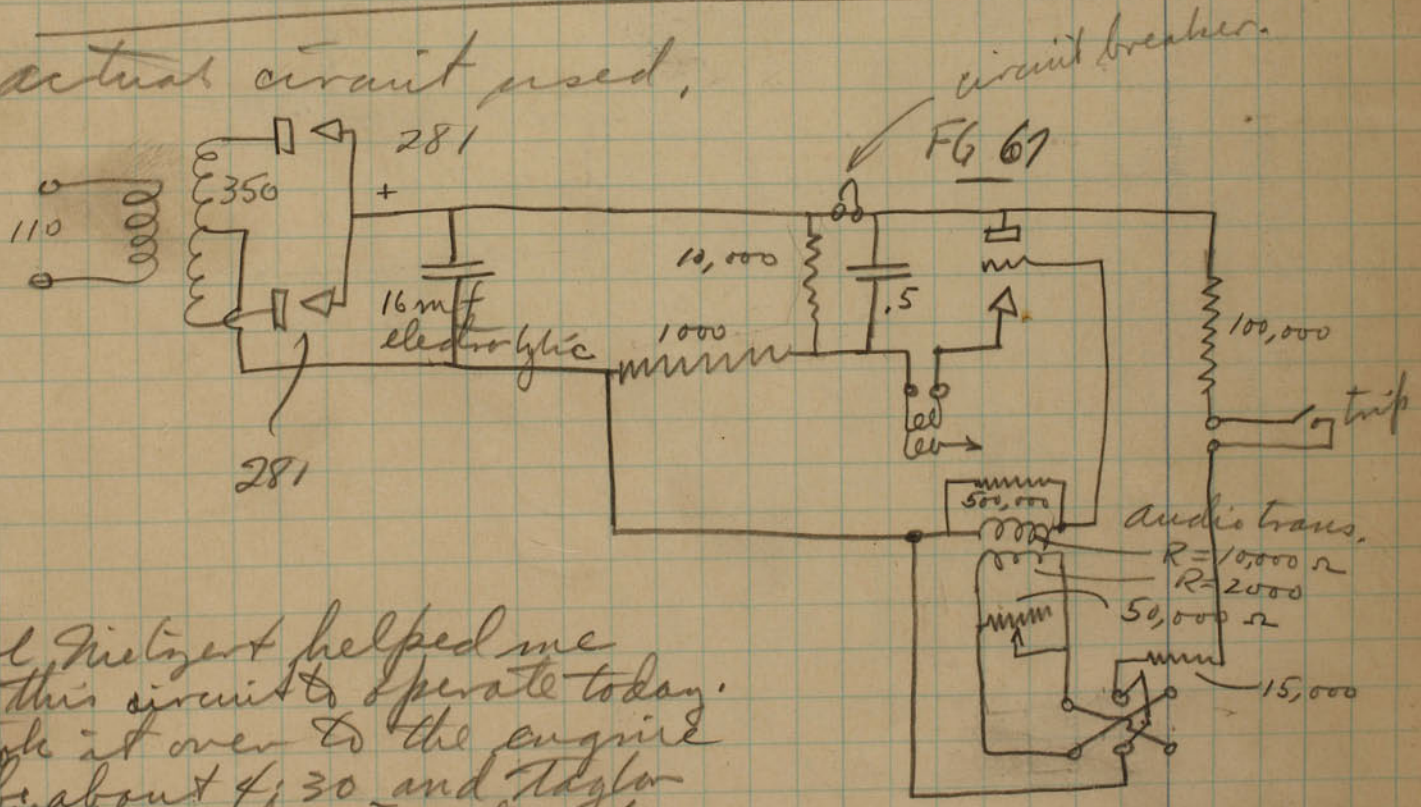


Carl Dietzert helped me get this circuit to operate today. I took it over to the engine lab. about 4:30 and Taylor and two lab. constants saw it work. We did not get a chance to take any indicator cards.

cont p 126.

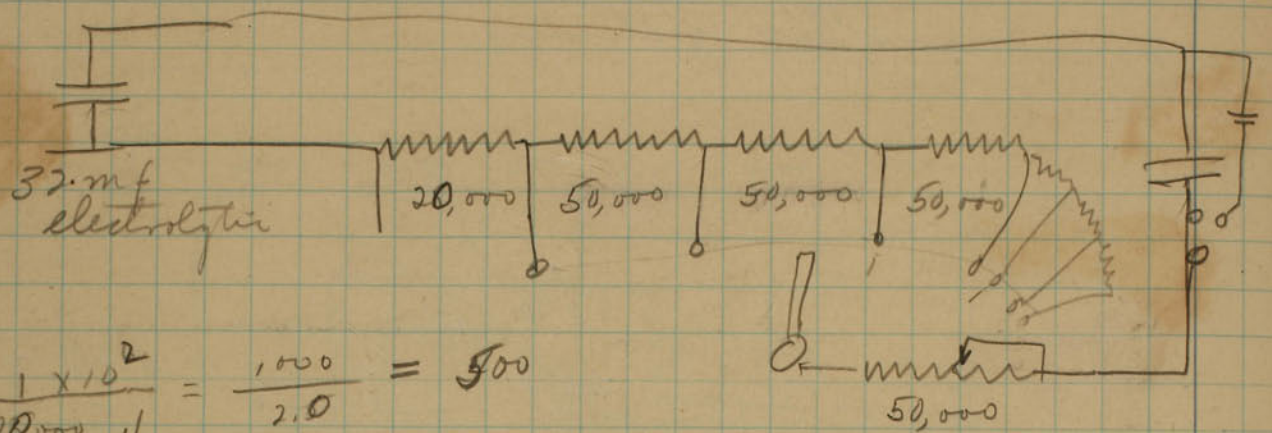


$$\frac{1 \times 10^2}{20,000 \cdot 1} = \frac{1,000}{2.0} = 500$$
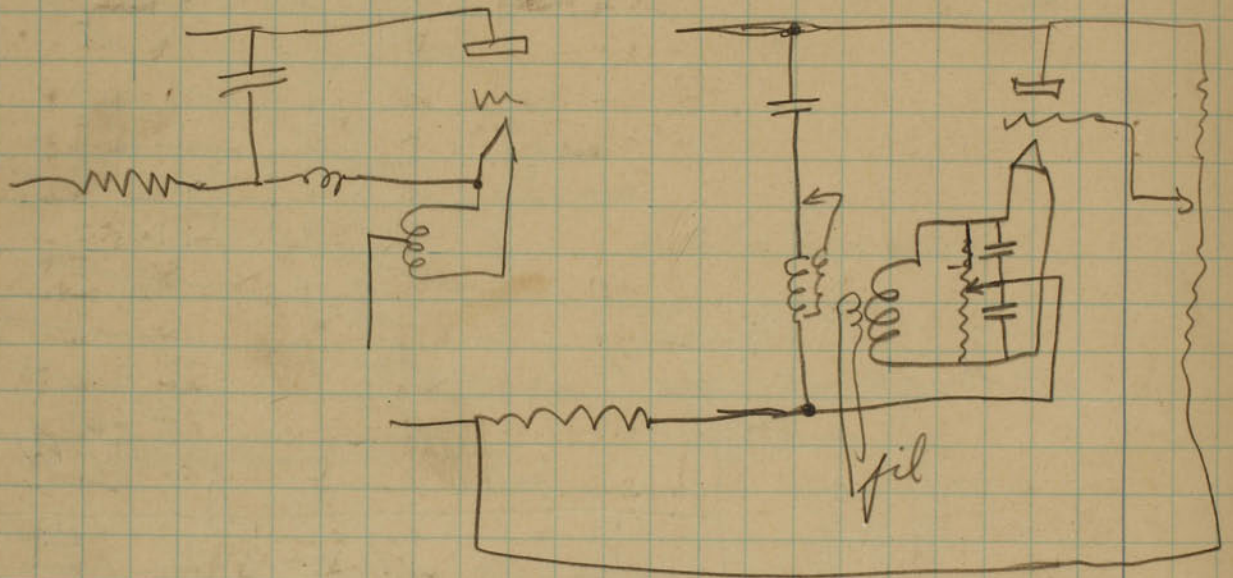
$$\frac{10^6}{R \cdot 5} = 5 \quad R = \frac{10^6}{3 \cdot 5} = \frac{10^6}{2.5} = 400,000 \text{ ohms.}$$



June 23, 1931. Suggested modifications of the circuit shown by Mc Lane and Stander and used in the lab. strobo.


JUNE 23, 1931.
H.F. EDGERTON.

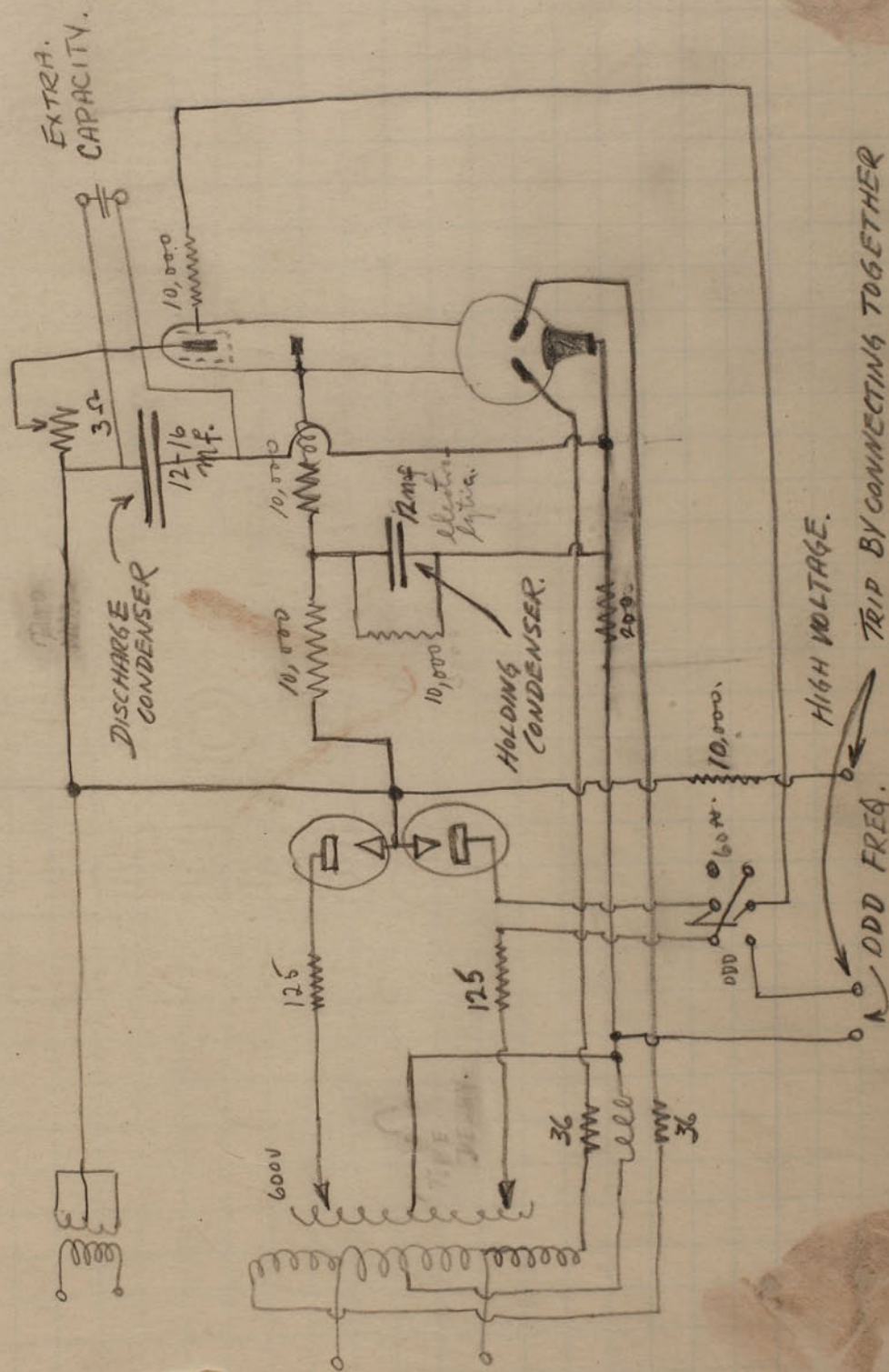

June 24
~~June 24~~

Mr. C.G. Smith of the Raytheon Inc was over and saw the lab. stroboscope which was built by Stander & McClure. I talked with him about the arrangement of p 112 wherein a high voltage starts the spot for each flash. He suggested that a filament placed close above the pool might help to establish a mercury spot because of the increase in vapor pressure. I plan to try this out.

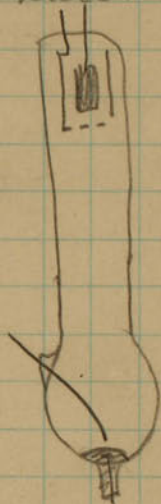I spent sat, mon, and tuesday exhausting a tube of the shape shown. No bombarder was available to drive all the gas out of the anode and grid and as a result the tube has some gas in it which gives a faint red glow when excited by the spark.



The tickler wire does not actuate the tube very consistently. I tried a piece of tinfoil around the bottom and this seemed to work OK.


A spark from a spark coil which resulted from a condenser discharge through a FG 67 thyatron was used to trip the tube by starting a spot.

June 25

I also tried the spark on a 22 inch standard ~~thyatron~~ Cooper Hewitt lamp and it worked alright.

I still need to test these circuits for flicker by observing a synchronous motor.

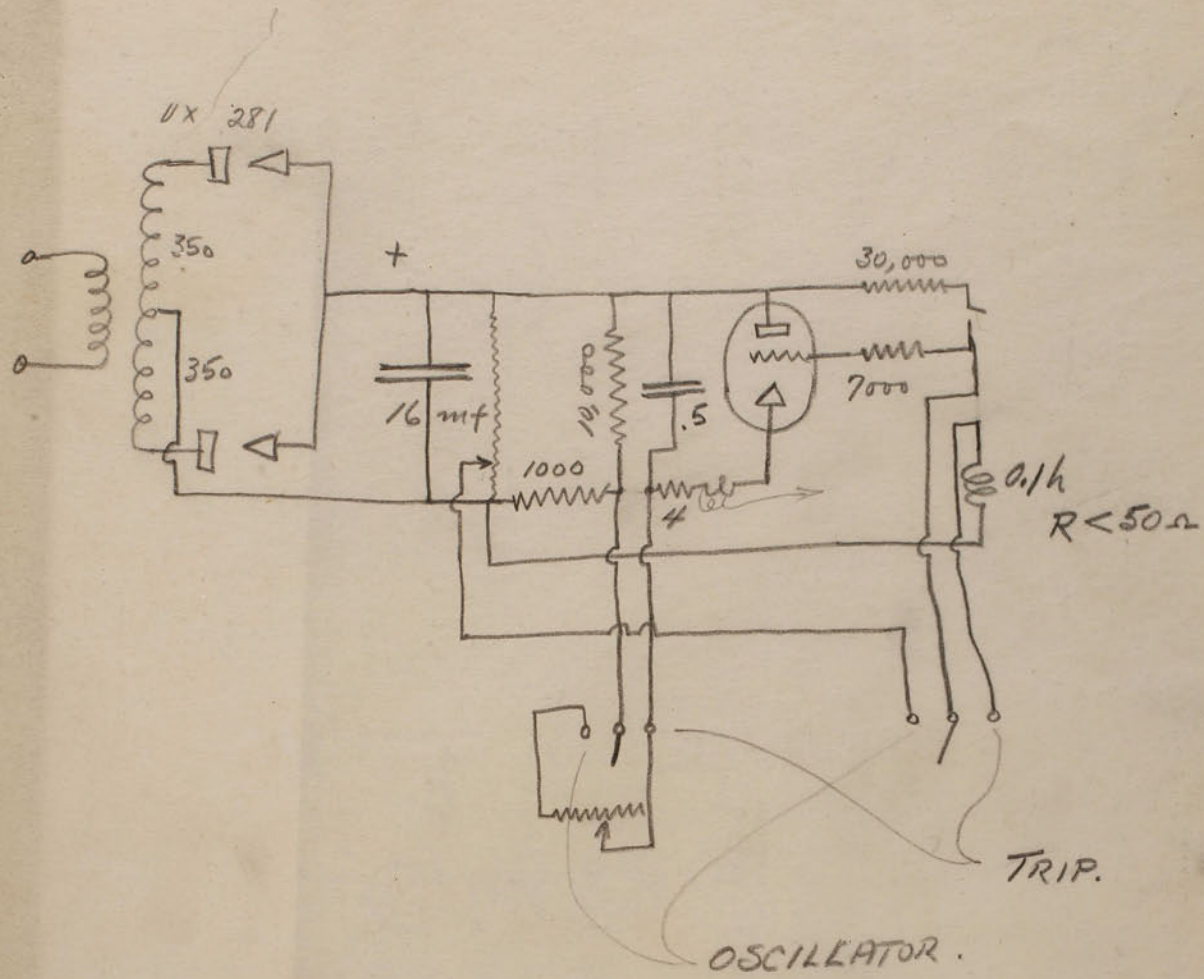
Appears to be OK. There was a small variation which was in phase with the noise from the motor which must have been due to hunting.



6 sec

D

June 25
cont p 127.

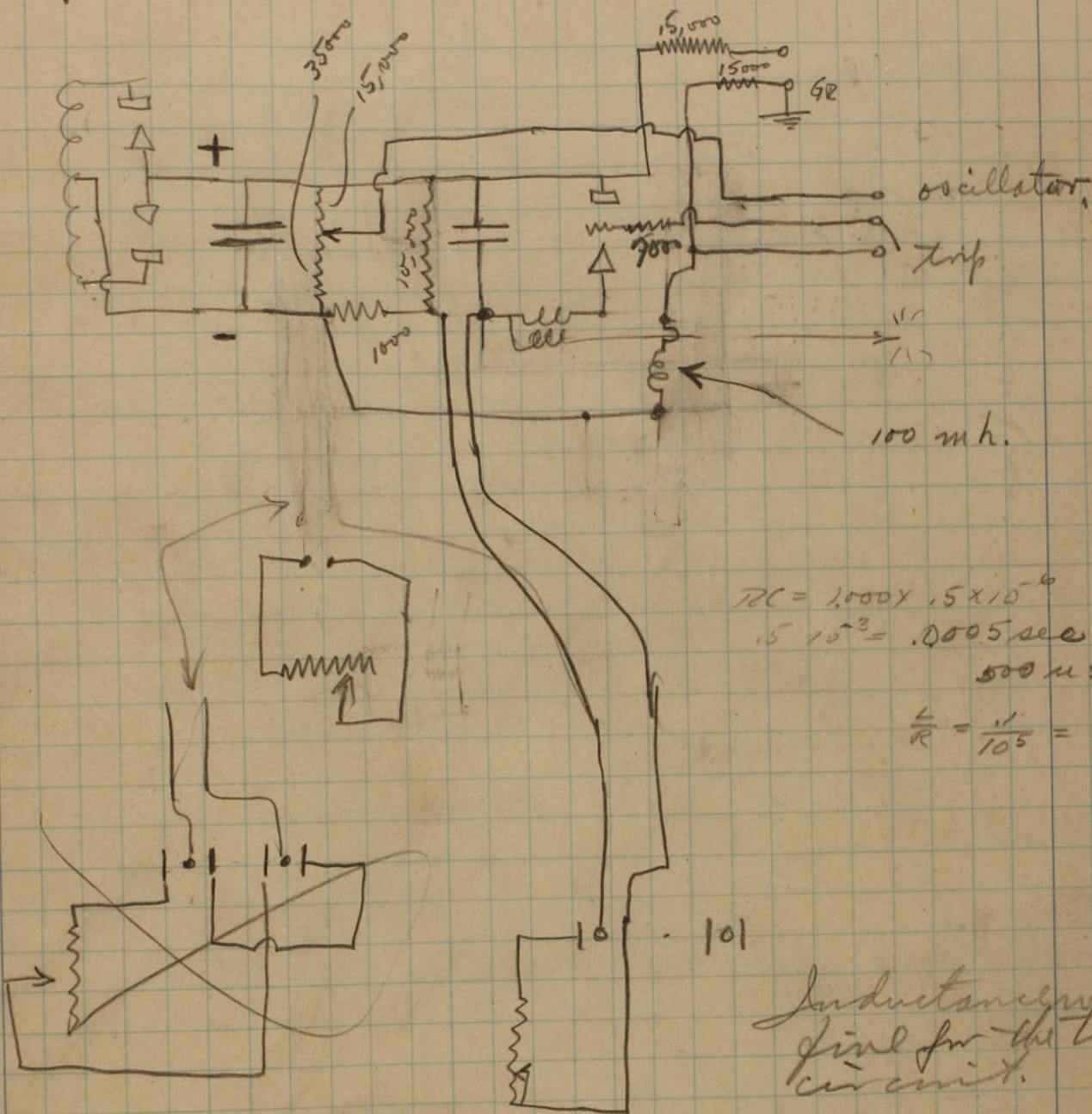

$$RC = 1,000 \times .5 \times 10^{-6}$$

$$.5 \times 10^{-3} = .0005 \text{ sec}$$

$$500 \mu\text{s.}$$

$$\frac{L}{R} = \frac{1}{105} = 1 \times 10^{-6} \text{ sec.}$$

Inductance works
fine for the trip
circuit.

$$\frac{1}{60 \text{ Acc}} = RC$$

$$1 = 60 RC$$

$$7 = \frac{30 \times 10^{-6}}{.5 \times 10^{-4}} R$$

$$10 \times 10^4 = R$$

$$100,000$$

Oscillator part fails
& won't work for some
reason.




June 25 1931.

My experiments of today are very encouraging. We can use for stroboscope tubes simple tubes with an anode and cathode instead of the complicated thyratrons that we have used in most of the experiments to date. Our laboratory stroboscope now has a special tube that has seven seals and it is expensive and dangerous to move and use.

A small thyatron will act as a switch which will trip a large tube from the outside by means of a condenser plate ^{around the cathode} and external grid.

We tried to do this same thing several years ago with a Cooper Hewitt lamp but the experiment was a failure because of the difficulty of starting the spot. The small thyatron does the trick.


June 25 1931.

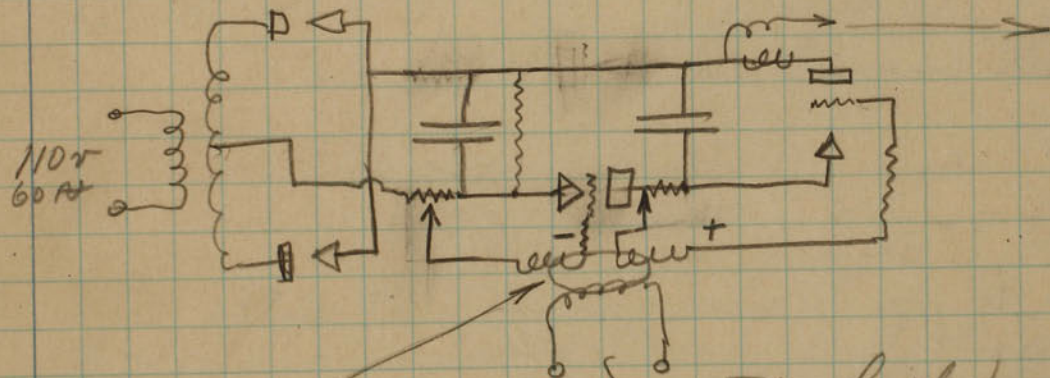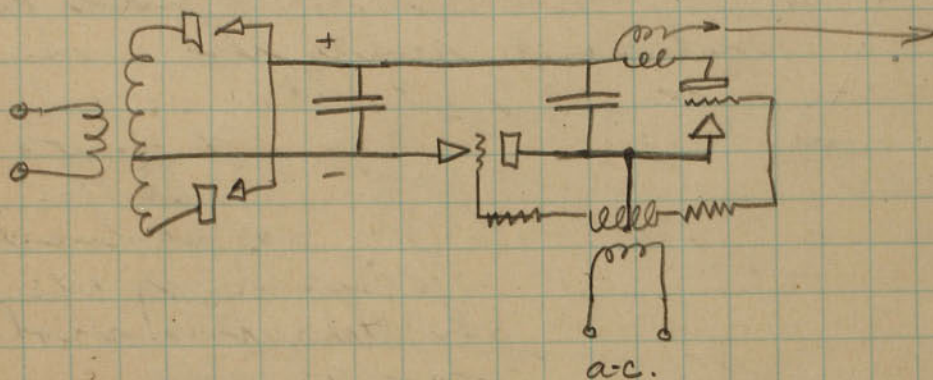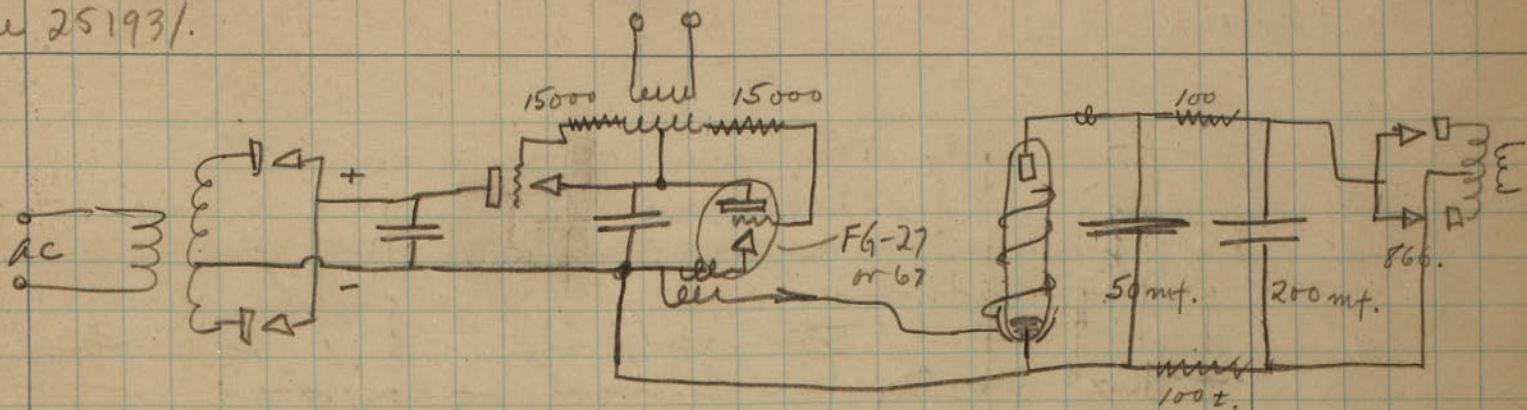

allows current to flow when the thyatron grid is negative and thus charges up the condenser.

To beat freq oscillator or other ac source to give stroboscopic light.


June 26 1931

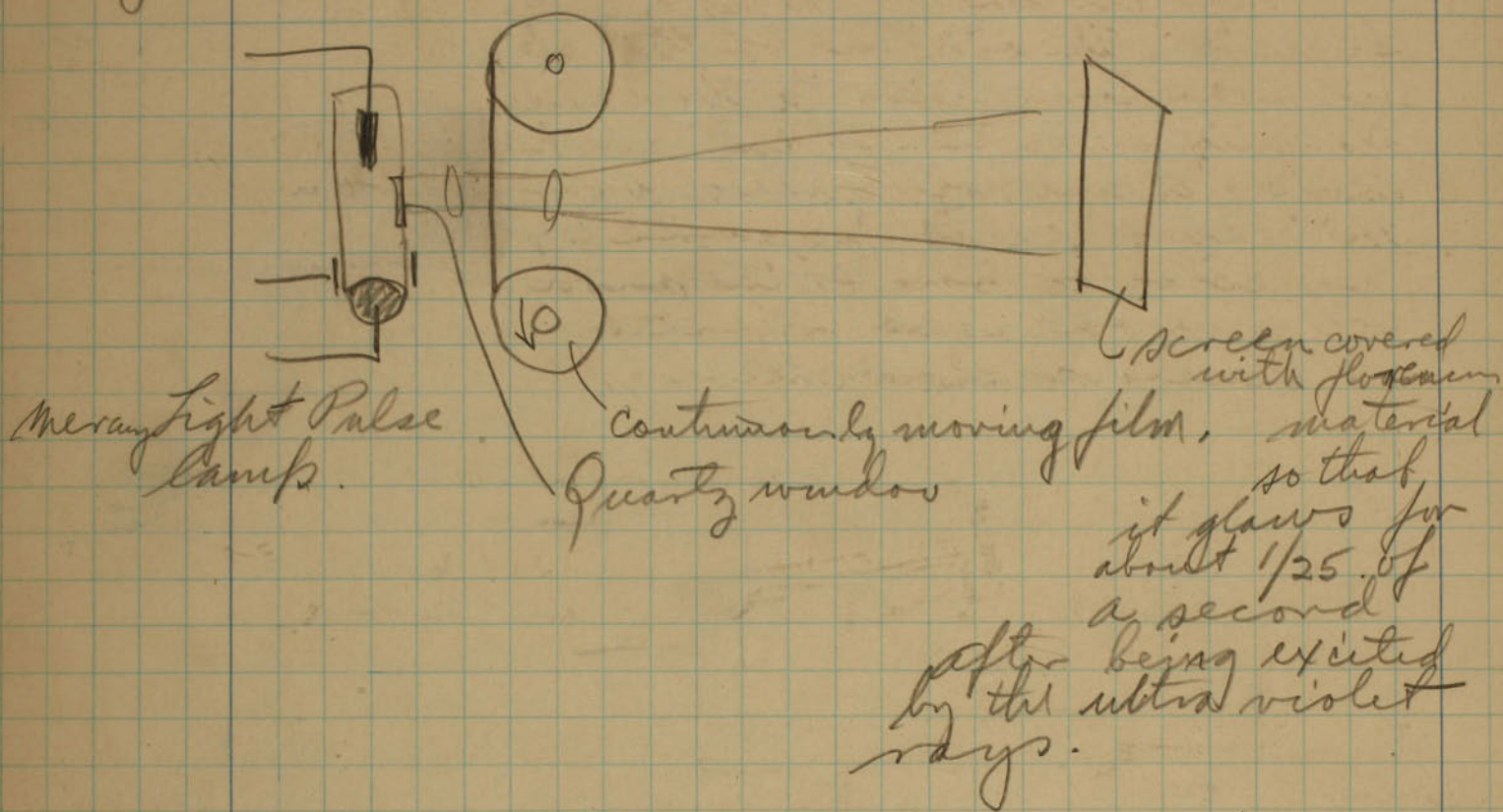

July 1. 1931. Film does not pass U.V. ?

June 26, 1931

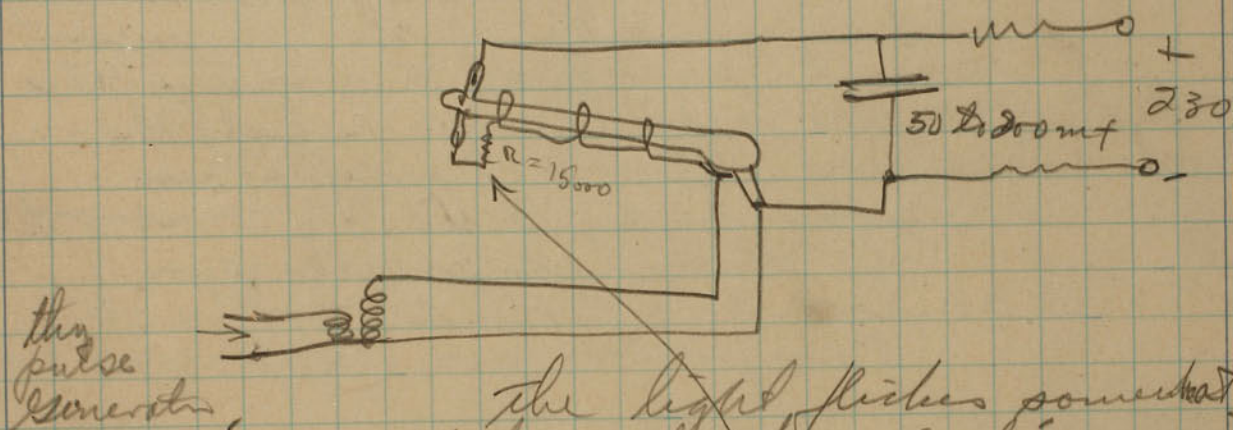Used circuit of p 131 as an oscillator. The output of the spark coil was connected to the condenser starting connection of the coope. Hewitt lamp. A fine wire was wound around the lamp up to the anode and connected to one of the anodes. The other anode was connected to a condenser as shown below.




The light flicks somewhat if the anode here is disconnected.

Took the arrangement of p 131 over to the engine laboratory and Prof. E. Taylor tried it out. It did not give an indication on the break for some reason. The contacts may be bad or the circuit somewhat slower than estimated. The oscillator part worked great and gave a lot of light from a neon tube.


The tube from Dr A. N. Hull of the G. E. Company arrived. It looks like a dandy.

June 27/1931

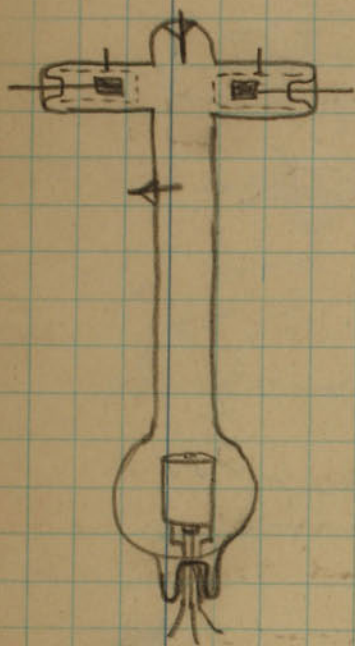

The special thyratron that Dr. A. W. Hull sent has a cathode about $1\frac{3}{4}$ inches in diameter. It is of the fin type, protected by the cap against excess heat radiation. The emitting surfaces do not appear to be coated with oxide. The metal appears clean or only slightly tarnished. I connected up the filament and ran it at 5 volts. The surfaces became a dull cherry red. About 15 amperes was passed from one of the anodes with an arc drop of 32 volts. With 5 amps the arc drop was 36v.

June 28 1931. Tests to be made.

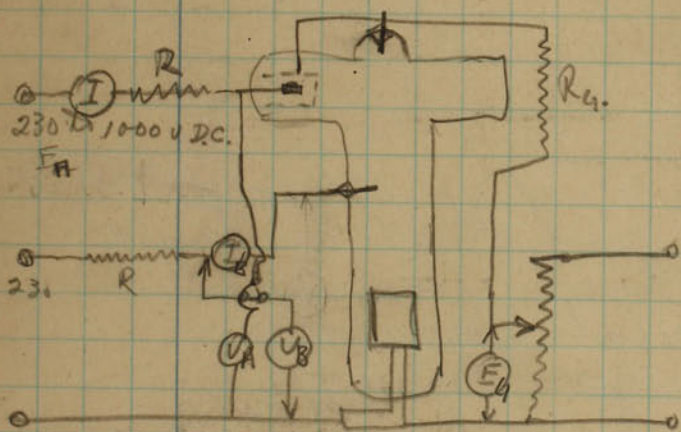


$I_B = \text{constant}$
1, 10, 100, 1000 ma.



$R = \text{such as to allow 5 amp to flow.}$

$E_C \approx E_A$ for arc to strike.

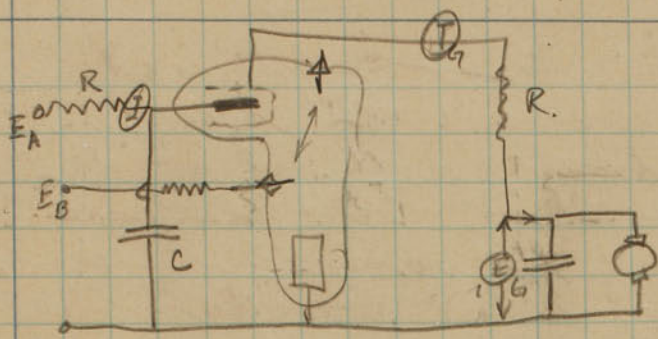
Put condenser across anode to cathode to see if the critical condition is the same.





Determine the limits of oscillation.

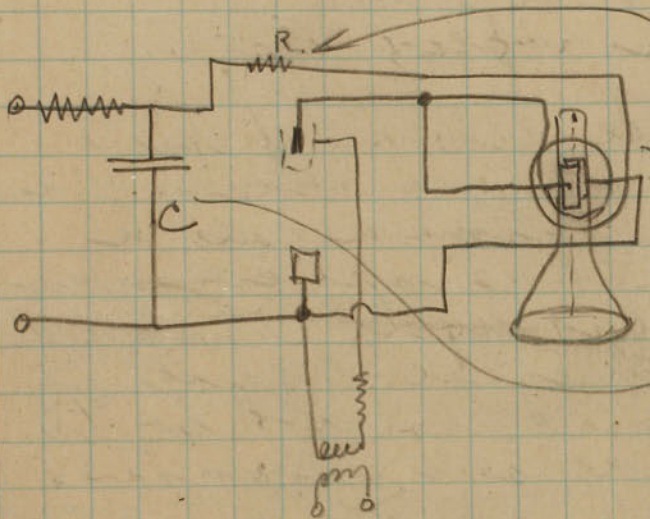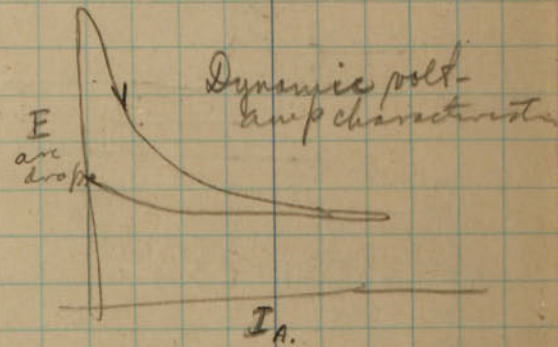

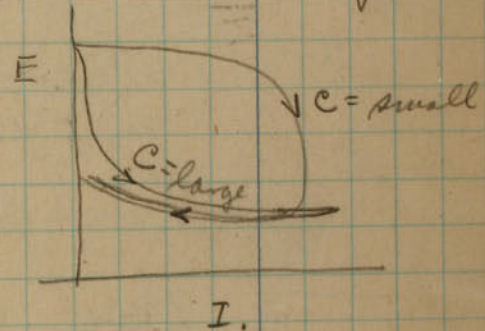keep R constant and obtain characteristics for different values of C




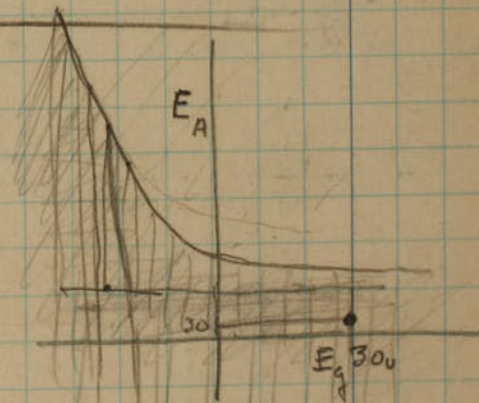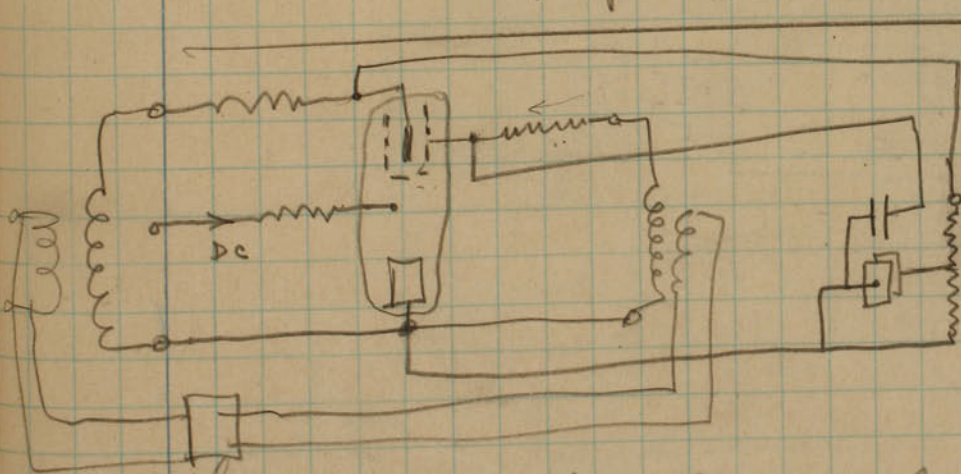magnetic field deflects beam proportional to the current.




phase shifter


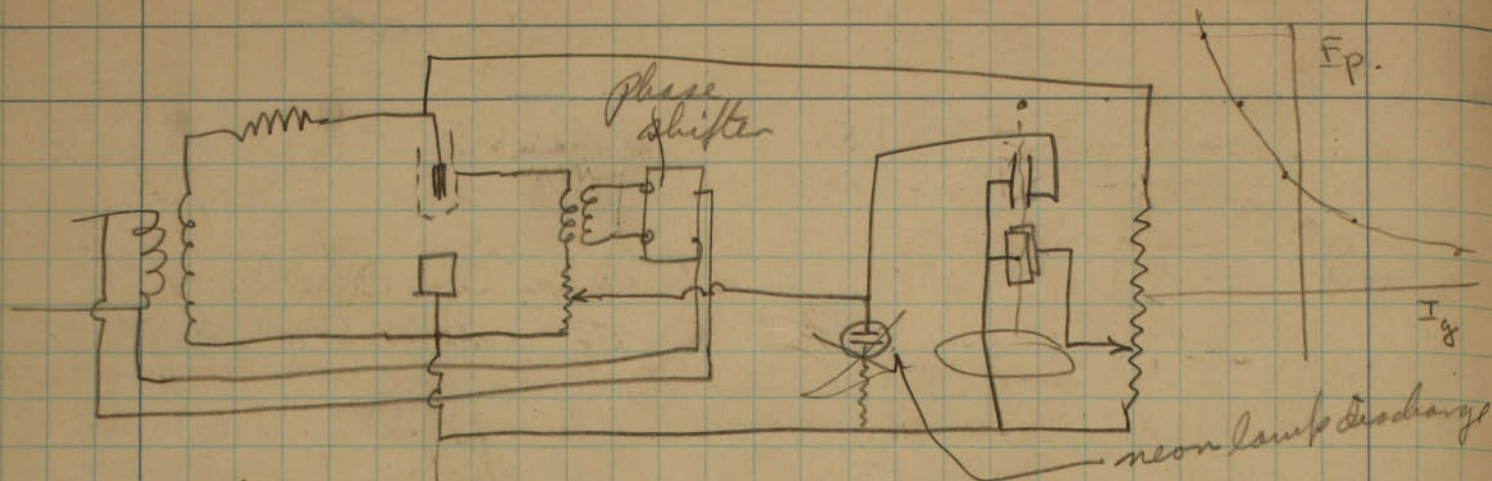
This looks like a fine method to determine the $E_A - E_G$ characteristics of thyratrons. It should be fast and accurate since it is a dynamic determination.



This gives a curve of $E_p - I_g$

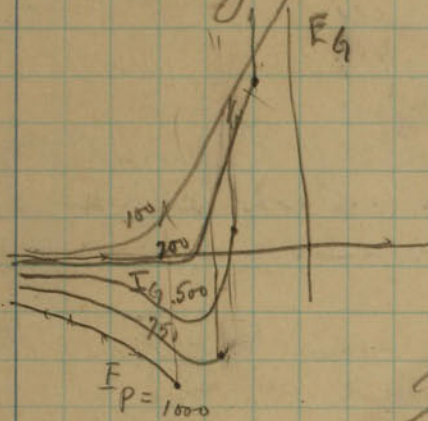

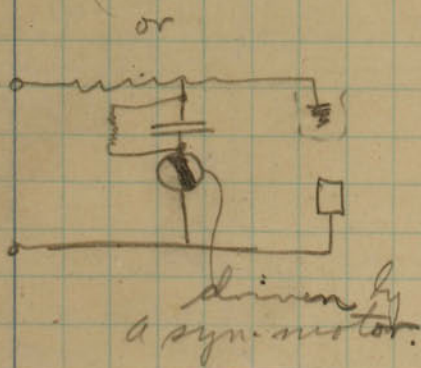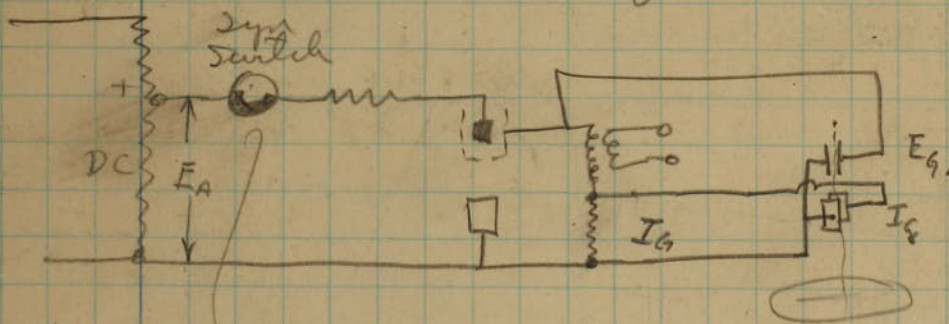Use dc on the plate with condenser and resistance as a stroboscope circuit so that it will extinguish each cycle. Another scheme would be to use a synchronous switch to disconnect the plate circuit.




June 29 1931

Filament when hot

873
5.1 v.


30041
27.4 amp.

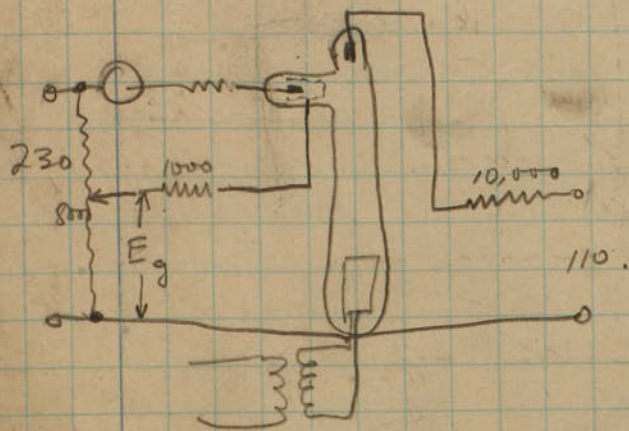

Condition to start 2 amp.

$E_g = 46 \text{ volts}$ $R_g = 10,000 \Omega$


94.5.	11,000	
101.	11,000	3.95 I
109.	11,000	2.00
111	11,000	3.95.
117	11,000	2.00

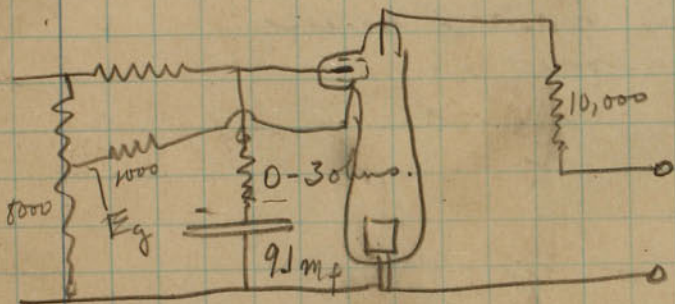


oscillates at a high frequency 3000 or 5000 cyc/sec.

Reduce R in series with C reduces freq.

Reduce E_g reduces freq.

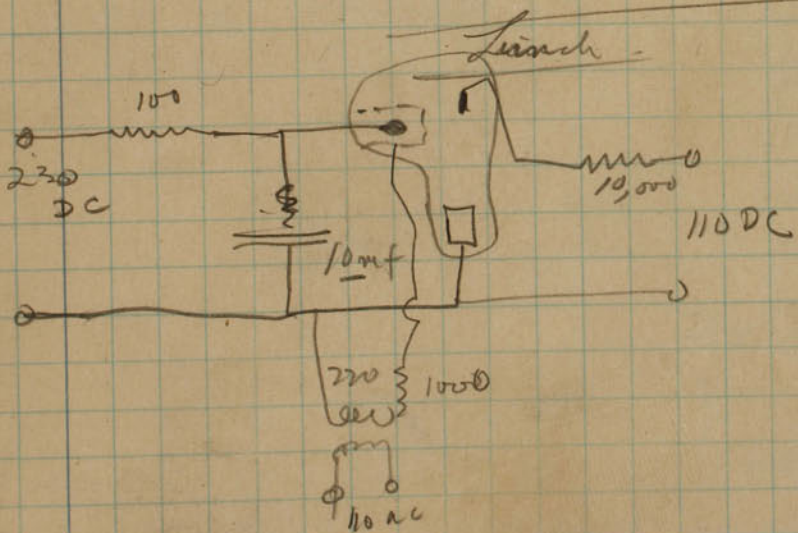

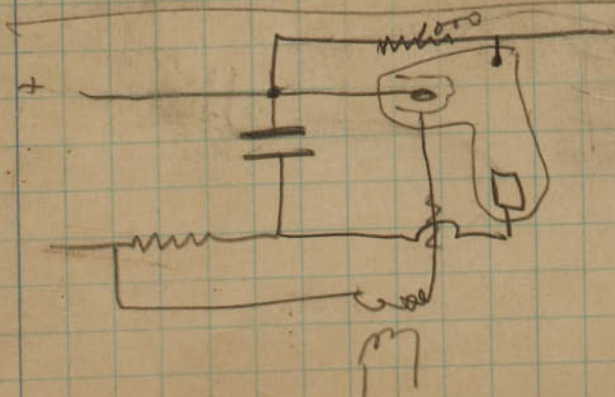works fine.
freq of trailers $\frac{54}{60}$
 $(27 \times 2) \times 60 = 3240 \text{ cycles/sec.}$




June 30 1930

Spent all day getting the rat on the exhaust system in 10-385. Dr Bush gave several suggestions regarding cleaning the tube and mercury. C. P. mercury was used today. The tube was washed with chromic acid, distilled water and alcohol. An oven must be built tomorrow.

- July 1 1930 Exhausted the tube and sealed off at 6 pm.
 2 1930 Tried tube in circuit and it works ok. Cleaned the mercury out of an old broken tube and will try to fix it up tomorrow. Practiced making tungsten to molybdenum seals.
- July 3 1931. Worked in office and hunted for a house.

July 5 1931
H. E. Edgerton.

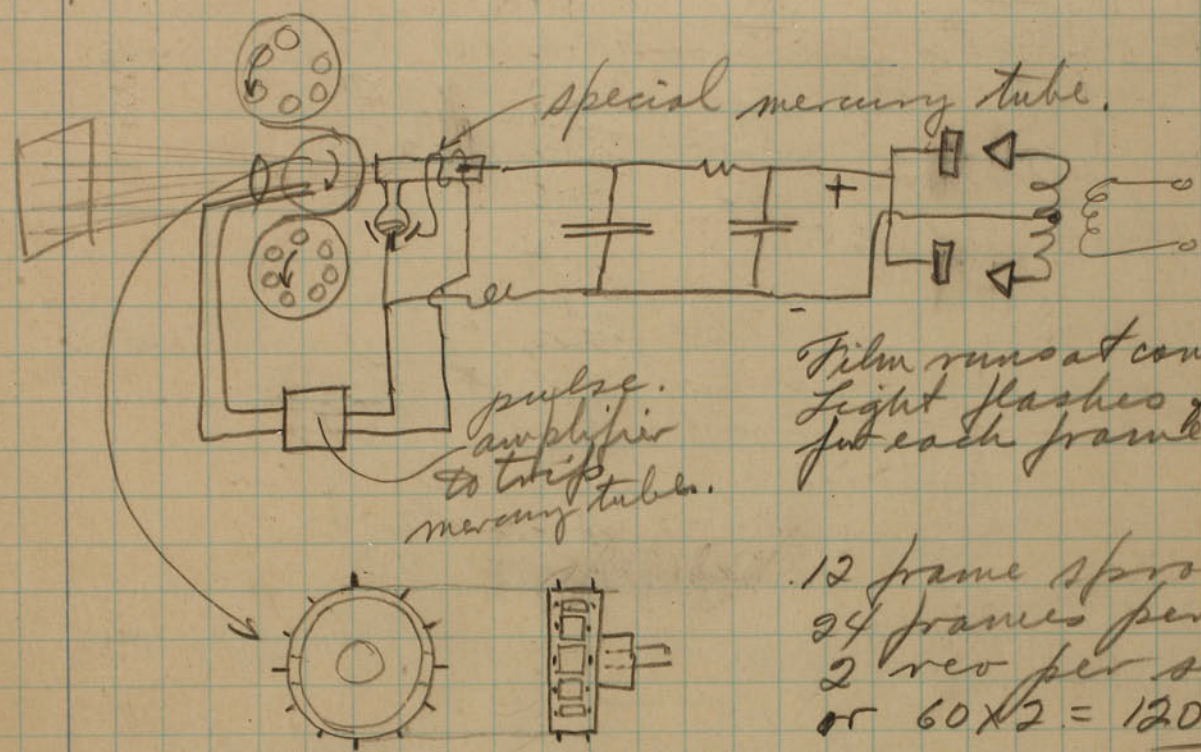Moving Picture Projector. (Stroboscopic).



special mercury tube.
pulse amplifier to trip mercury tubes.

Film runs at continuous speed.
Light flashes for about 20 m.s. for each frame.

12 frame sprocket.
24 frames per second.
2 rev per sec
or $60 \times 2 = 120$ r.p.m.

This was shown and explained to me on July 8, 1931 by C. S. Draper

$$\begin{array}{r} 33\frac{1}{3} \overline{) 1440} \\ 132 \\ \hline 120 \end{array}$$

$$\begin{array}{r} 480 \overline{) 1440} \\ 12 \\ \hline 24 \end{array}$$


$\frac{120}{3} = 40$ to gear to sound.

$.5 \text{ in} \times 12 \text{ inch} \frac{6}{\pi} = 2 \text{ inches}$
~~say 3 inches~~

or the sprocket can be run at $33\frac{1}{3}$ r.p.m.

Make sprocket 20 frame 1 rev. in
 $20 \times 24 = 480$ r.p.s.
 $\frac{480}{60} = 80$ r.p.m.

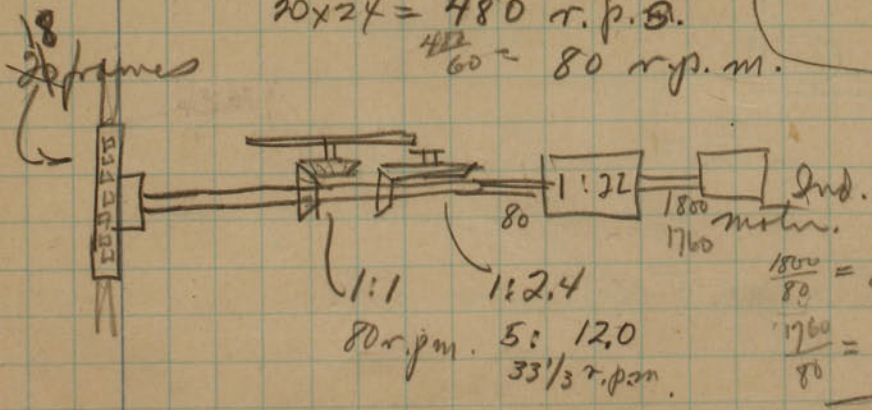$\frac{10}{33\frac{1}{3}} = .03 \text{ sec.}$
or 1.8 sec
 $24 \times 1.8 = 43.2$ frames per rev.
 $78 \text{ r.p.m.} = 468 \text{ r.p.s.}$
 $\frac{468}{24} = 19.5$ frames.




$\frac{1800}{80} = 22.5$ ratio.
 $\frac{1760}{80} = 22.0$ ratio.

? X ✓

Cont.

20 frame sprock.

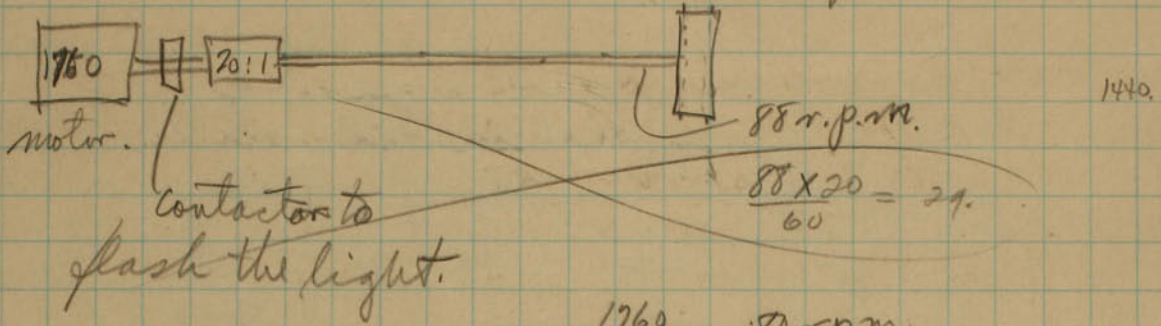


$$\frac{88 \times 20}{60} = 29.$$

$$\frac{1760}{22} = 80 \text{ rpm.}$$

$$\frac{80 \times 22}{60} = 29.$$

30.

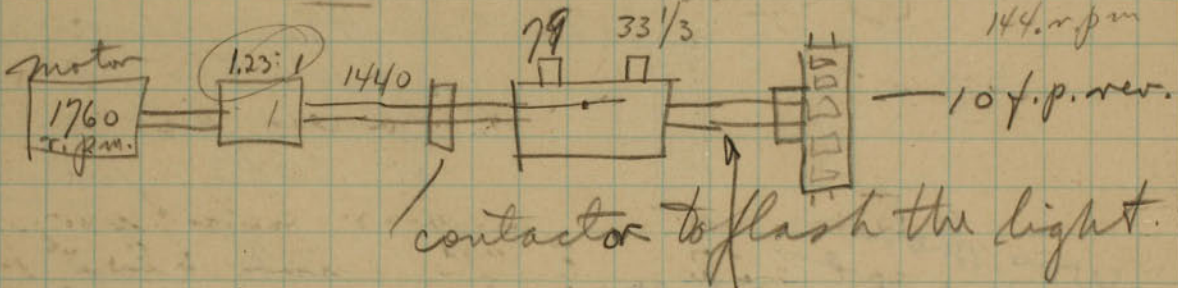

contactor to flash the light.

24 f.p.s.


10	2.4	144
20	1.2	72

$$\frac{1}{960} = \frac{1760}{1.83}$$

144 r.p.m. or 2.4 r.p.s.

110 1182

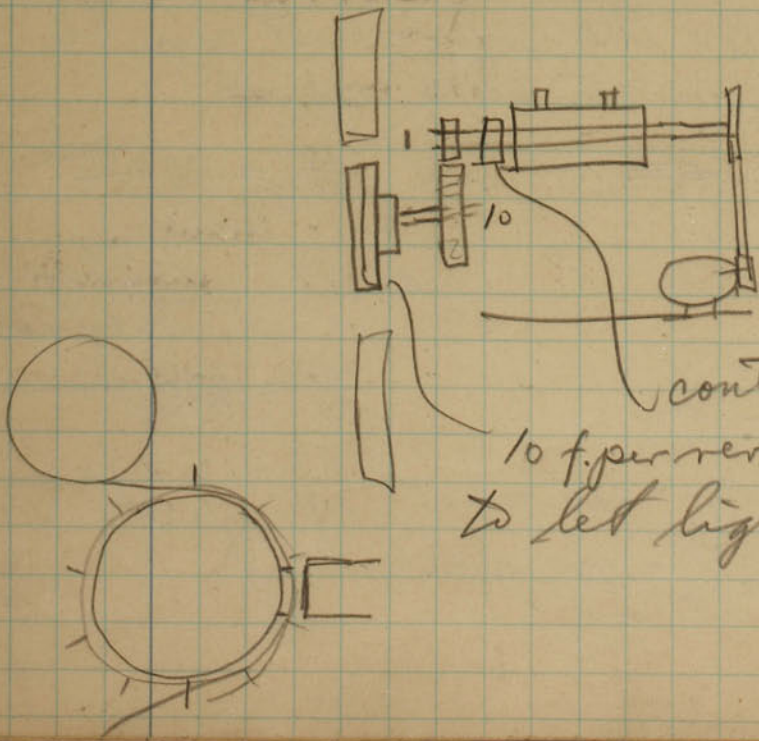
Experimental setup with a Sprague Visivox projector





cont.

16mm $16 \times 2.54 = .628$ inches.

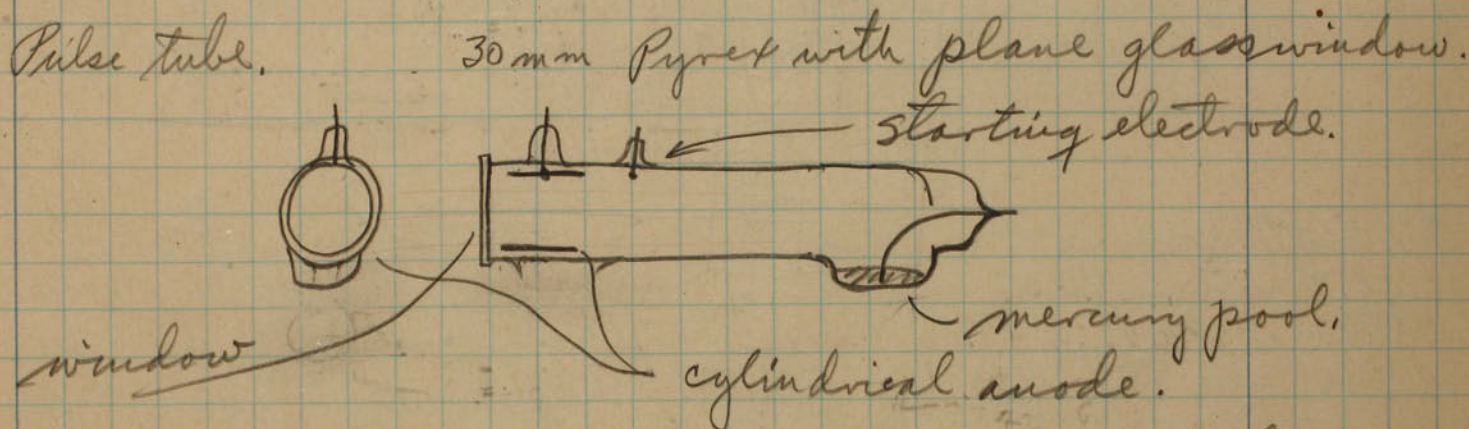$.628 \times 10 = 6.28$ inch in circumference
 $\frac{6.28}{\pi} = 2$ inches in diameter for the sprocket.



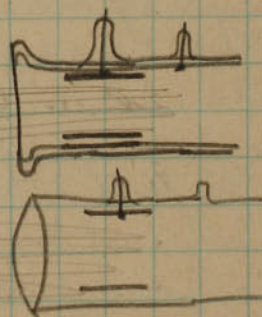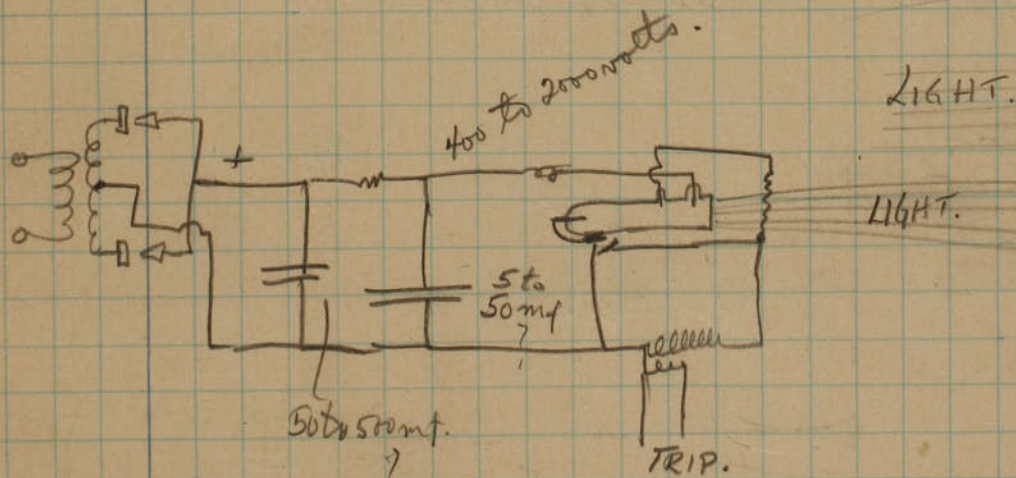Ventilation will be provided for the back end of the tube. The heat from the anode should be sufficient to keep the window clean of condensed mercury. The window should be as thin as possible. Bell ends may be employed. The window can be a lens.




- 1- projector. 1000
 - 2 mechanical alterations 1000
 - 3 electrical circuits, tubes etc. 1000
 - 4. Search Patents 2000
 - 5. Misc 1000
5000.
 \$ 500.

Ordinary projector 100 watts for $\frac{1}{42}$ of a sec.
 If the light is on $\frac{1}{1000}$ of $\frac{1}{42}$ of a sec
 the light intensity needs to be that of a 100×1000 watt lamp.
 "100,000 watt."
 $500v \times 100amp = 200 amp (leaky!)$

Prelim exp.


July 1, 1931

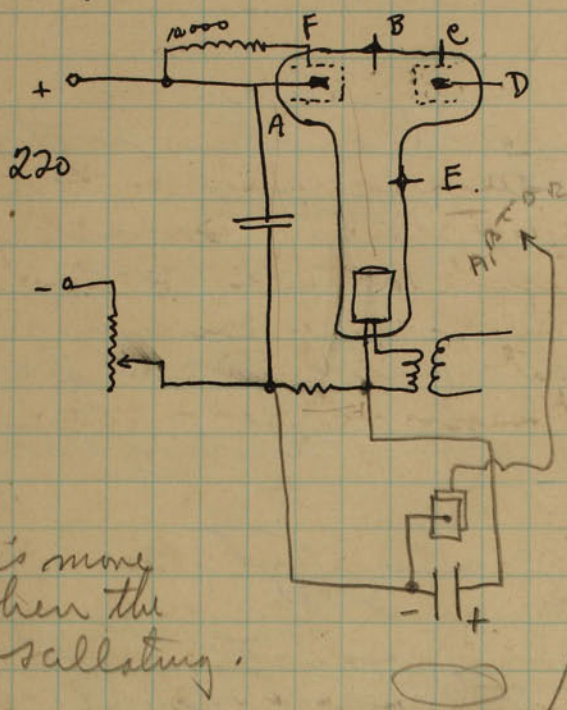Dynamic Volt-Amp Characteristics of Special
Thyratron Described on p. 136. General Radio Cathode Ray Osc.



The light is more
white when the
tube is oscillating.

small kinks showing
negative current?

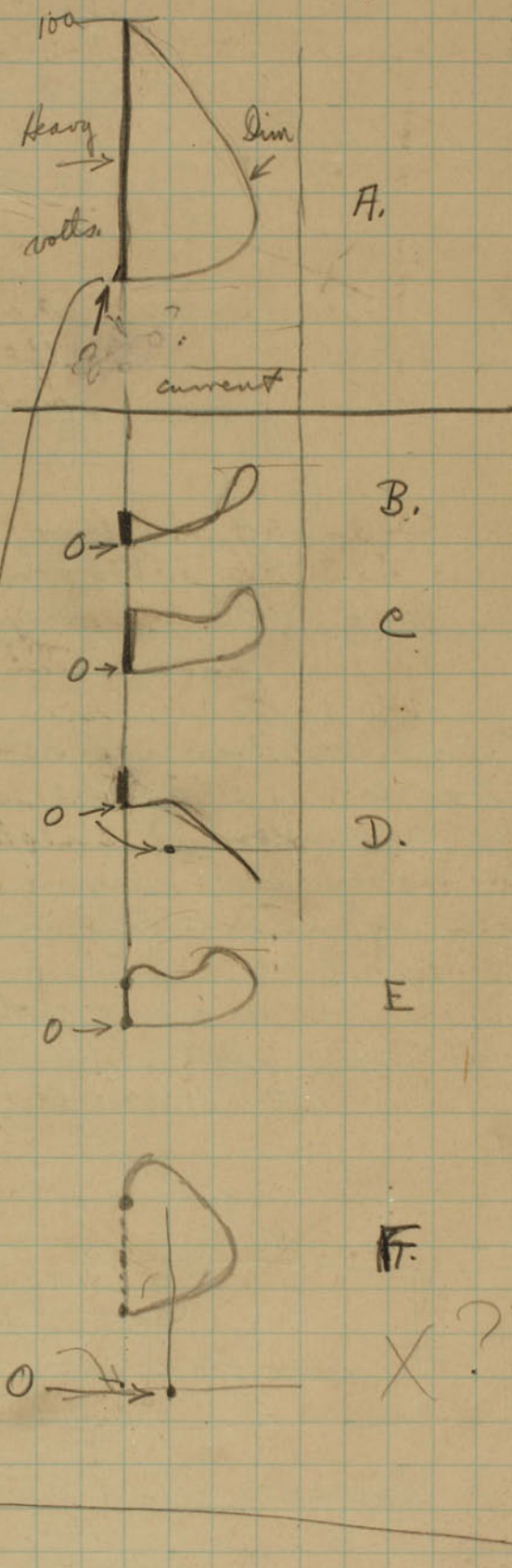


Continued experiment
to find zero of these
curves. The zero seems
to be displaced for the
current.

During the tests the
characteristic of the
phenomena grew slower.
The $V-I$ character at
the bottom became
like this.
Then the
tube stopped
oscillating
and the arc
drop was
about 230
volts.

Zero.

Current
was flowing in the tube but it was small. I used the spark
on the grid and the conduction with a 42 volt arc drop resulted.

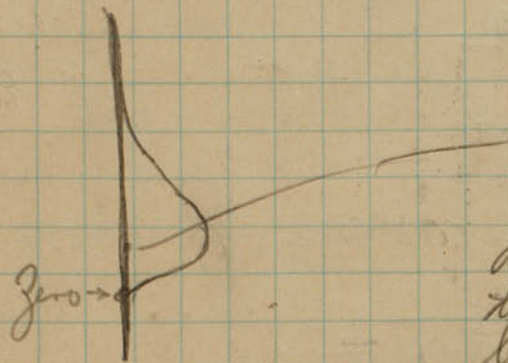Coil # 6 copper 17 turns $2\frac{1}{2}$ " in diam put in series with the discharge.



There is also a bright spot and a small kink at this point. As the voltage builds up the tube starts to conduct but cannot hold the arc.



Yesterday G.G. Smith of Raytheon inc brought over his spectroscope and we measured the wave lengths of the radiation of the light from the stroboscope built for the M. T. Lab. by McClure and Standard. 12 m.f. were used and the 600 volt tap. The 3ohm resistor in the discharge was varied from .5 to 3ohms and the following wave lengths measured when the resistance was .5. These lines do not appear when there is 3ohms or more in ~~the~~ series with the tube.

The lines that appear for the flash are

6150	Red
5887	
5869	
5683	
5420	
5122	
4968	
3981.	violet.

July 7, 1931.
H. S. Edgerton.

60 cyc Stroboscope.

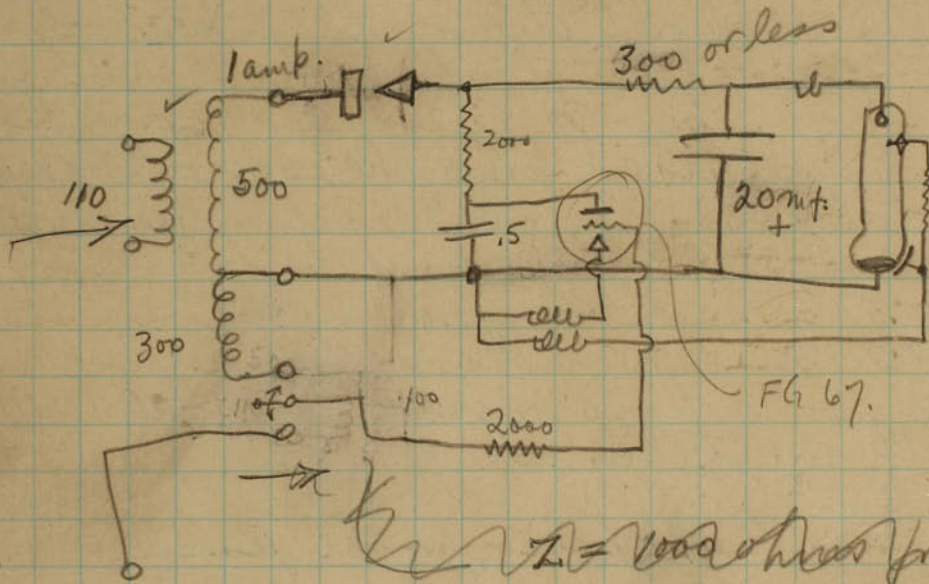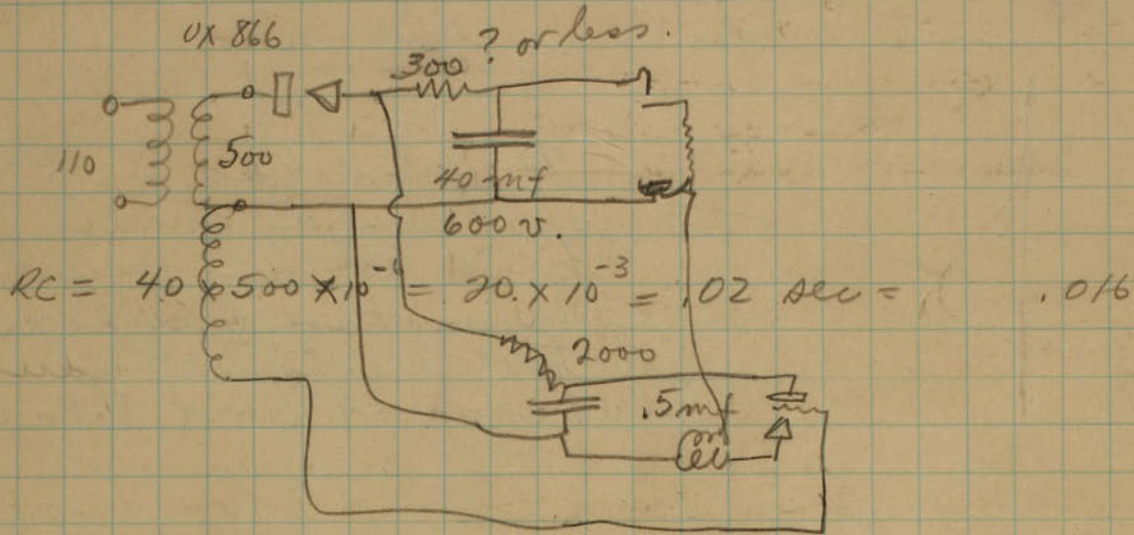

July 8 1931 Three phase Stroboscope.

Many of the disturbances to electrical power systems are caused by some unbalanced condition on the various phases. It then becomes difficult to say just what the phase angle of a synchronous machine is.

Two methods appear to be feasible. One is to use a positive sequence network to operate the stroboscope so that the phase angle of the rotor to the positive sequence component of the terminal voltage is determined. A second method is to have the stroboscope arranged to flash for each phase voltage. Then three readings will be taken which give the instantaneous angles between the rotor and the different phase or terminal voltages. Three stroboscopes could be used and three cameras.

July 9 1931 Worked on stroboscope arrangement shown on the bottom of p 148. Tried a long coope torch lamp in place of the 22 inch lamp. There was some flicker at first. I increased the small capacity to .9 m.f. Some difficulty was experienced by burn out of the grid resistances of the rectifier, a 56-33. Aside from these few minor difficulties the circuit works great.

July 10 (1931). Worked on the same stroboscope setup. Pushed the voltage up to 1500 volts on the secondary tap and it seemed to work all right. There was some small sparks or points of light on the anode when the discharge resistance was cut out. The anode also became red hot after several minutes of use. I made a long coil of lamp cord (approximately 30 turns) and put it on the tube lengthways so the magnetic field would be at right angles to the electron stream. This current



from the discharge was put through this coil. It made the light have a mottled effect and caused the tube to heat up. This showed that the arc drop in the tube had been apparently increased.

Koller of the P.E. Research Labs. has been here at Tech giving a course on thermionic emission. I took him down to see this stroboscope and he was very impressed by the red appearance of the mercury arc when it was flashing with high peak currents.

Biggs of the Hygrade company also saw the arrangement. He invited me out to their factory and I intend to go next week.

July 11 and 12 Worked on network analyzer.

July 13. Worked on vacuum system and cleaned tubes. Blew a special tube for stroboscopic work. It is long and slender.

July 14 Distilled Hg and pumped out tube of form shown on p 143. Graded seal and had anode. Hope to have another made tomorrow.

June 15, 1931. Went out to Hygrade Lamp Co in Salem and visited the factory. Saw Howard Biggs and Label there. Worked on tubes and set up exhaust system after returning.


June 16 1931 Exhausted a special tube of 14 mm Pyrex that I built. The seals were bad and leaked. This tube was about a foot long and had a ⁵⁹pool at the bottom, and a graphite anode at the top. I connected my stroboscope circuit, shown on p. 147, to the tube while it was still on the pump. As the tube got hot due to the violent discharge, the light became a very bright yellow which was so intense that it was hard to look at. I believe that the tube did not deionize in a half cycle and that the transformer was thus shorted once in a while. The transformer did ground once in a while probably for this reason. The temperature was up to 140 degrees C (meas. by bulb thermometer). There was considerable gas evolved from the tube during these tests as could be seen from the ionization gage. After some time the leak became so bad that a sufficiently high vacuum could not be maintained. R. Gernedersen helped with the tests. I built a second Pyrex tube with a long nickel rod for an anode. This tube is somewhat taller than the other and I hope the seals will not leak tomorrow when I pump it.



The experiments of today show, I believe, that more light is obtained with high pressure. Also impurities apparently help to give better light. I hope I can get all my stroboscopes to give out the intensity that I obtained today.

July 16, 1931

Pulse light Projector

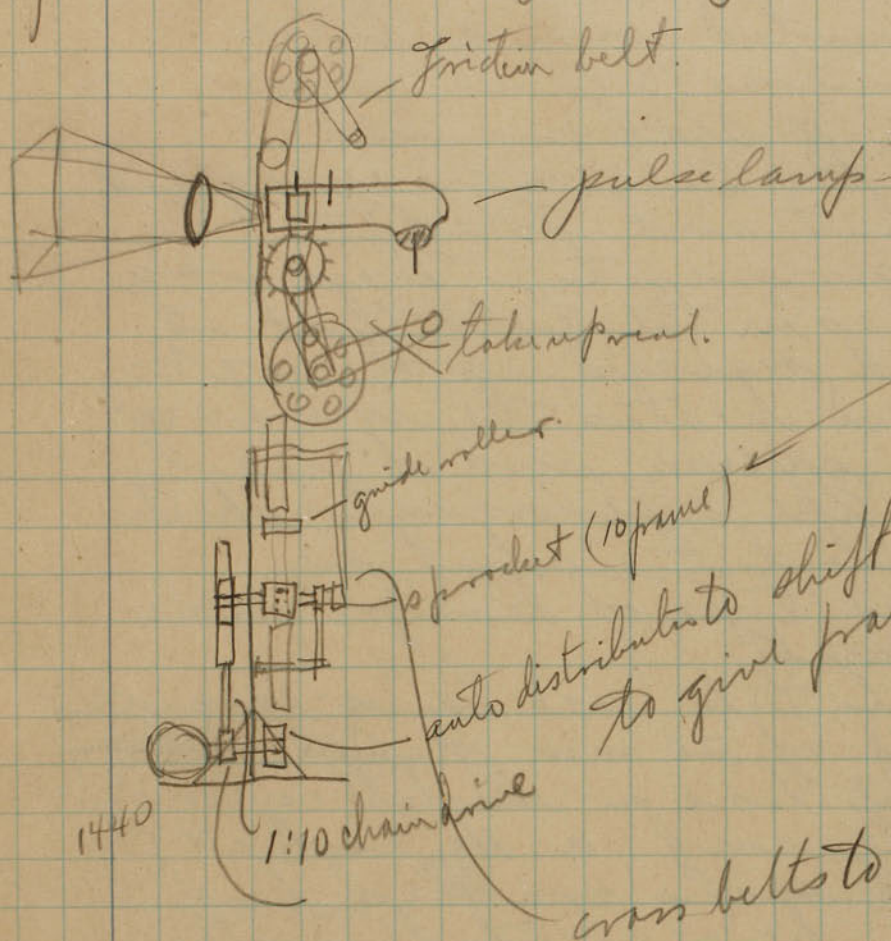

$$\frac{24}{10} = 2.4 \text{ rev per sec}$$

$$2.4 \times 60 = 144 \text{ rev per min}$$

1440

$$\frac{1760}{12} = 146.7$$



July 17, 1931. Exhausted the long 12mm Pyrex tube shown on the bottom of the preceding page. Several leaks were repaired with de Khotinsky cement and a good vacuum was obtained. The circuit of page 147 was used to excite the tube and a very bright sharp light was obtained with a capacity of a little over 4 m.f. of capacity. L.S. Bernshausen rewired the electrical circuits and put the apparatus ~~there~~ in a box so that the portability was increased.

July 18, 1931. Experimented more with the long slip tube. Prof. Stockbarger, Johnson, and Burns of the radiation lab. saw the arrangement in operation and we plan to take some spectrograms next Monday a.m.

July 19, 1931
 A. S. Elyator.
 K. S. Semtschauer
 G. S. Brown.


Experimented with a pulse lamp similar to those shown on page 143. A seal cracked shortly after the tube was energized. Cemented it shut and tried to continue experiments. There was so much gas in the tube that it splattered and messed up the walls of the tube. I heated the window to remove the sputum and it nearly sucked in. The experiments show some possibilities but an entirely new type of design needs to be employed.

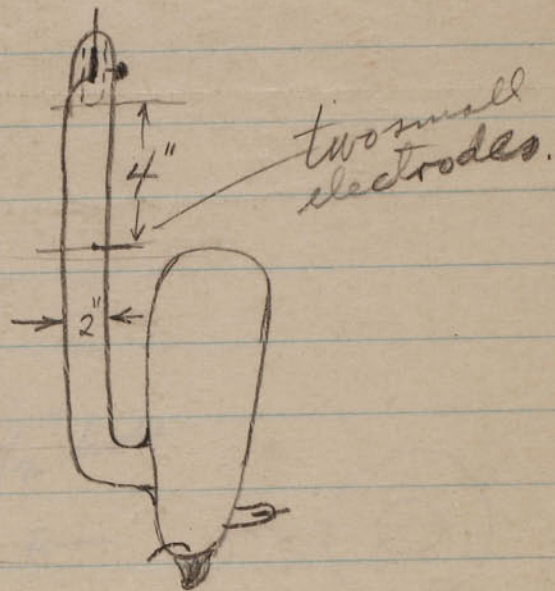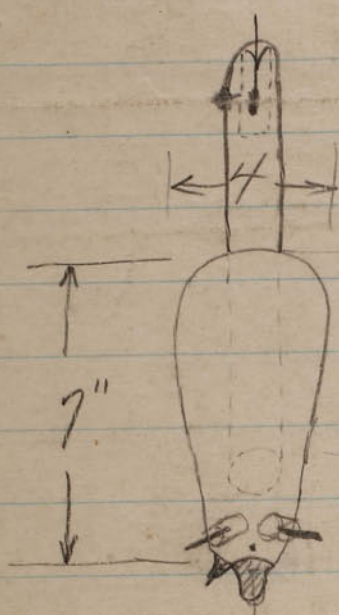While this tube was being exhausted I blew a tube of 20 mm ~~Pyrex~~ glass. The tube has a nickel cylinder for an anode and a Hg pool at the bottom. Both seals cracked but I think they can be cemented together for the preliminary experiment.



Mar. 1, 1931.
H. E. Edgerton.

Strobo-scope tubes.

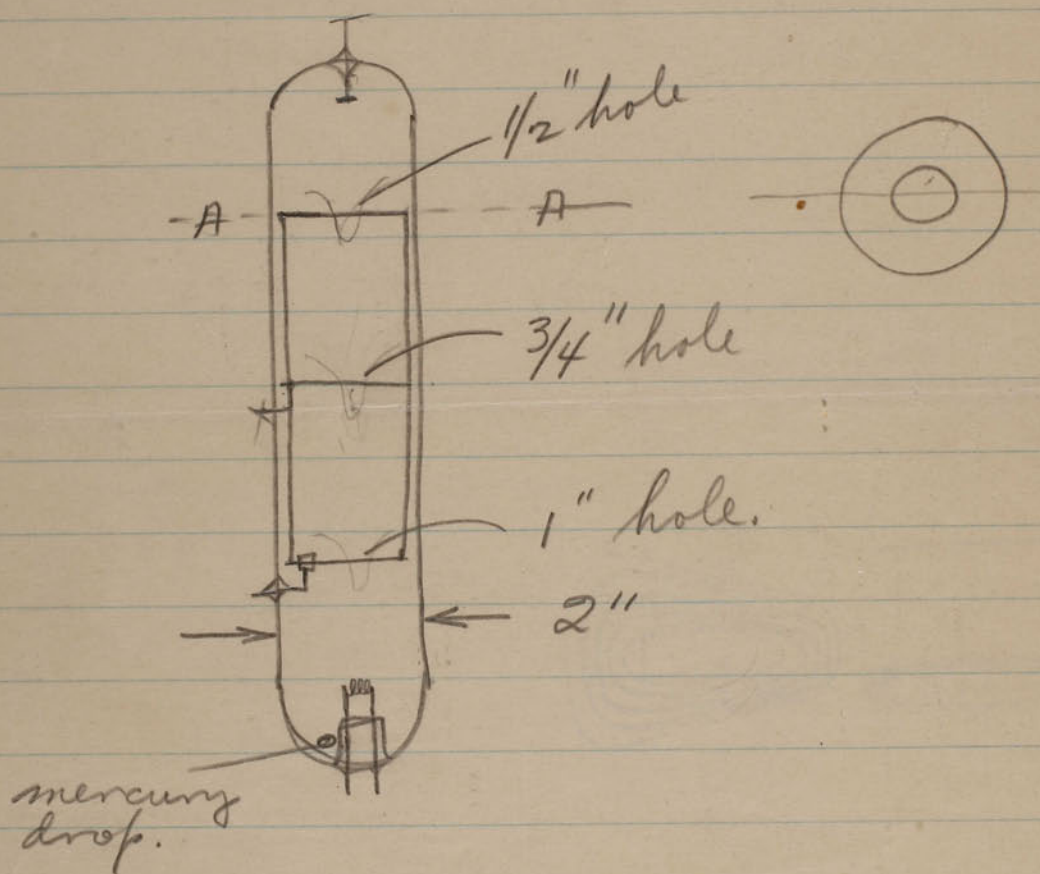

Special hot-cathode
mercury-arc tube.

H. E. Edgerton
M.I.T. Feb. 13, 1931.

